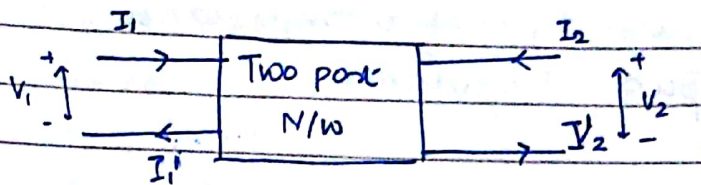


3. Two Port Network.



Amp $\Rightarrow Z_{in}, Z_{out}, V_g$ ratio, I ratio. $\Rightarrow$ parameters

$\rightarrow Z$ parameter (Impedances)

$\rightarrow Y$ parameter (Admittances)

$\rightarrow H$ parameter (Hybrid)

$\rightarrow ABCD$ (transmission parameter).

* Z parameter: (o/c parameter)

$$V_1 = f(I_1, I_2)$$

$$V_2 = f(I_1, I_2)$$


$$\Rightarrow V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

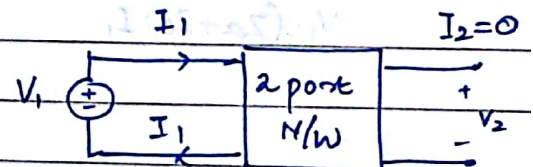

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

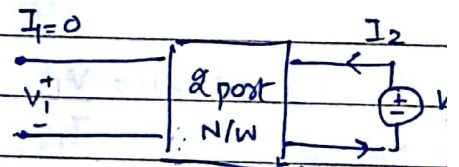


Z_{11} = open circuit input impedance


Z_{21} = open ckt forward transfer impedance

Z_{12} = o/c reverse transfer impedance

Z_{22} = o/c output impedance

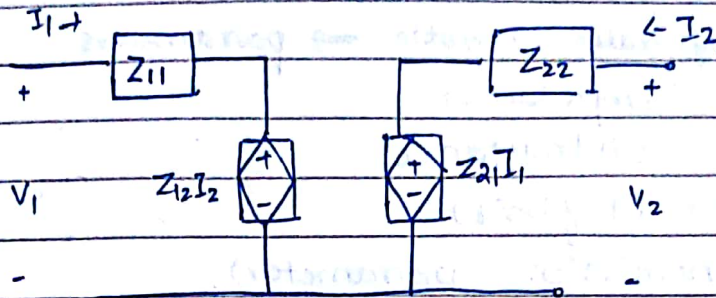

eg 1:

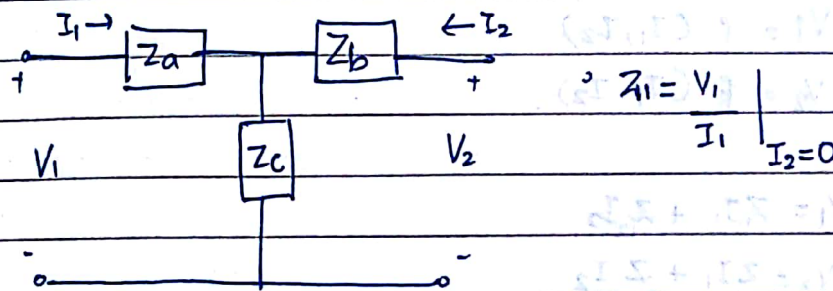


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

• To find Z_{11}

$$V_1 = (Z_a + Z_c) I_1$$

$$V_1 =$$

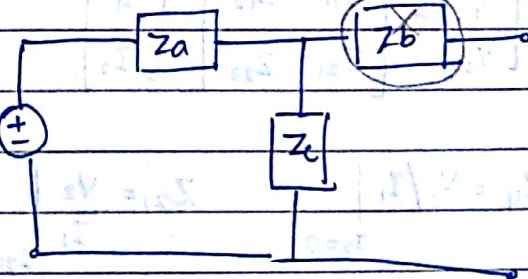

$$\Rightarrow Z_{11} = \frac{V_1}{I_1} = \frac{(Z_a + Z_c) I_1}{I_1} = (Z_a + Z_c) \Omega$$

- For $Z_{11} = \frac{V_1}{I_1} \mid I_2=0$ (same ckt)


$V_1 =$ voltage across Z_c

$$V_1 = V_{Zc}$$

$$V_1 = Z_c \times I_1$$


$$Z_{11} = \frac{Z_c \times I_1}{I_1} = Z_c \Omega$$

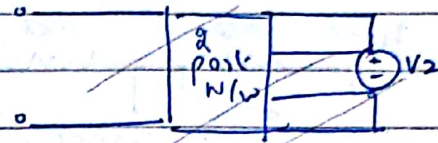- For $Z_{12} = Z_{21} = \frac{V_1}{I_2} \mid I_1=0$



$$V_1 = Z_c I_2$$
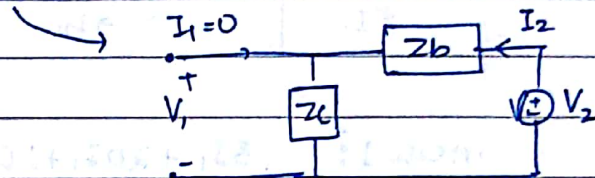
$$Z_{12} = \frac{Z_c I_2}{I_2} = Z_c \Omega$$



Illy


$$Z_{22} = \frac{V_2}{I_2} \mid I_1=0 = \frac{(Z_b + Z_c) I_2}{I_2} = (Z_b + Z_c) \Omega$$

$$\Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z = \begin{bmatrix} Z_c & Z_c \\ Z_c & (Z_b + Z_c) \end{bmatrix} \Omega$$

* By mesh analysis.

mesh 1:

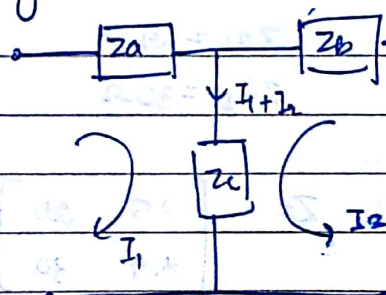

$$-V_1 + Z_a I_1 + Z_c (I_1 + I_2) = 0$$

$$V_1 = (Z_a + Z_c) I_1 + Z_c I_2 \quad \text{--- (1)}$$

mesh 2:


$$-V_2 + Z_b I_2 + Z_c (I_1 + I_2) = 0$$

$$V_2 = Z_c I_1 + (Z_b + Z_c) I_2 \quad \text{--- (2)}$$

$Z_{21} = Z_{12}$ symmetric network
system is reciprocal

$Z_{11} = Z_{22} \rightarrow$ system is symmetric

eg 2. * Given this network, find the Z parameter

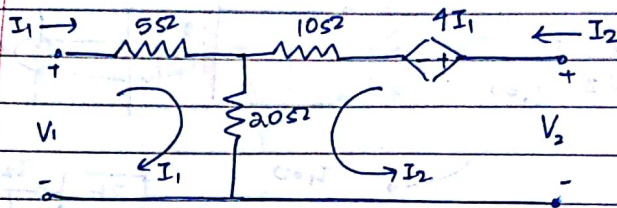

mesh 1: $5I_1 + 20I_1 + 20I_2 = V_1$ — ①

mesh 2: $4I_1 + 10I_2 + 20I_2 + 20I_1 = V_2$ — ②

$25I_1 + 20I_2 = V_1$ — ①

$24I_1 + 30I_2 = V_2$ — ②

$\therefore Z_{11} \Rightarrow$

$V_1 = Z_{11}I_1 + Z_{12}I_2$

$V_2 = Z_{21}I_1 + Z_{22}I_2$

comparing eq

$Z_{11} = 25\Omega$

$Z_{12} = 20\Omega$


$Z_{21} = 24\Omega$

$Z_{22} = 30\Omega$

$Z = \begin{bmatrix} 25 & 20 \\ 24 & 30 \end{bmatrix} = 270\Omega$

eg 3 *

eg 4.

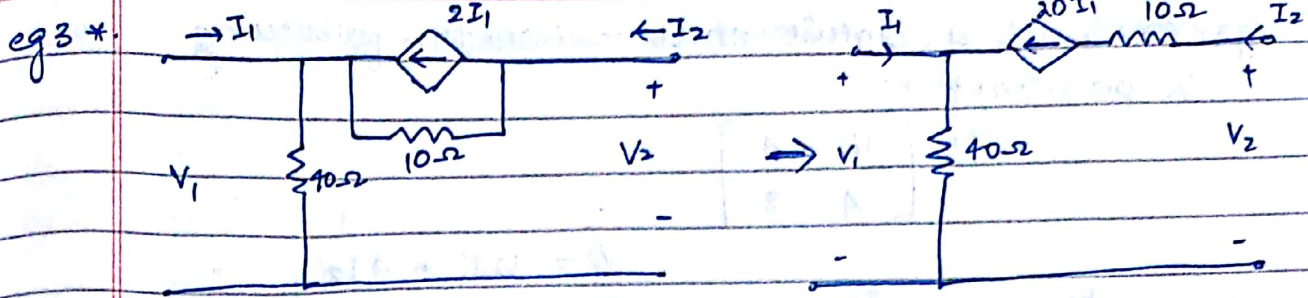

$$V_1 = 40I_1 + 40I_2 \quad \text{--- (1)}$$

$$V_2 = -20I_1 + 50I_2 + 40I_1 \quad \text{--- (2)}$$


comparing $Z_{11} = 40$

$$Z_{12} = 40$$

$$Z_{21} = 20$$

$$Z_{22} = 50$$
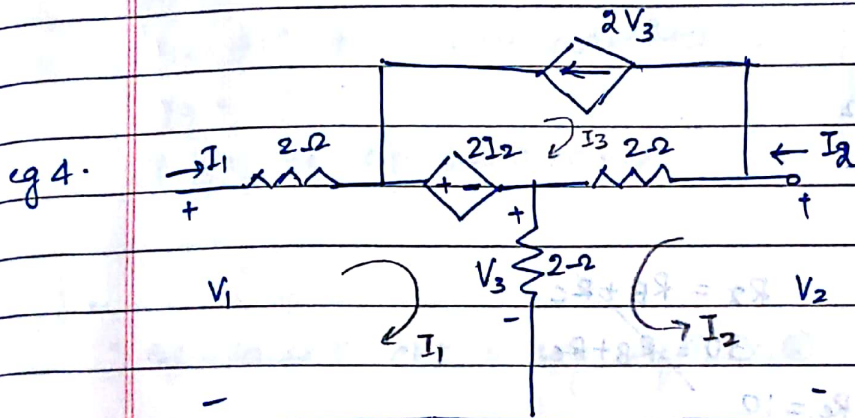
$$Z = \begin{bmatrix} 40 & 40 \\ 20 & 50 \end{bmatrix}$$



$$I_3 = -2V_3$$

$$V_3 = 2(I_1 + I_2)$$

$$\Rightarrow I_3 = -4I_1 - 4I_2$$

mesh 1:

$$-V_1 + 2I_1 + 2I_2 + 2(I_1 + I_2) = 0$$

$$4I_1 + 4I_2 = V_1$$

mesh 2:

$$2(I_2 + I_3) + 2(I_2 + I_1) = V_2$$

$$2I_1 + 4I_2 + 2I_3 = V_2$$

$$2I_1 + 4I_2 - 8I_1 - 8I_2 = V_2$$


$$-6I_1 - 4I_2 = V_2$$

$$Z_{11} = 4, Z_{12} = 4, Z_{21} = -6, Z_{22} = -4 \Omega$$

$$Z = \begin{bmatrix} 4 & 4 \\ -6 & -4 \end{bmatrix}$$

eg5. construct a circuit that realises the following Z parameter.
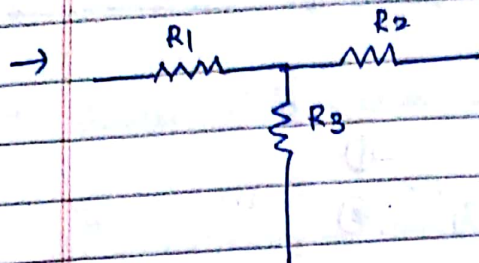
$$Z = \begin{bmatrix} 12 & 4 \\ 4 & 8 \end{bmatrix}$$



$$V_1 = 12I_1 + 4I_2$$

$$V_2 = 4I_1 + 8I_2$$

$$Z_{11} = 12 \quad Z_{12} = 4$$

$$Z_{21} = 4 \quad Z_{22} = 8$$

$$R_1 = 8\Omega$$

$$R_3 = 4\Omega$$

$$R_2 = 4\Omega$$

$$Z_{11} = R_1 + R_3 = 8 + 4 = 12$$

$$Z_{22} = R_2 + R_3 = 4 + 4 = 8$$

Z_{12} & Z_{21} are same

$$R_1 = 8 \quad R_2 = 4 \quad R_3 = 4$$

eg6:

$$Z = \begin{bmatrix} 40 & 10 \\ 20 & 30 \end{bmatrix} \Omega$$

$$R_1 = 40 + R_A + R_C$$

$$R_2 = R_B + R_C$$

$$R_1 = 40 = R_A + R_C$$

$$30 = R_B + R_C$$


$$R_3 = R_C = 10$$

$$40 = R_A + 10$$

$$30 = R_B + 10$$

$$R_A = 30$$

$$R_B = 20$$

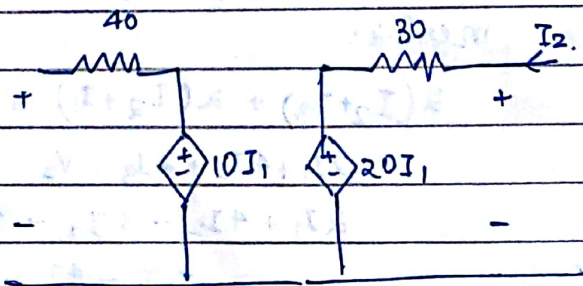

* Y parameters (admittance parameters) / sh parameter

$$I_1 = f(V_1, V_2)$$


$$I_2 = f(V_1, V_2)$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

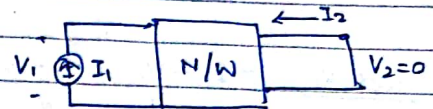

$$Y_{21} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

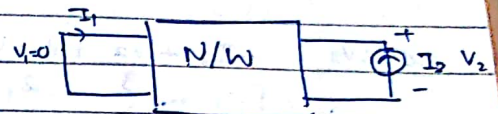

Y_{11} = s/c i/p admittance


Y_{12} = s/c transfer admittance

Y_{21} = "


Y_{22} = s/c o/p admittance

} equal $\rightarrow$ reciprocal
if $Y_{22} = Y_{11} \rightarrow$ symmetric

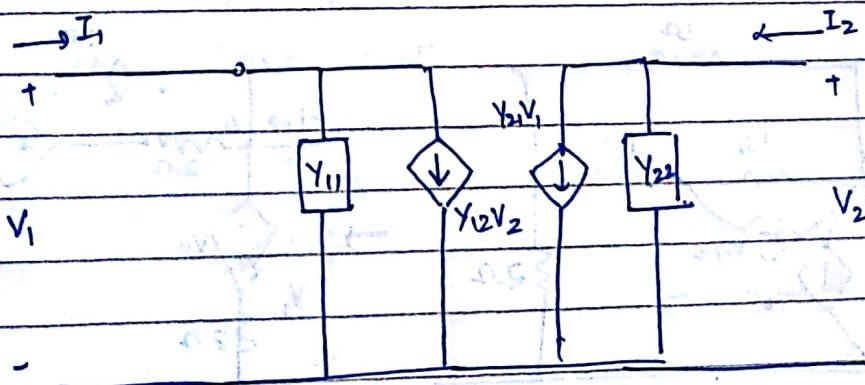• equivalent ckt using eq (1) & (2) for y parameter





for $y \rightarrow$ make in π network

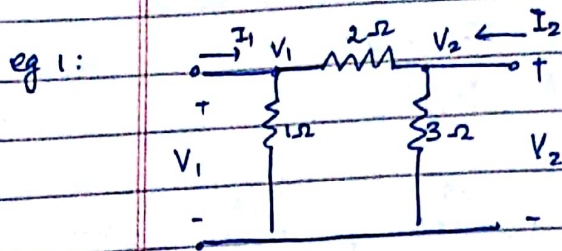

node V_1
$$-I_1 + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = 0 \Rightarrow V_1 \left[1 + \frac{1}{2} \right] + V_2 \left[-\frac{1}{2} \right] = I_1$$

node V_2
$$-I_2 + \frac{V_2}{3} + \frac{V_2 - V_1}{2} = 0 \Rightarrow V_1 \left[-\frac{1}{2} \right] + V_2 \left[\frac{1}{3} + \frac{1}{2} \right] = I_2$$

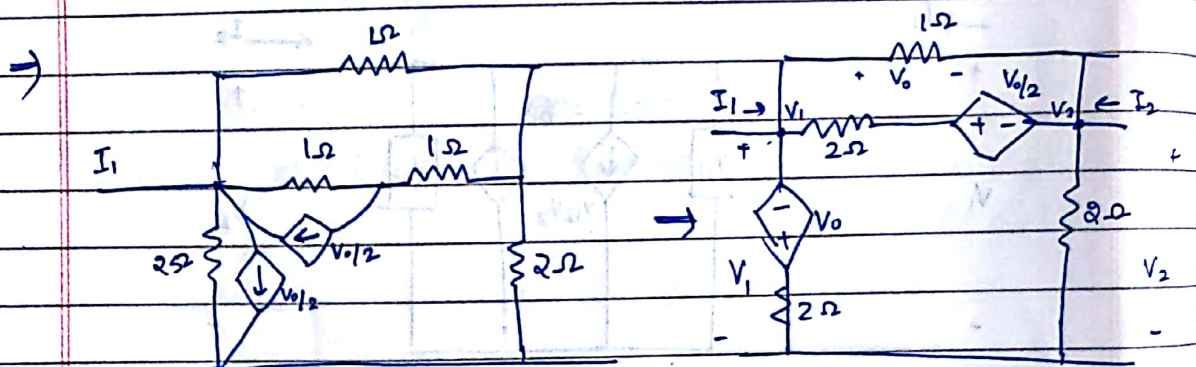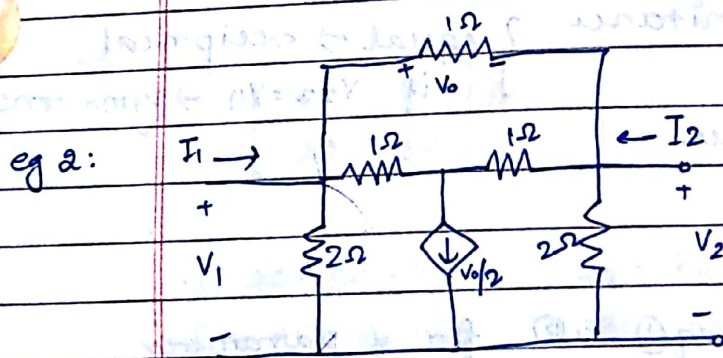comparing $Y_{11} = \frac{3}{2} \Omega$ $Y_{12} = -\frac{1}{2} \Omega$
 $Y_{21} = -\frac{1}{2} \Omega$ $Y_{22} = \frac{5}{6} \Omega$



store
67

For node 1:
$$-I_1 + \frac{V_1 + V_0}{2} + \frac{V_1 - V_0/2 - V_2}{2} + \frac{V_1 - V_2}{1} = 0 \quad \text{--- (1)}$$

For node 2:
$$-I_2 + \frac{V_2 + V_0/2 - V_1}{2} + \frac{V_2}{2} + \frac{V_2 - V_1}{1} = 0 \quad \text{--- (2)}$$

① $\rightarrow V_1 \left[\frac{1}{2} + \frac{1}{2} + 1 \right] + V_2 \left[-\frac{1}{2} - 1 \right] + V_0 \left[\frac{1}{2} - \frac{1}{4} \right] = 0$
As $V_0 = V_1 - V_2$

$$V_1 \left[\frac{1}{2} + \frac{1}{2} + 1 \right] + V_2 \left[-\frac{1}{2} - 1 \right] + (V_1 - V_2) \left(\frac{1}{2} - \frac{1}{4} \right) = 0$$

$$V_1 \left[\frac{1}{2} + \frac{1}{2} + 1 + \frac{1}{2} - \frac{1}{4} \right] + V_2 \left[-\frac{1}{2} - 1 - \frac{1}{2} + \frac{1}{4} \right] = 0 \quad \text{--- (1)}$$

② $\rightarrow V_1 \left[-\frac{1}{2} - 1 \right] + V_2 \left[\frac{1}{2} + \frac{1}{2} \right] + V_0 \left[\frac{1}{4} \right] = 0$

As $V_0 = V_1 - V_2$

$$V_1 \left[-\frac{1}{2} - 1 + \frac{1}{4} \right] + V_2 \left[\frac{1}{2} + \frac{1}{2} - \frac{1}{4} \right] = 0 \quad \text{--- (2)}$$

comparing the eqs

$$Y_{11} = 2.25$$


$$Y_{12} = -1.75$$

$$\rightarrow Y = \begin{bmatrix} 2.25 & -1.75 \\ -1.25 & 1.75 \end{bmatrix}$$

$$Y_{21} = -1.25$$

$$Y_{22} = 1.75$$

eg 3:

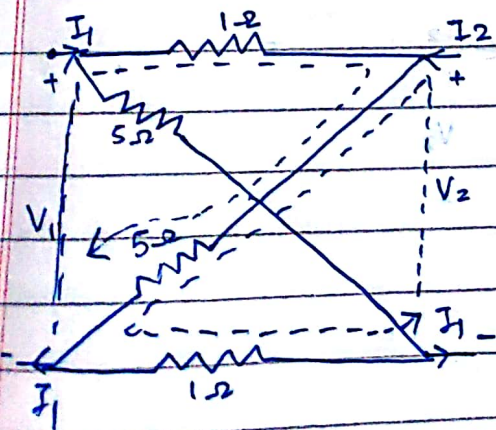


mesh 1:

$$-V_1 + 1(I_1 - I_2) + 5(I_1 + I_2) = 0$$

mesh 2:

$$-V_2 + 5(I_1 + I_2) + 1(I_2 - I_1) = 0$$


Redrawing the circuit

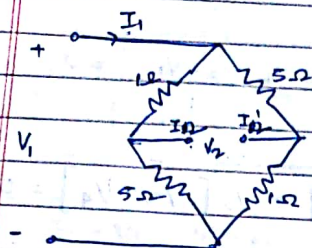

mesh 1:

$$-V_1 + 1(I_1 - I_2) + 5(I_1 + I_2) = 0$$

$$V_1 = 6I_1 + 4I_2$$

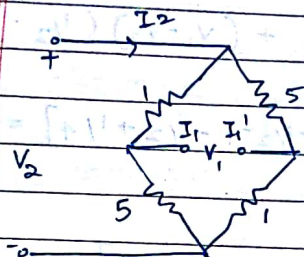

mesh 2:

$$-V_2 + 1(I_2 + I_1)$$

$$-V_2 + 1(I_2 - I_1) + 5(I_2 + I_1) = 0$$

$$V_2 = 6I_2 + 4I_1$$

Comparing

$$Z_{11} = 6$$


$$Z_{21} = 4$$

$$Z_{12} = 4$$

$$Z_{22} = 6$$

$$Z = \begin{bmatrix} 6 & 4 \\ 4 & 6 \end{bmatrix}$$

Q.4 Find y parameter and z parameter

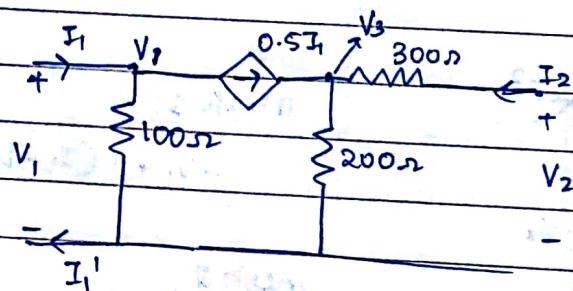

By nodal analysis.

node V_1

$$\frac{V_1}{100} - I_1 + \frac{V_1}{100} + 0.5 I_1 = 0$$

$$\frac{V_1}{100} - 0.5 I_1 = 0 \quad \text{--- (1)}$$

$$V_1 = 50 I_1$$

$$I_1 = \frac{V_1}{50} \quad \text{--- (2)}$$

node V_3

$$-0.5 I_1 + \frac{V_3}{200} + \frac{V_3 - V_2}{300} - I_2 = 0$$

$$\frac{V_3}{200} - 0.5 I_1 - I_2 = 0 \quad \text{--- (3)}$$

Also =

$$\frac{V_2 - V_3}{300} = I_2$$

$$V_2 - 300 I_2 = V_3 \quad \text{--- (3)}$$

Sub eq (3) in eq (2)

$$\frac{V_2 - 300 I_2}{200} - 0.5 I_1 - I_2 = 0$$

$$\frac{V_2}{200} - 0.5 I_1 - 301 I_2 = 0 \quad \text{--- (4)}$$

$$Z_{11} = 50 \quad Z_{12} = 0$$

$$Z_{21} = 100 \quad Z_{22} = 500$$

$$V_2 = 100 I_1 + 500 I_2$$

$$Y_{11} = \frac{1}{50} \quad Y_{12} = 0$$

$$Y_{21} = \frac{1}{100} \quad Y_{22} = \frac{1}{500}$$

$$Y_{21} = -0.004 \text{ S}$$

$$I_1 = \frac{V_2}{100} \quad I_2 = \frac{V_2}{500} - \frac{100 I_1}{500} \quad \text{--- (5)}$$

$$I_1 = \frac{V_2}{100} - \frac{500 I_2}{100} \quad \text{--- (6)}$$

got
 Y_{11} &
 Y_{12}
from
eq (2)

eq (5) composing with


$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

I_1 is not reqd $\therefore$ eliminate

$$-\frac{100}{500} I_1 \text{ in eq (5)}$$

$$\therefore \text{eq (5)} \Rightarrow I_2 = \frac{-1(0.002 V_1)}{5} + \frac{V_2}{500}$$

eg 5: Find y and z parameters.

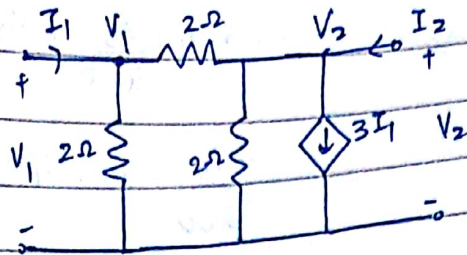

Nodal analysis:

node V_1 :

$$-I_1 + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 \left[\frac{1}{2} + \frac{1}{2} \right] + V_2 \left[\frac{-1}{2} \right] = I_1$$

$$\frac{V_1 - V_2}{2} = I_1 \quad \text{--- (1)}$$

node 2

$$\frac{V_2}{2} + \frac{V_2 - V_1}{2} + 3I_1 - I_2 = 0$$

$$\frac{V_2}{2} + V_1 \left[\frac{-1}{2} \right] + V_2 \left[\frac{1}{2} \right] + 3I_1 = I_2$$

$$\frac{V_2}{2} + \frac{-V_1}{2} + \frac{V_2}{2} + 3V_1 - 3V_2 = I_2$$

$$\frac{5V_1 - V_2}{2} = I_2 \quad \text{--- (2)}$$

$$Y_{11} = 1 \quad Y_{12} = -0.5$$

$$Y_{21} = 2.5 \quad Y_{22} = -0.5$$

$$Y = \begin{bmatrix} 1 & -0.5 \\ 2.5 & -0.5 \end{bmatrix}$$

from eq (1) $\Rightarrow I_1 = V_1 - 0.5V_2$

$$V_1 = I_1 + 0.5V_2$$

$$I_2 = 2.5V_1 - 0.5V_2$$

$$V_2 = \frac{2.5V_1 - I_2}{0.5}$$

Rearrange $\left[\begin{array}{l} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{array} \right]$

$$\Rightarrow V_1 = I_1 + 0.5V_2$$

$$V_1 = I_1 + 0.5(-3.3I_1 + 1.33I_2)$$

$$V_1 = I_1 - 1.66I_1 + 0.665I_2$$

$$V_1 = -0.66I_1 + 0.66I_2$$

$$V_2 = 5[I_1 + 0.5V_2] - \frac{I_2}{0.5}$$

$$-0.5V_2 = 5I_1 - \frac{I_2}{0.5}$$

$$V_2 = -3.3I_1 + 1.33I_2$$

$$Z = \begin{bmatrix} -0.66 & 0.66 \\ -3.3 & 1.33 \end{bmatrix}$$


hybrid parameter.

$$V_1 = f(I_1, V_2)$$

$$I_2 = f(I_1, V_2)$$

$$V_1 = H_{11}I_1 + H_{12}V_2$$

$$I_2 = H_{21}I_1 + H_{22}V_2$$

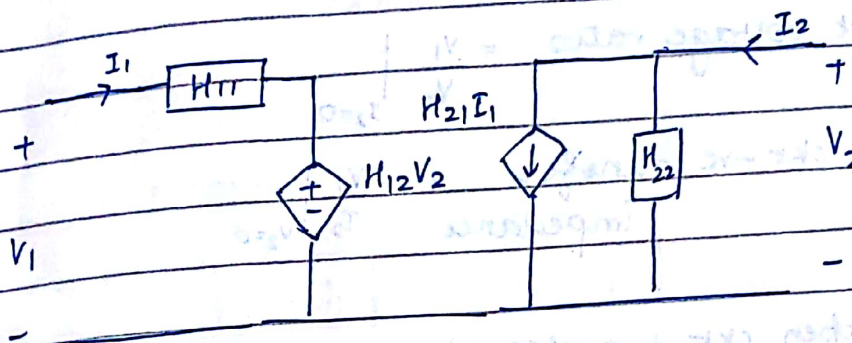

$$H_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0} = \text{s/c input impedance}$$

$$H_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0} = \text{o/c Reverse voltage gain}$$


$$H_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0} = \text{s/c forward current gain}$$

$$H_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0} = \text{o/c op admittance}$$

$$* H_{12} = -H_{21} \rightarrow \text{Reciprocal}$$

$$* \Delta H = 1 \rightarrow \text{Symmetric.}$$

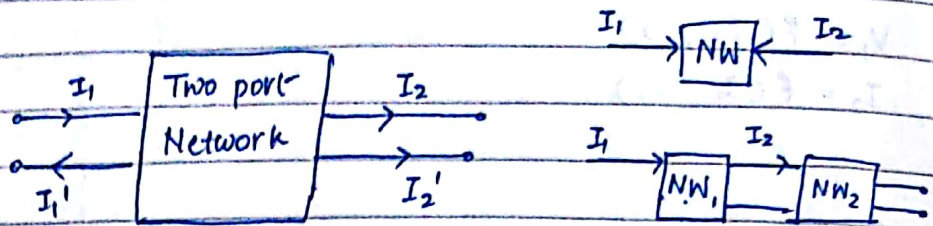* T-transmission parameter / ABCD parameter



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \text{open ckt voltage ratio} = \frac{V_1}{V_2} \bigg|_{I_2=0}$$

$$B = \text{short ckt -ve transfer impedance} = \frac{-V_1}{I_2} \bigg|_{V_2=0}$$


$$C = \text{open ckt transfer admittance} = \frac{I_1}{V_2} \bigg|_{I_2=0}$$

$$D = \text{negative short circuit current ratio} = \frac{-I_1}{I_2} \bigg|_{V_2=0}$$

* $AD - BC = 1 \rightarrow \text{Reciprocal}$

* $A = D \rightarrow \text{Symmetry}$

eg 2: Find all the parameters.

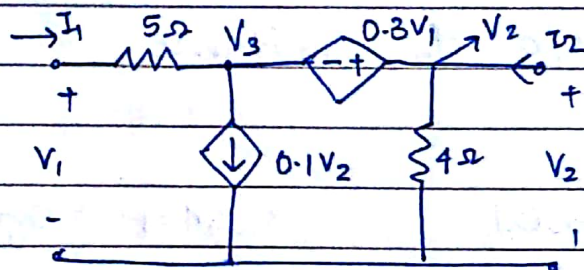

Supernode

store
67

source eq: $V_2 - V_3 = 0.3V_1$ — ①

$V_2 - 0.3V_1 = V_3$ — ①

node(V_3, V_2)

$$\frac{-I_1 + 0.1V_2 + \frac{V_2}{4} - I_2}{4} = 0$$
 — ②

$V_2 = 2.85I_1 + 2.85I_2$ — ③

$I_1 = \frac{V_1 - V_3}{5}$

$V_3 = V_1 - 5I_1$

sub in eq ①

① $\Rightarrow V_2 - V_1 + 5I_1 = 0.3V_1$

$1.3V_1 = 5I_1 + V_2$

$I_1 = 0.26V_1 - 0.2V_2$ — ④

$I_1 = Y_{11}V_1 + Y_{12}V_2$

$V_1 = Z_{11}V_1 + Z_{12}V_2$

$I_2 = Y_{21}V_1 + Y_{22}V_2$

$V_2 = Z_{21}V_1 + Z_{22}V_2$

$Y_{11} = 0.26$

$Y_{12} = -0.2$

$Z_{21} = 2.85$

$Z_{22} = 2.85$

③ $\Rightarrow V_2 = 2.85(0.26V_1 - 0.2V_2) + 2.85I_2$

$V_2 = 0.741V_1 - 0.57V_2 + 2.85I_2$

$I_2 = -0.26V_1 + 0.55V_2$ — ⑤

$Y_{21} = -0.26$

$Y_{22} = 0.55$

$$Y = \begin{bmatrix} 0.26 & -0.2 \\ -0.26 & 0.55 \end{bmatrix}$$

$$I_1 = 0.26V_1 - 0.2V_2$$

$$= 0.26V_1 - 0.2(2.85I_1 + 2.85I_2)$$

$$I_1 = 0.26V_1 - 0.57I_1 - 0.57I_2$$

$$V_1 = 6.038I_1 + 2.192I_2 \quad \text{--- (6)}$$

$$Z_{11} = 6.03 \quad Z_{12} = 2.19$$

$$Z = \begin{bmatrix} 6.03 & 2.19 \\ 2.85 & 2.85 \end{bmatrix}$$

put eq (5) in eq (6)

$$V_1 = 6.038I_1 + 2.192(-0.26V_1 + 0.550V_2)$$

$$V_1 = 6.038I_1 - 0.569V_1 + 1.2056V_2$$

$$1.569V_1 = 6.038I_1 + 1.2056V_2$$

$$V_1 = 3.848I_1 + 0.768V_2$$

$$I_2 = -0.26V_1 + 0.550V_2 \quad \text{put eq (6) in eq (5)}$$

$$I_2 = -0.26(6.038I_1 + 2.192I_2) + 0.550V_2$$

$$I_2 = -1.56I_1 - 0.569I_2 + 0.550V_2$$

$$I_2 = -0.994I_1 + 0.350V_2 \quad \text{--- (7)}$$

$$h_{11} = 3.848 \quad h_{12} = 0.768$$

$$h_{21} = -0.994 \quad h_{22} = 0.350$$

$$H = \begin{bmatrix} 3.848 & 0.76 \\ -0.99 & 0.355 \end{bmatrix}$$

transmission

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$\text{eq ⑥} \rightarrow V_1 = 6.038I_1 + 2.19I_2 \quad (\text{put eq ④})$$

$$V_1 = 6.036(0.26V_1 - 0.26V_2) + 2.19I_2$$

$$V_1 = 1.569V_1 - 1.569V_2 + 2.19I_2$$

$$V_1 = 2.75V_2 - 3.84I_2$$

$$\text{eq ④} \rightarrow I_1 = 0.26V_1 - 0.26V_2$$

$$I_1 = 0.26(2.75V_2 - 3.84I_2) - 0.26V_2$$

$$\text{eq ⑤}$$

$$I_1 = \frac{0.35V_2}{0.994} - \frac{I_2}{0.994}$$

$$I_1 = 0.352V_2 - 1.066I_2$$

$$A = 2.75$$

$$B = 3.84$$

Trans

$$C = 0.35$$

$$D = 1.066$$

$$\therefore T = \begin{bmatrix} 2.75 & 3.84 \\ 0.35 & 1.066 \end{bmatrix}$$


Z

Y

$$Z \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \quad Y \begin{bmatrix} Y_{22}/\Delta Y & -Y_{12}/\Delta Y \\ -Y_{21}/\Delta Y & Y_{11}/\Delta Y \end{bmatrix}$$

$$Y \begin{bmatrix} Z_{22}/\Delta Z & -Z_{12}/\Delta Z \\ -Z_{21}/\Delta Z & Z_{11}/\Delta Z \end{bmatrix} \quad \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

eg 7.

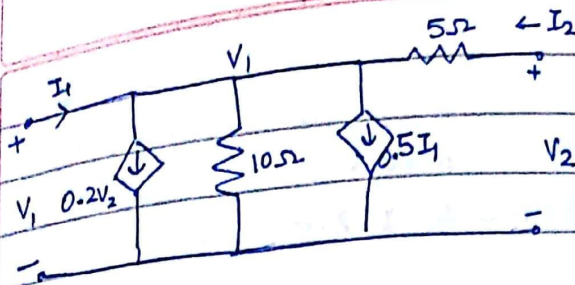

By nodal V_1 :

$$-I_1 + \frac{V_1}{10} + 0.2V_2 + 0.5I_1 + \frac{V_1 - V_2}{5} = 0$$

$$V_1 \left[\frac{1}{10} + \frac{1}{5} \right] + V_2 \left[-\frac{1}{5} + 0.2 \right] + I_1 [0.5 - 1] = 0$$

node V_2 :

$$\frac{V_2 - V_1}{5} - I_2 = 0$$

$$\frac{V_2 - V_1}{5} = I_2$$

eq ① $I_1 = +0.6V_1 + 0$

$V_1 = 1.667I_1 + 0$ — (3)

eq ② $I_2 = -0.2V_1 + 0.2V_2$

$V_2 = \frac{I_2}{0.2} + \frac{0.2V_1}{0.2}$

$Y_{11} = 0.6$ $Y_{12} = 0$

$V_2 = 5I_2 + V_1$ — (4)

$Y_{21} = -0.2$ $Y_{22} = 0.2$

$V_2 = 5I_2 + 1.667I_1$ — (5)

$X_{11} = 1.66$ $X_{12} = 0$

~~$X_{21} = 5$~~ ~~$X_{22} = 1.66$~~

$X_{21} = 1.66$ $X_{22} = 5$

$V_1 = H_{11} I_1 + H_{12} V_2$

$I_2 = H_{21} I_1 + H_{22} V_2$

$$\text{eq (3)} \rightarrow V_1 = 1.667 I_1 + 0.$$

$$H_{11} = 1.66 \quad H_{12} = 0$$

$$H_{21} = -0.33 \quad H_{22} = 0.2.$$

$$\begin{aligned} \text{eq (5)} \rightarrow I_2 &= \frac{V_2}{5} - \frac{I_1(1.66)}{5} \\ &= 0.2 V_2 - 0.332 I_1 \end{aligned}$$

$$H = \begin{bmatrix} 1.667 & 0 \\ 0.2 & -0.332 \end{bmatrix}$$

T parameter

$$\text{eq (4)} \rightarrow V_1 = A V_2 - B I_2$$

$$\text{eq (5)} \rightarrow I_1 = C V_2 - D I_2$$


$$V_1 = V_2 - 5 I_2$$

$$I_1 = \frac{V_2}{1.66} - \frac{5 I_2}{1.66}$$

$$A = 1 \quad B = +5$$

$$C = 0.602 \quad D = 3.01$$
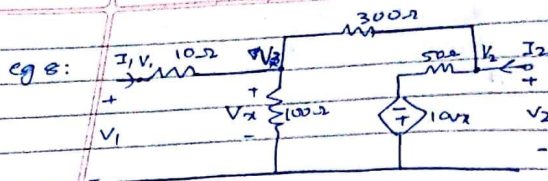
$$T = \begin{bmatrix} 1 & 5 \\ 0.602 & 3.01 \end{bmatrix}$$



node V_3

$$\frac{V_3 - V_1}{10} + \frac{V_3}{100} + \frac{V_3 - V_2}{300} = 0$$

$$\textcircled{1} \rightarrow V_1 \left[-\frac{1}{10} \right] + V_2 \left[-\frac{1}{300} \right] + V_3 \left[\frac{1}{10} + \frac{1}{100} + \frac{1}{300} \right] = 0$$

node V_2

$$\frac{V_2 - V_3}{300} + \frac{V_2 + 10V_3}{50} - I_2 = 0$$

$$\frac{V_2 - V_3}{300} + \frac{V_2 + 10V_3}{50} - I_2 = 0$$

$$\textcircled{2} \rightarrow V_2 \left[\frac{1}{300} + \frac{1}{50} \right] + V_3 \left[-\frac{1}{300} + \frac{10}{50} \right] = I_2$$

node V_1

$$-I_1 + \frac{V_1 - V_3}{10} = 0$$

$$I_1 = \frac{V_1 - V_3}{10}$$

$$\boxed{-10I_1 + V_1 = V_3} \quad \text{--- (*)}$$

$$10I_1 = \dots$$

$$I_1 = 0.1V_1 - 0.1V_3$$

$$V_3 =$$

70.

$$\textcircled{1} \rightarrow V_1 \left[-\frac{1}{10} \right] + V_2 \left[-\frac{1}{300} \right] + (0.1V_1 - 0.1V_3) - (0.113) = 0$$

eq ①

$$-0.1V_1 - 0.003V_2 + \overbrace{(V_1 - 10I_1)(0.113)}^{\text{store 67}} = 0 \quad \text{due to eq ④}$$

$$-0.1V_1 - 0.003V_2 + 0.113V_1 - 1.13I_1 = 0$$

$$I_1 = 0.0115V_1 + 0.0026V_2$$

$$Y_{11} = 0.0115 \quad Y_{12} = -0.0026$$

eq ②

$$V_2(0.023) + 0.196V_3 = I_2$$

← due to eq ④

$$V_2(0.023) + (0.196)(0.1V_1 - 0.1 - 10I_1 + V_1) = I_2$$

$$0.0023V_2 - 1.96I_1 + 0.196V_1 = I_2$$

sub eq ③ in this

$$0.0023V_2 - 0.0225V_1 - 0.0050V_2 + 0.196V_1 = I_2$$

$$I_2 = 0.1735V_1 + 0.0027V_2$$

$$Y_{21} = 0.1735 \quad Y_{22} = 0.0027$$

$$Y \begin{bmatrix} 0.0115 & -0.0026 \\ 0.1735 & 0.0027 \end{bmatrix}$$

$$\Delta Y = 0.73$$

$$3.105 \times 10^{-5} + 4.511 \times 10^{-4}$$

$$(0.3105 + 4.511) \times 10^{-4}$$

$$4.82 \times 10^{-4}$$

$$0.482 \times 10^{-3}$$

rearranging eq

$$V_1 = \frac{I_1}{0.0115} + \frac{0.0026V_2}{0.0115}$$

$$= 8.69I_1 + 0.226V_2$$

$$= 8.69I_1 + 0.226 \left(\frac{I_2}{0.0027} - \frac{0.1735V_1}{0.0027} \right)$$

$$V_1 = 8.69I_1 + 8.37I_2 - 1.45V_1$$

$$V_1 = 3.54I_1 + 3.29I_2$$

$$V_2 = \frac{I_2}{0.0027} - \frac{0.1735 V_1}{0.0027}$$

$$V_2 = 370.37 I_2 - 64.25 V_1$$

$$V_2 = 370.37 I_2 - 64.25 (3.54 I_1 + 3.29 I_2)$$



$$V_2 = 370.37 I_2 - 227.445 I_1 - 211.38 I_2$$

$$V_2 =$$

$$Z_{11} = \frac{V_{22}}{\Delta y} = \frac{0.7}{0.73m} - \frac{0.0026}{0.0073} = \frac{0.002}{0.0073} = 2.7$$

1a. Determine max. power that could be dissipated in R_L


store
67

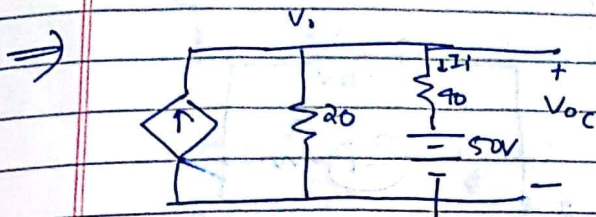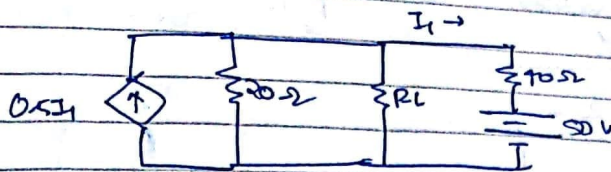

$$-0.5I_1 + \frac{V_{oc}}{20} + \frac{V_{oc} - 50}{40} = 0$$

$$-0.5 \left(\frac{V_{oc} - 50}{40} \right) + \frac{V_{oc}}{20} + \frac{V_{oc} - 50}{40} = 0$$

$$\boxed{V_{oc} = 10V}$$

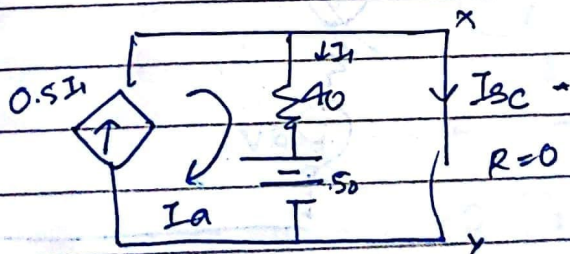


$$I_a = 0.5I_1 = 0.5(I_a - I_b)$$

$$= 40(I_b - I_a) = 50$$

$$I_a =$$

$$I_b = 0.625A = I_{sc}$$





R_L

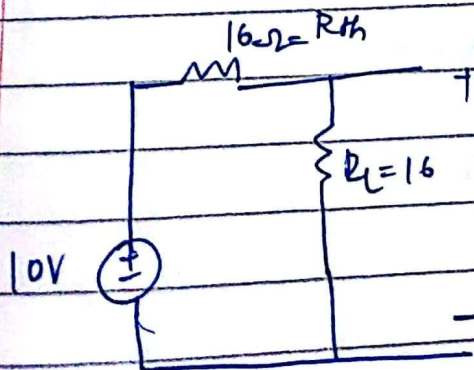

$$R_{th} = \frac{10}{0.625} = 16\Omega = R_L$$


$$P_{max} = \frac{5^2}{16} = 1.5625$$

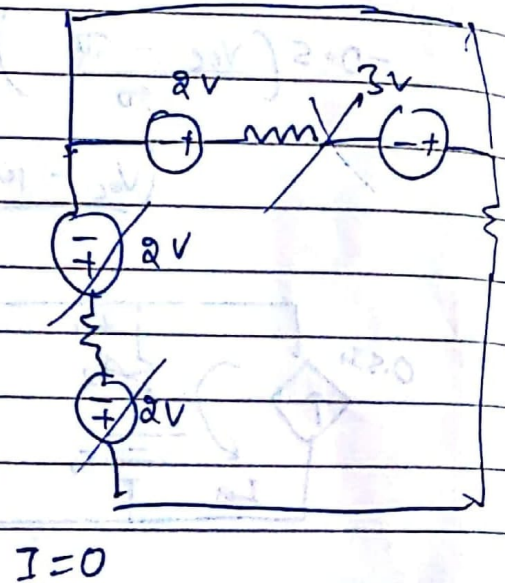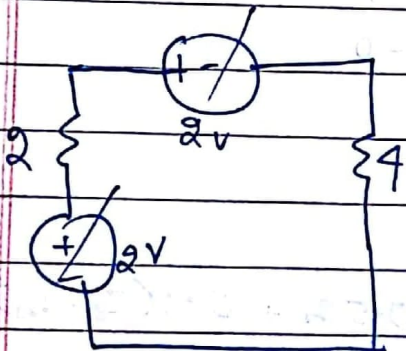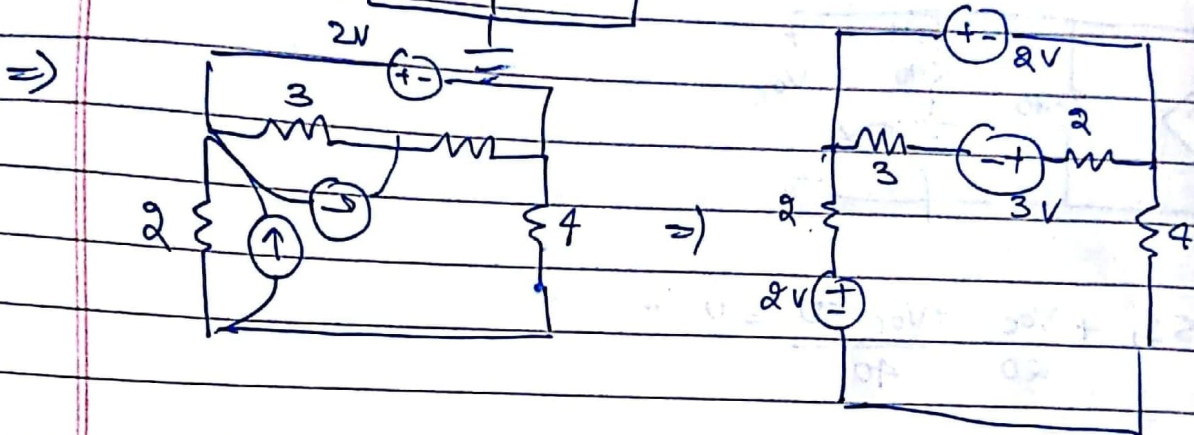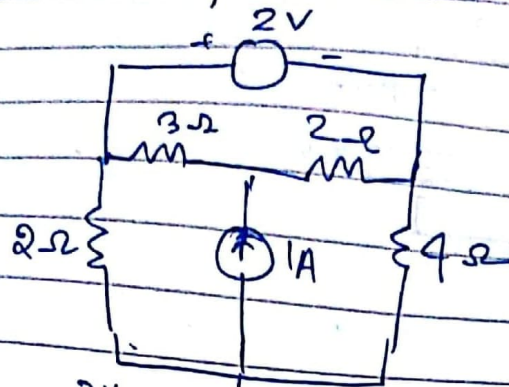1b) Find the current through 4Ω using source transformation technique



8

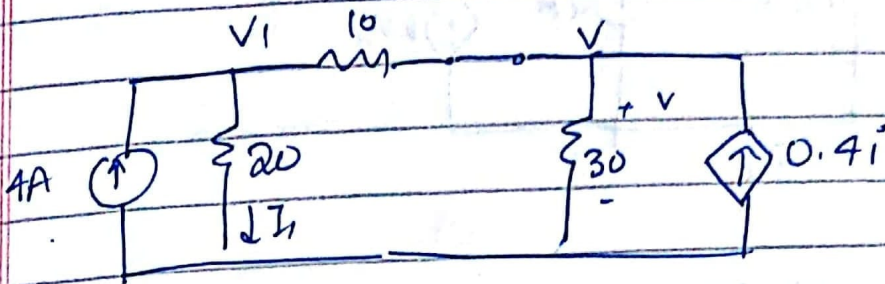1c) Find the voltage V using superposition theorem for a network shown below.




$$-4 + \frac{V_1}{20} + \frac{V_1 - V}{10} = 0$$

$$\frac{V}{30} - 0.4i_1 + \frac{V - V_1}{10} = 0$$

where $i_1 = \frac{V_1}{20}$

$V = 60 \text{ volts}$

Consider 60V

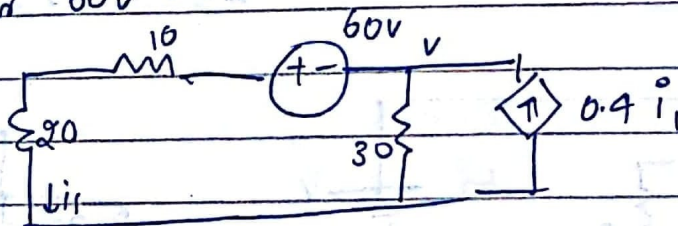


$$\frac{V+60}{30} + \frac{V}{30} - 0.4i_1 = 0 \quad \text{--- (i)}$$

where $i_1 = \frac{V+60}{30}$ Sub in (i) $\frac{V+60}{30} + \frac{V}{30} - 0.4 \left(\frac{V+60}{30} \right) = 0$

$V = 60 + 22.5 = 82.5 \text{ V}$

$V = 22.5$

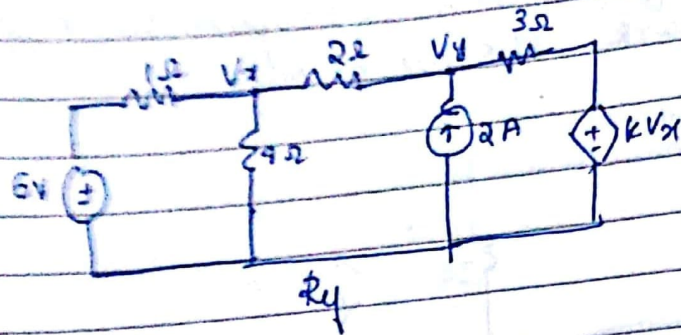Find the value of k that will cause V_y to be zero




Apply KCL at V_x

$$\frac{V_x}{4} + \frac{V_x - V_y}{2} + 2 = 0$$



Apply KCL at V_y

$$\frac{V_y - V_x}{2} - 2 + \frac{V_y}{3} - kV_x = 0$$

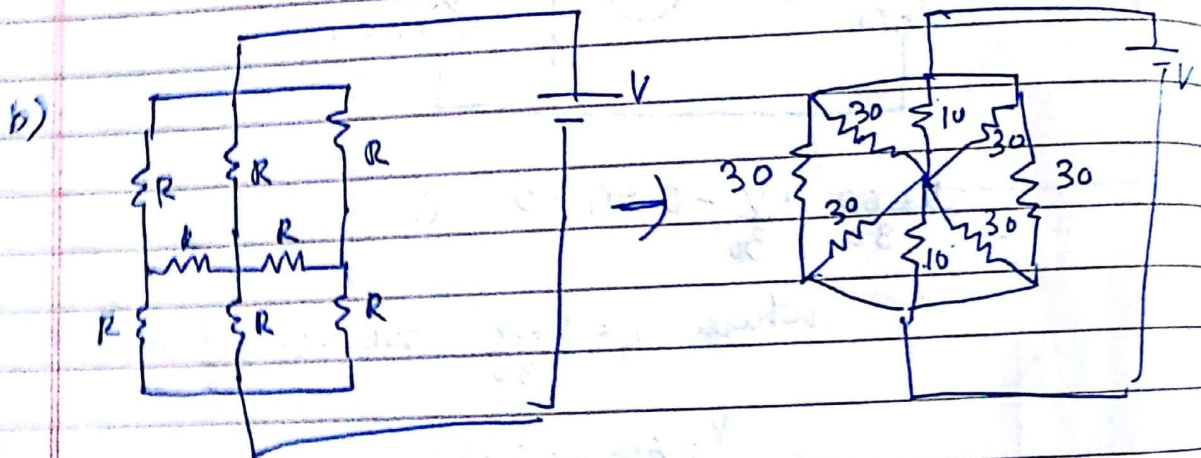
Make $V_y = 0 \Rightarrow$ find k
 $k = -3.25$




store
67

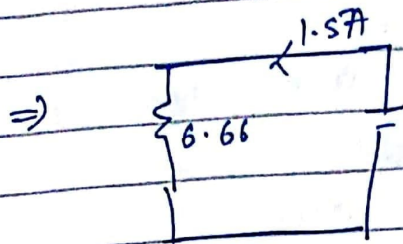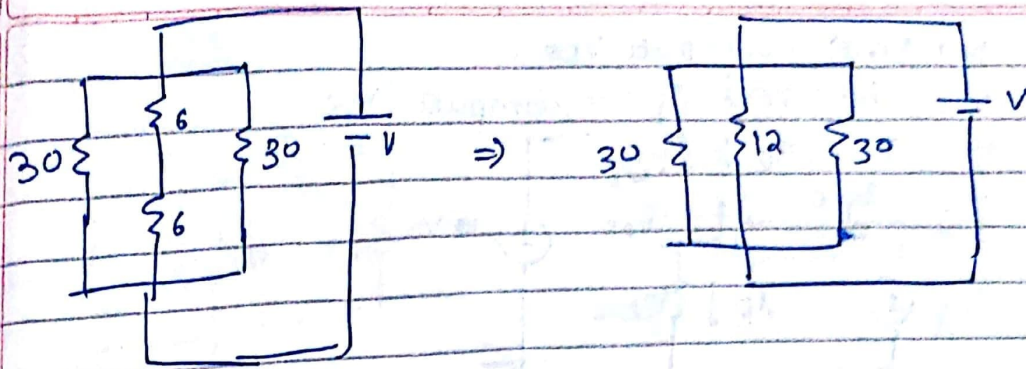

2) c)

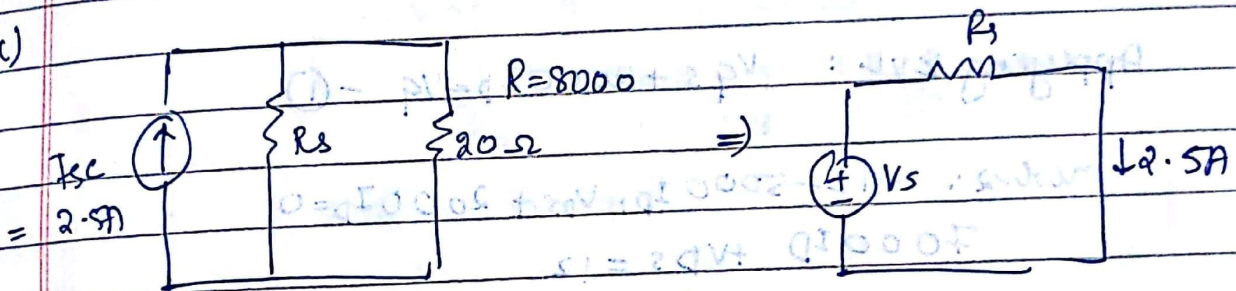
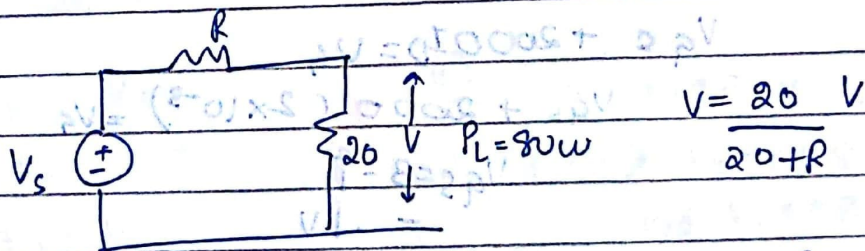
$$2.5 = \frac{V}{R_s} \quad \text{or} \quad V = 2.5 R_s \quad \text{--- (1)}$$




$$V = \frac{20}{20 + R} V_s$$

$$P_L = 80 = \frac{V^2}{20} = \frac{\left(\frac{20 V_s}{20 + R} \right)^2}{20} \quad \text{--- (2)}$$

$$V_{oc} = 200V, \quad P_{max} = 185W$$

$$R_L = 80\Omega$$

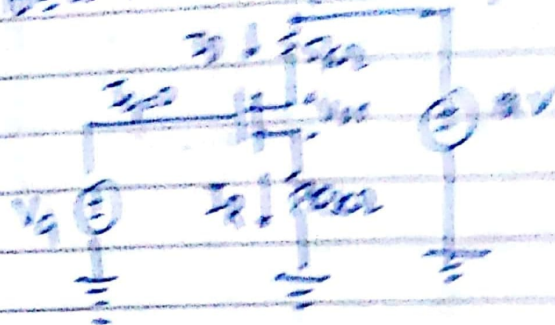- 2) If $I_D = 1.5 \text{ mA}$, compute V_{GS} .
 3) If $I_D = 2 \text{ mA}$ and $V_G = 3 \text{ V}$, compute V_{GS} .



$$I_D = 1.5 \text{ mA}$$

$$V_{GS} = ?$$

$$\text{eg: } I_D = 2 \text{ mA}; V_G = 3 \text{ V}$$

Find V_{GS} .

Applying KVL: $V_{GS} + 2000 I_D = V_G$ — (1)

Mesh 2: $-12 + 5000 I_D + V_{DS} + 2000 I_D = 0$

$$7000 I_D + V_{DS} = 12$$

$$\text{Due to } I_D = 1.5 \text{ mA}$$

$$V_{DS} = 1.5 \text{ V}$$

Sub in eq (1)

$$V_{GS} + 2000 I_D = V_G$$

$$V_{GS} + 2000 (2 \times 10^{-3}) = V_G$$


$$V_{GS} = 3 - 4$$

$$= -1 \text{ V}$$

$$\therefore V_{GS} = -1 \text{ V}$$

$$V_{DS} = 1.5 \text{ V}$$

$$; V_{GS} = -1 \text{ V}$$

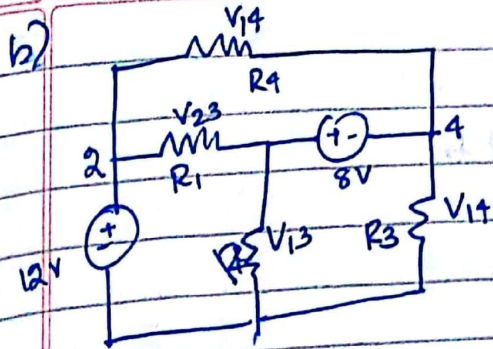

$$V_{23} = V_3 - V_2 \quad \text{--- (1)}$$

$$V_{13} = V_3 - V_1 = V_3 \quad \text{--- (2)}$$

$$V_{14} = V_4 - V_1 = V_4 \quad \text{--- (3)}$$

$$V_{24} = V_4 - V_2 \quad \text{--- (4)}$$

$$V_{34} = V_4 - V_3 = -8V$$

$$V_2 = 12V$$

node 3 & 4 $\rightarrow$ supernode:

$$V_{43} = V_3 - V_4 = 8 \quad \text{--- (5)}$$

$$\frac{V_3 - V_2}{R_1} + \frac{V_3}{R_2} + \frac{V_4}{R_3} + \frac{V_4 - V_2}{R_4} = 0$$

using eq (1), (2), (3), (4)

$$\frac{V_{23}}{R_1} + \frac{V_{13}}{R_2} + \frac{V_{14}}{R_3} + \frac{V_{24}}{R_4} = 0$$

$$\text{eq (5)} \quad V_3 - V_4 = 8$$

$$V_3 - V_4 = 8$$

$$V_{13} - V_{14} = 8$$

$$V_{13} = 8V$$

$$V_3 = 8 \quad \text{--- (6)}$$

$$V_4 = V_{14}$$

$$V_3 = V_{13}$$

$$V_{14} = 0V$$

$$\bullet \quad V_{23} = V_3 - V_2$$

$$V_{23} = 8 - 12 = -4V$$

$$\bullet \quad V_{24} = V_4 - V_2$$

$$= 0 - (+12) = -12$$

ii) when $V_{14} = 6V$

$$\text{eq (5)} \Rightarrow V_3 - V_4 = 8$$

$$V_{13} - V_{14} = 8$$

$$V_{13} = 8 + 6$$

$$V_{13} = 14 = V_3$$

$$V_{23} = V_3 - V_2$$

$$= 14 - 12$$

$$V_{23} = 2V$$

$$V_{24} = V_4 - V_2$$

$$= 6 - 12$$

$$= -6V$$

iv) when $V_{14} = 6V$


$$\text{eq (5)} \Rightarrow V_3 - V_4 = 8$$

$$V_{13} = 8 - 6 = 2 = V_3$$

$$V_{23} = V_3 - V_2 = 2 - 12 = -10$$

$$V_{24} = V_4 - V_2 = 6 - 12 = -6V$$

c)

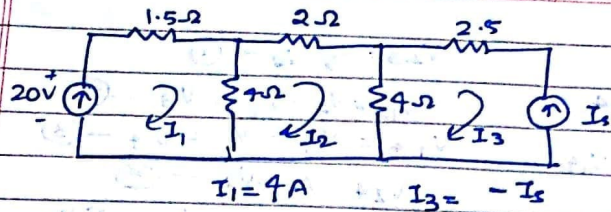

lo

loop 2:

$$-2I_2 - 4(I_2 - I_3) - 14(I_2 - I_1) = 0$$

$$-2I_2 - 4I_2 + 4I_3 - 14I_2 + 14I_1 = 0$$

$$-20I_2 + 4I_3 = -14(4)$$

$$-20I_2 + 4I_3 = -56 \quad \text{--- (1)}$$

loop 1:

$$20 - 1.5I_1 - 14(I_1 - I_2) = 0$$

$$-20 - 1.5(4) - 14(4) + 14I_2 = 0$$

$$14I_2 = -20 + 6 + 56$$

$$I_2 = 3A$$

Sub in eq (1)

$$-20(3) + 4I_3 = -56$$

$$4I_3 = -56 + 60$$

$$4I_3 = 4$$

$$I_3 = 1$$

$$I_3 = -I_2$$

$$I_3 = -1A$$

$$P_{1.5} = (1.5) \times (4)^2 = 24W$$

$$P_{22} = I^2 R$$

$$= 3^2 \times 2 = 18 \text{ W}$$

$$P_{25} = I_3^2 R$$

$$= 1^2 \cdot 2.5 = 2.5 \text{ W}$$

$$P_{14} = (I_1 - I_2)^2 R$$


$$= (4 - 3)^2 \cdot 14 = 14 \text{ W}$$

$$P_4 = (I_2 - I_3)^2 R$$

$$= 4 \times 4 = 16 \text{ W}$$

8. A certain circuit consists 6 elements and 4 nodes numbered 1, 2, 3 and 4. Each circuit element is connected between a different pair of nodes, the voltage V_{12} (positive reference at first named node) is 12V and $V_{34} = -8\text{V}$. Apply suitable KVL find V_{13} , V_{23} and V_{24} , if $V_{14} =$

- i) 0
- ii) 6V
- iii) -6V

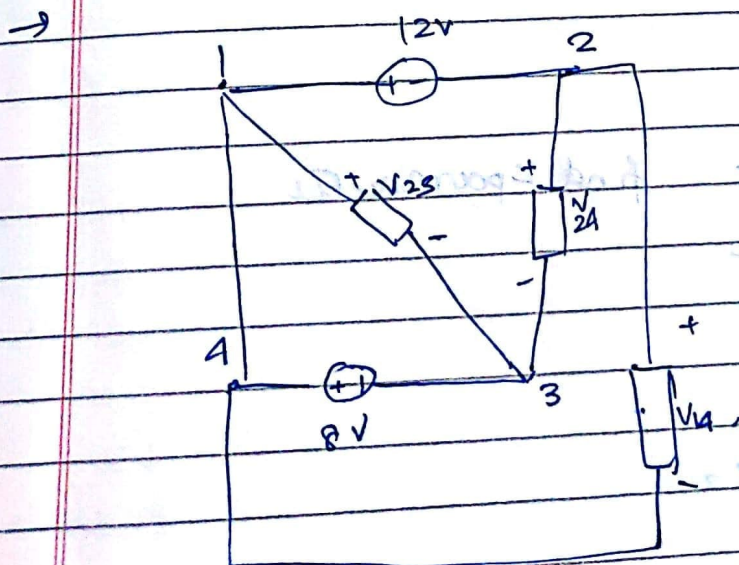

$$-8 + 12 + V_{23} = 0$$

$$V_{23} = -4$$

$$V_{24} =$$

$$12 + V_{24} - V_{23} = 0$$


$$12 + V_{24} + 4 = 0$$

$$V_{24} = -16$$

$$8 - V_{24} + V_{14} = 0$$

$$8 - V_{24} + V_{14} = 0$$

$$8 + 16 + V_{14} = 0$$

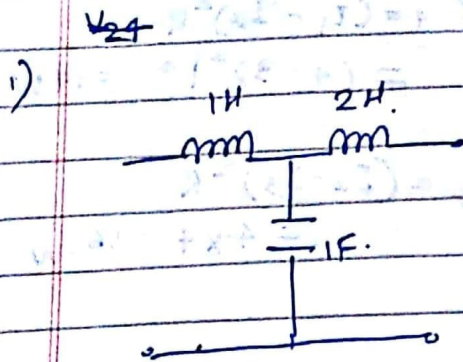

$$X_C = 1/j\omega C$$


$$X_L = j\omega L$$

$$S = j\omega$$

$$V_1 = (1 + \frac{1}{S}) I_1$$

find Z parameter


$$+ \frac{I_2}{S}$$

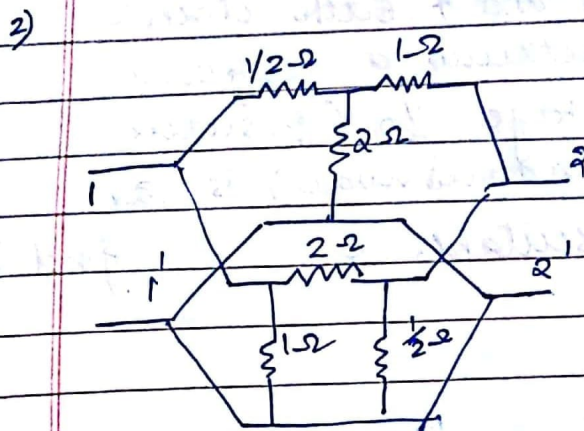


$$V_2 = (\frac{1}{S}) I_1 + (2S + 1) I_2$$

$$Z = \frac{1}{S} + \dots$$

find the y parameter

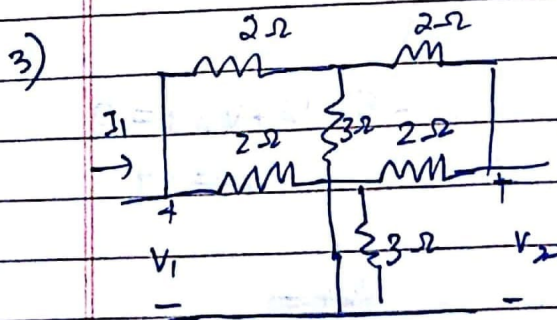


find Z parameter

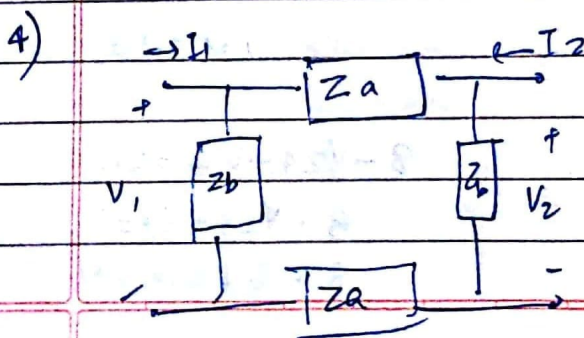

find Z parameter


store
67

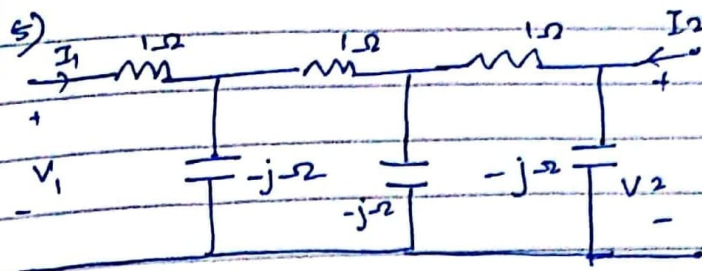

find T parameters.

Network Topology

Graph

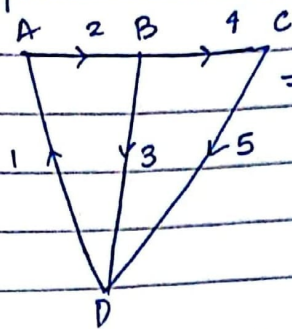


⇒ oriented graph.
(closed)

$$n = 4$$

$$b = 5$$


Tree

(not closed)

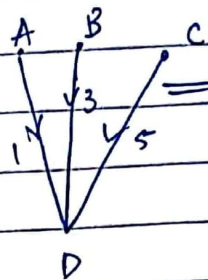

⇒ twigs (1, 3, 5)
(n-1)

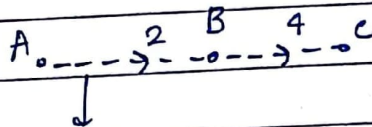co-tree - branches which are not present in the tree



Branches = links

$$l = b - (n - 1)$$

- Graph: The connection of network topology shown by replacing all physical elements by lines is called as graph.
- Oriented graph: A graph with directions represented for each branch is called as oriented graph.


- **Tree:** A tree of a graph is any set of branches that connects every other node directly or indirectly without forming closed loop.
- **Twigs:** The branches of a tree is called as twigs. twig is represented by thick lines
- no of branches in a tree is $n-1$.
- **co-tree - (complementary tree):** The set of branches of the connected graph not included in the tree, is called co-tree
- **links** - the branches of the co-tree are called links and is represented by dotted lines & the no of links is given by $b - (n-1)$.

oriented graph



→








$$n=5$$

$$b=8$$

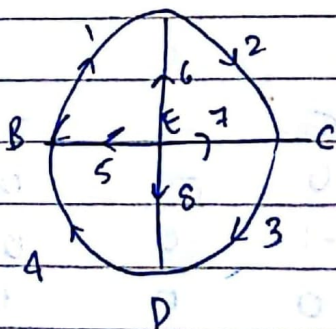

tree = $n-1 = 4$ branches

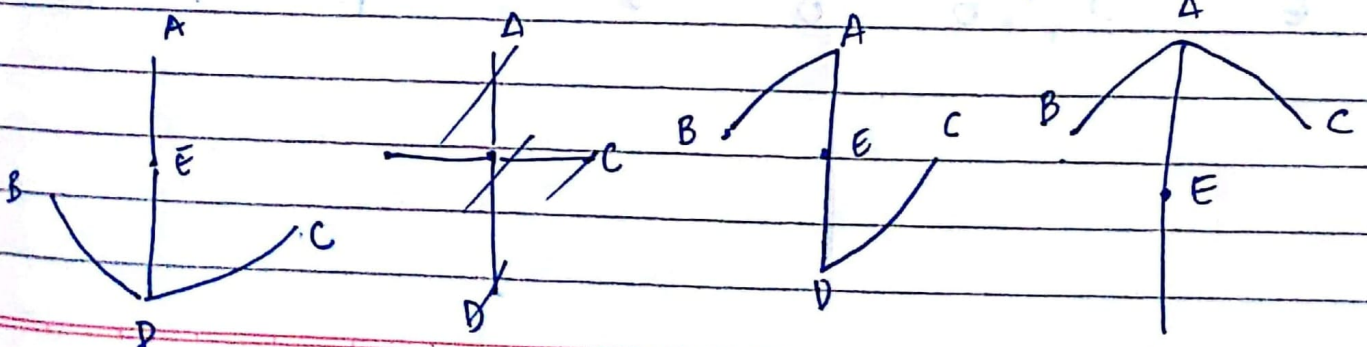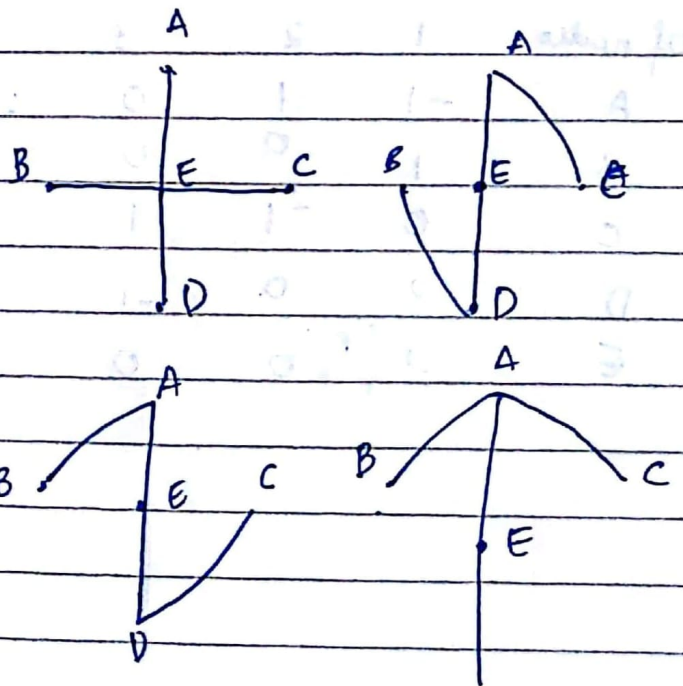

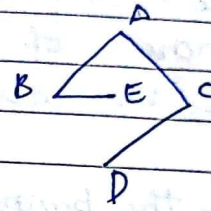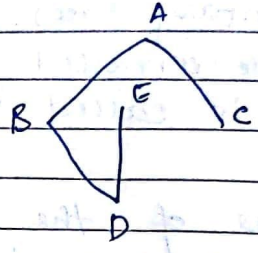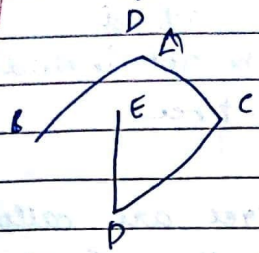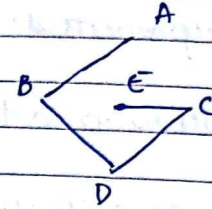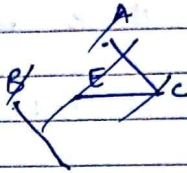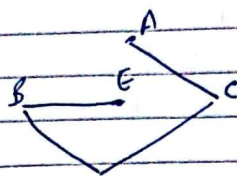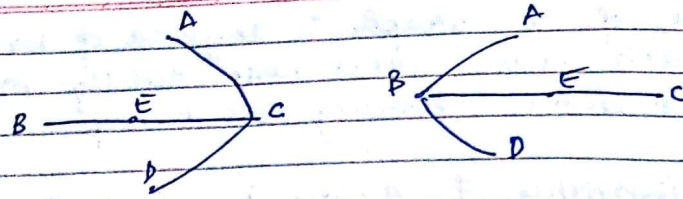

Entry I $\Rightarrow$ -ve
 leaving I $\Rightarrow$ +ve
 not connected $\Rightarrow$ 0

	Branch no							
no of nodes	1	2	3	4	5	6	7	8
A	-1	1	0	0	0	-1	0	0
B	1	0	0	-1	-1	0	0	0
C	0	-1	1	0	0	0	0	0
D	0	0	-1	1	0	0	-1	0
E	0	0	0	0	1	1	1	1

Incidence matrix

It's a mathematical model that represents a given network & its graph with all information available in the network. This matrix shows which branch is connected to which node & its orientation

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 1 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 \end{bmatrix}$$

Adding columns = 0.

$\Rightarrow$ particular node $I_{leaving} = I_{entering}$



deleting one node row $\Rightarrow$ reduced incidence matrix (A_r)

$$[A_r] = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 1 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & -1 \end{bmatrix}$$

Total number of possible trees $[A_r \cdot A_r^T]$

$$= \det \det [A_r \cdot A_r^T]$$

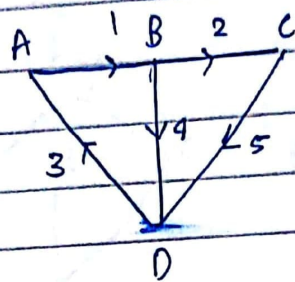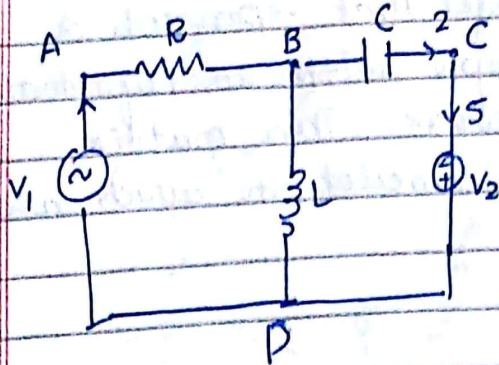Q.1. The incidence matrix for the network is given draw the corresponding graph.
 nodes = 4
 branches = 5



$$\Rightarrow IM = A =$$

$$b = n - 1 = 4 - 1 = 3$$

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} A \\ B \\ C \\ D \end{matrix} & \begin{bmatrix} 1 & 0 & -1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \\ 0 & 0 & 1 & -1 & -1 \end{bmatrix} \end{matrix}$$

$$A_R = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} A \\ B \\ C \end{matrix} & \begin{bmatrix} 1 & 0 & -1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

$$A \cdot A_R (A_R)^T = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \Rightarrow A_R \cdot (A_R)^T =$$


store
67

$$\begin{bmatrix} 1+1 & -1 & 0 \\ -1 & 1+1+1 & -1 \\ 0 & -1 & 1+1 \end{bmatrix} = \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix}$$

$$\text{Det} [A_R \cdot A_R^T] = 2(6-1) + 1(-2-0) + 0$$

$$= 5 \times 2 + 1(-2) = 10 - 2 = 8$$




possible trees

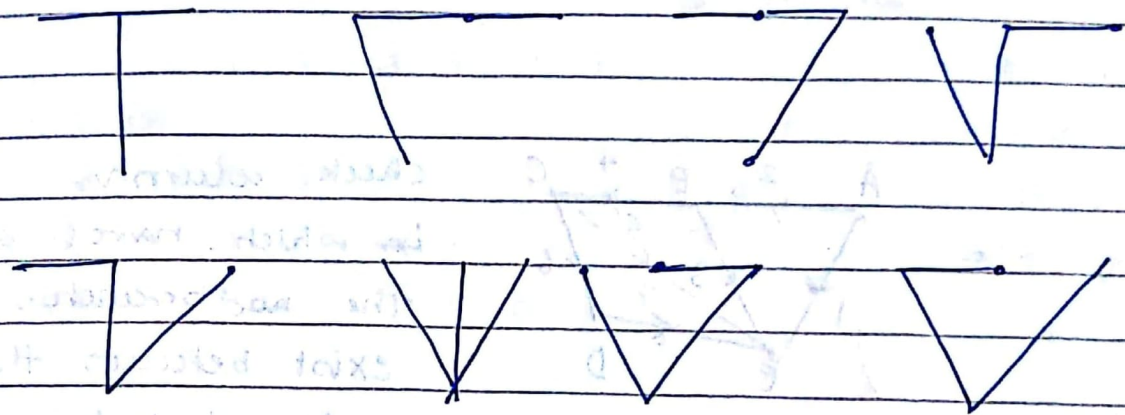

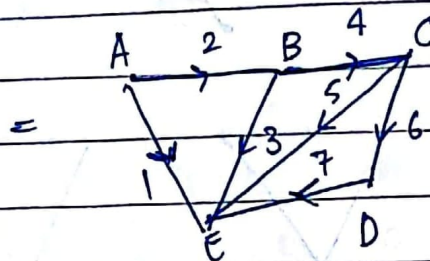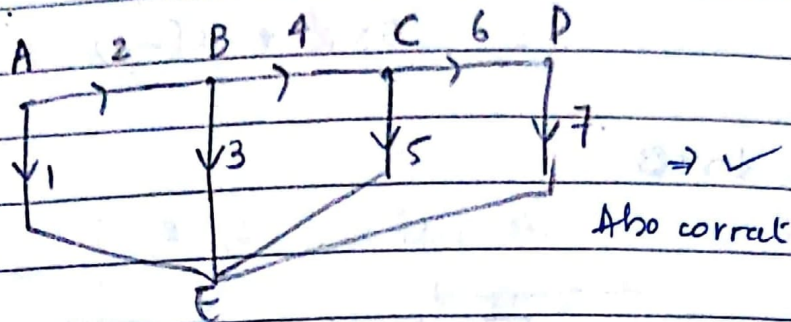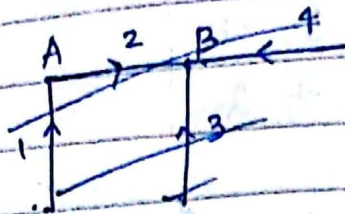Q2) the incidence matrix for the net ---


$$I_m = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \leftarrow \text{Reduced}$$

$$I_m = A \begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ \begin{matrix} A \\ B \\ C \\ D \\ E \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix} \end{matrix}$$




check columns
in which have (1 or -1)
the nodes branches
exist between those
nodes which have 1 & -1
the put direction

Q. Draw the incidence matrix

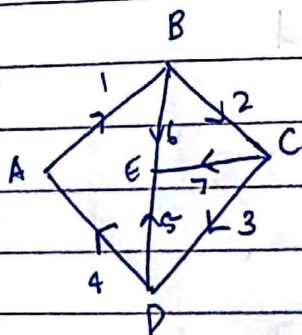


	1	2	3	4	5	6	7
A	1	0	0	-1	0	0	0
B	-1	1	0	0	0	1	0
C	0	-1	1	0	0	0	1
D	0	0	-1	1	1	0	0
E	0	0	0	0	-1	-1	-1


8. Draw the graph

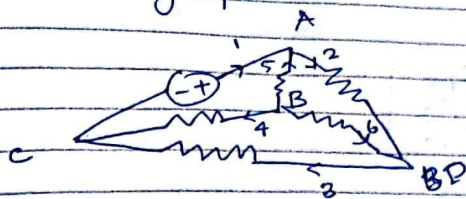

o. graph

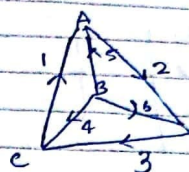

+ tree

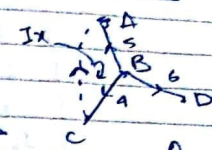


twigs

(5, 4, 6)

$n-1$

= 3 branches

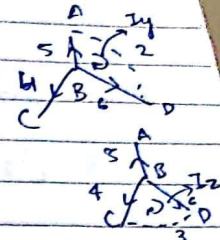

loop currents

$$\begin{matrix} I_x \\ I_y \\ I_z \end{matrix} \begin{bmatrix} 1 & 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{bmatrix} \Rightarrow B$$

$$V_1 + V_4 - V_5 = 0$$

$$V_2 + V_5 - V_6 = 0$$

$$I_1 = I_x$$

$$I_4 = I_x - I_z$$

$$I_2 = I_y$$

$$I_5 = I_y - I_x$$

$$I_3 = I_z$$

$$I_6 = I_z - I_y$$

see columns

KVL

I_x

$$V_1 + V_4 - V_5$$

I_y

$$V_2 + V_5 - V_6$$

I_z

$$V_3 - V_4 + V_6$$

[Tie-set matrix]


$$BV_B = 0$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix}$$

see rows

$$I_B = B^T I_L$$
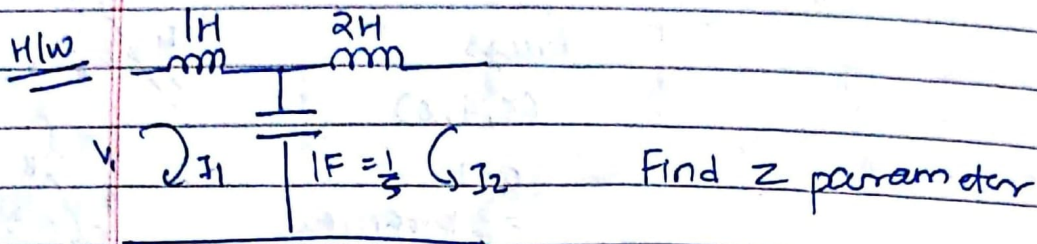
$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_k \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \\ \quad \\ \quad \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$



$$X_C = \frac{1}{j\omega C} \quad X_L = j\omega L$$

$$V_1 = \left(1 + \frac{1}{s}\right) I_1 + \frac{1}{s} I_2$$

$$= \left(1 + \frac{1}{j\omega}\right) I_1 + \frac{1}{j\omega} I_2$$


$$V_1 = \left(\frac{1+j\omega}{j\omega}\right) I_1 + \left(\frac{1}{j\omega}\right) I_2$$

$$V_2 = \left(\frac{1}{2} + \frac{1}{s}\right) I_1 + \left(2s + \frac{1}{s}\right) I_2$$

$$= \left(\frac{1}{2} + \frac{1}{j\omega}\right) I_1 + \left(2j\omega + \frac{1}{j\omega}\right) I_2$$



$$= \left(\frac{2+j\omega}{2j\omega}\right) I_1 + \left(\frac{2j\omega^2+1}{j\omega}\right) I_2$$
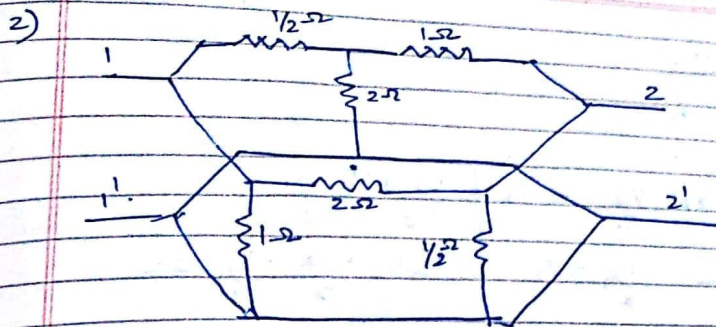
$$Z = \begin{bmatrix} 1+j\omega/j\omega & 1/j\omega \\ 2+j\omega/2j\omega & 2(j\omega)^2+1/j\omega \end{bmatrix}$$



Find Y parameter.

n/w a

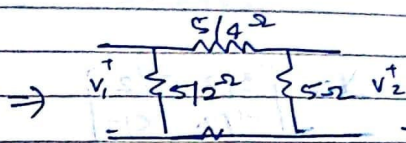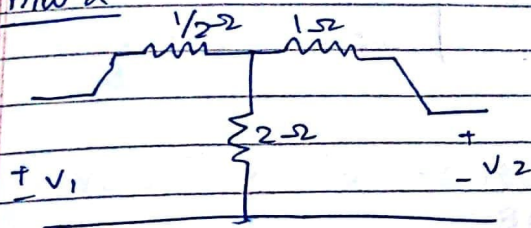

$Y \rightarrow \Delta$

$$\frac{1/2 + 2 + 1}{2} = \frac{5/2 \times 1/2}{1}$$

$$= 5/4$$

$$\frac{5/2}{1/2} = \frac{5}{1} \times \frac{2}{1}$$

Applying nodal

$$\frac{V_1}{5/2} + \frac{V_1 - V_2}{5/4} = I_1$$

$$I_1 = \frac{2V_1}{5} + \frac{4V_1 - 4V_2}{5}$$


$$I_1 = \frac{6V_1}{5} - \frac{4V_2}{5} \quad \text{--- (1)}$$

$$\frac{V_2}{5} + \frac{V_2 - V_1}{5/4} = I_2$$

$$\frac{V_2}{5} + \frac{4V_2 - 4V_1}{5} = I_2$$

$$I_2 = -\frac{4V_1}{5} + \frac{5V_2}{5}$$
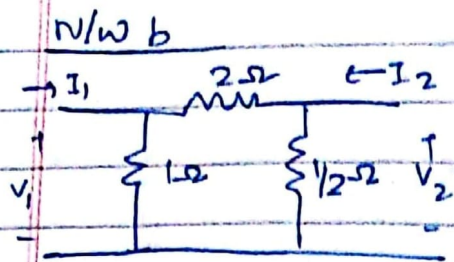
$$Y_0 = \begin{bmatrix} 6/5 & -4/5 \\ -4/5 & 1 \end{bmatrix}$$



$$\text{nodal} \quad \frac{V_1}{1} + \frac{V_1 - V_2}{2} = I_1 \quad \left| \quad \frac{V_2 + V_2 - V_1}{1/2} = I_2\right.$$


$$V_1 + \frac{V_1}{2} - \frac{V_2}{2} = I_1 \quad \left| \quad \frac{2V_2 + V_2 - V_1}{2} = I_2\right.$$



$$\Rightarrow I_1 = \frac{3}{2}V_1 - \frac{V_2}{2} \quad \left| \quad I_2 = \frac{-V_1}{2} + \frac{5V_2}{2}\right.$$

$$Y_b = \begin{bmatrix} 3/2 & -1/2 \\ -1/2 & 5/2 \end{bmatrix}$$

$$Y = \begin{bmatrix} 6/5 & -4/5 \\ -4/5 & 1 \end{bmatrix} + \begin{bmatrix} 3/2 & -1/2 \\ -1/2 & 5/2 \end{bmatrix}$$
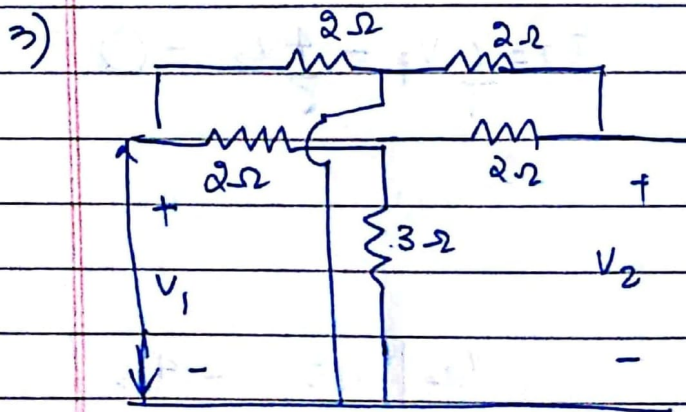
$$Y = \begin{bmatrix} 2.7 & -1.3 \\ -1.3 & 3.5 \end{bmatrix} \Omega$$



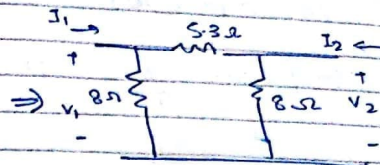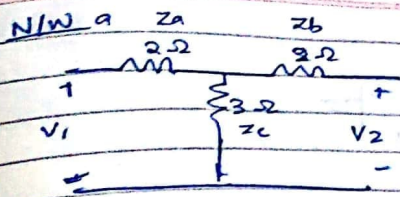

nodal

$$\frac{V_1}{8} + \frac{V_1 - V_2}{5.33} = I_1$$

$$I_1 = 0.3126V_1 - 0.1876V_2$$

$$I_2 = -0.1876V_2 + 0.3126V_2$$

$$\frac{V_2}{8} + \frac{V_2 - V_1}{5.33} = I_2$$



$$Y_a = \begin{bmatrix} 0.3126 & -0.1876 \\ -0.1876 & 0.3126 \end{bmatrix} \Omega \quad Z_a = \begin{bmatrix} 5 & 3 \\ 3 & 5 \end{bmatrix} \Omega$$

$$Z_{11} = Z_a + Z_c = 5 \Omega$$

$$Z_{12} = Z_c = 3 \Omega$$

$$Z_{21} = Z_c = 3 \Omega$$

$$Z_{22} = Z_b + Z_c = 5 \Omega$$

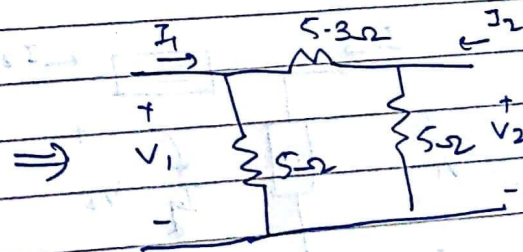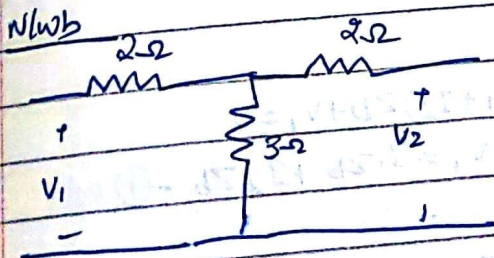

$$I_1 = 0.3126V_1 - 0.1876V_2$$

$$I_2 = -0.1876V_1 + 0.3126V_2$$


$$Y_b = \begin{bmatrix} 0.3126 & -0.1876 \\ -0.1876 & 0.3126 \end{bmatrix} \Omega$$

$$Y = [Y_a] + [Y_b]$$

$$Y = \begin{bmatrix} 0.6252 & -0.3752 \\ -0.3752 & 0.6252 \end{bmatrix} \text{ S}$$


$$Z = [Z_a] + [Z_b]$$
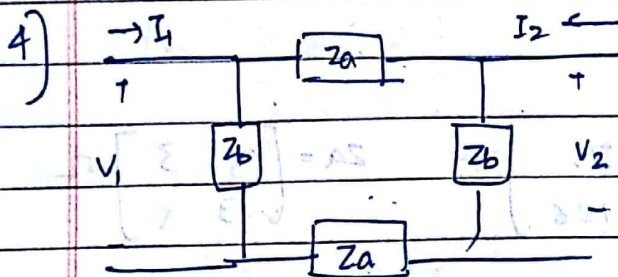
$$Z = \begin{bmatrix} 10 & 6 \\ 6 & 10 \end{bmatrix} \Omega$$



Find Z parameter

n/w a

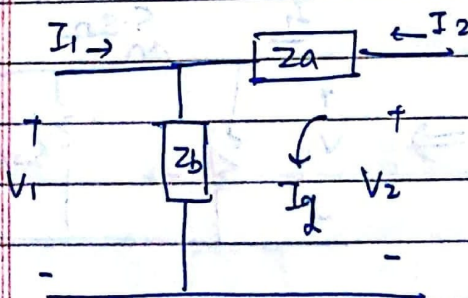

$$-(I_1 + I_2)Z_b + V_1 = 0$$

$$V_1 = I_1 Z_b + I_2 Z_b \quad \text{--- (1)}$$


$$[-I_1 Z_a - (I_2 + I_1)Z_b + V_2 = 0$$

$$V_2 = I_2 Z_a + I_2 Z_b + I_1 Z_b$$

$$V_2 = I_1 Z_b + (Z_a + Z_b)I_2 \quad \text{--- (2)}$$

$$Z_a = \begin{bmatrix} Z_b & Z_b \\ Z_b & Z_a + Z_b \end{bmatrix} \Omega$$

n/w b

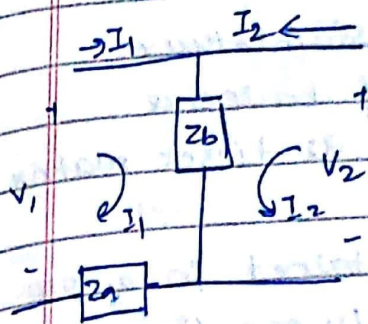

$$-(I_1 + I_2)Z_b - I_1 Z_a + V_1 = 0$$

$$V_1 = I_1 Z_b + I_2 Z_b + I_1 Z_a$$

$$V_1 = (Z_a + Z_b)I_1 + Z_b I_2 \quad \text{--- (1)}$$

$$-(I_1 + I_2)Z_b + V_2 = 0$$

$$V_2 = I_1 Z_b + I_2 Z_b \quad \text{--- (2)}$$

$$Z_b = \begin{bmatrix} Z_a + Z_b & Z_b \\ Z_b & Z_b \end{bmatrix}^{-1}$$

$$Z = [Z_a] + [Z_b]$$

$$Z = \begin{bmatrix} Z_a + Z_b & 2Z_b \\ 2Z_b & Z_a + 2Z_b \end{bmatrix}^{-1}$$

$$\textcircled{5} \text{ n/w a) } = T_a \begin{bmatrix} -(1 - \frac{j\omega}{j\omega}) & -(1 - 2\frac{j\omega}{j\omega}) \\ -1/j\omega & -(1 - j\omega/j\omega) \end{bmatrix}$$

$$\text{n/w b) } T = - \frac{1}{j^2} \begin{bmatrix} -4j^3 + 7j^2 - 6j + 2 & -2j^2 + 2j \\ -2j^3 + 4j^2 - 4j + 2 & -j^2 + 2j \end{bmatrix}$$


Network Topology Continued:

• Tieset matrix


A matrix representing the relationship between no of ~~link~~ link currents and no of branches in the directed graph is known as tieset matrix

- **Link** is a set of branches contained in a loop such that each loop contains only one link and rest are the branches

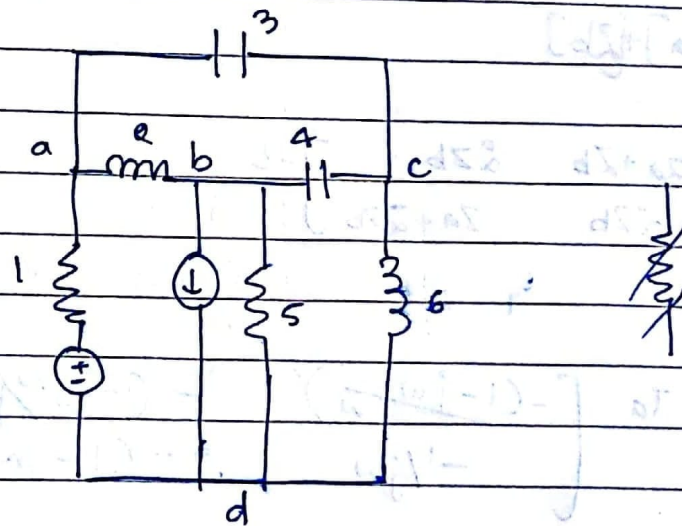Q. Draw the tieset schedule for the given network considering 2, 3, 6 as tree





Q. graph

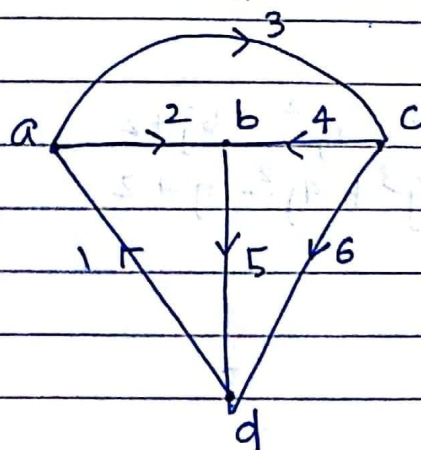

$$\text{nodes} = 4$$

$$\text{twigs} = 4 - 1 = 3 \text{ twigs}$$

$$\Rightarrow 2, 3, 6.$$

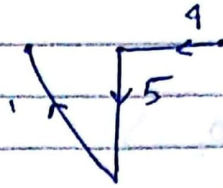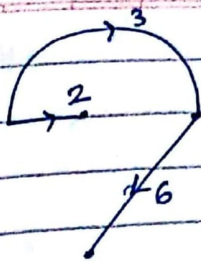

[1, 5, 4]

Tree.

co-tree. (make in dotted lines)

~~Tie set matrix.~~ Tie set matrix



	1	2	3	4	5	6
A	-1	1	1	0	0	0
B	0	-1	0	-1	1	0
C	0	0	-1	1	0	1
D	1	0	0	0	-1	-1

1st case:

add 1 to the tree


Case 2:

add 5 to the tree

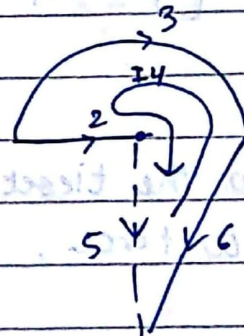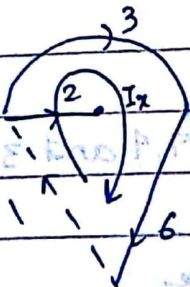

Tie set schedule

Case 3: add 4 to the tree

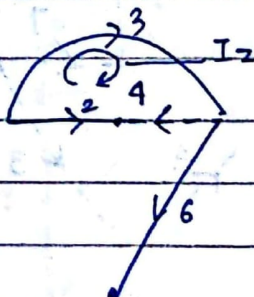

	1	2	3	4	5	6
I_1	1	0	1	0	0	1
I_2	0	1	-1	0	1	-1
I_3	0	-1	1	1	0	0

$$= B \cdot V_B = 0 \begin{bmatrix} 1 & 0 & 1 & 0 & 1 \\ 0 & 1 & -1 & 0 & -1 \\ 0 & -1 & 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = 0$$

KVL equations

$$V_1 + V_3 + V_6 = 0$$

$$V_2 - V_3 + V_5 - V_6 = 0$$

$$-V_2 + V_3 + V_4 = 0$$

$$I_1 = I_x$$

$$I_4 = I_2$$

$$I_2 = I_y - I_2$$

$$I_5 = I_y$$


$$I_3 = I_x - I_y + I_2$$

$$I_6 = I_x - I_y$$


$$I_B = B^T \cdot I_L$$

$$= \begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & -1 \\ 1 & -1 & 1 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} I_x \\ I_y \\ I_z \end{bmatrix}$$

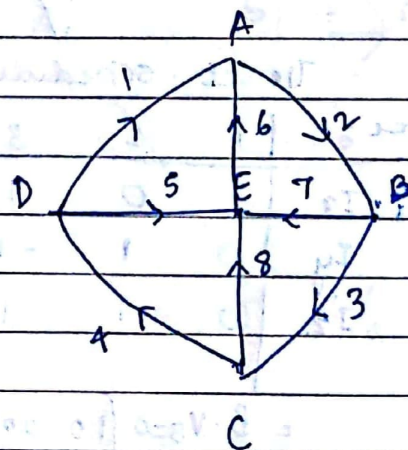Q. Draw the tie-set matrix considering 6, 7, 4 and 3 as co-tree.





co-tree

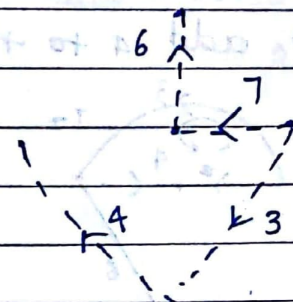


store
67

tree


case1: add 6 to the tree

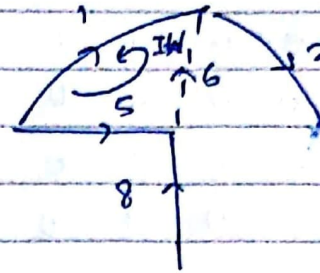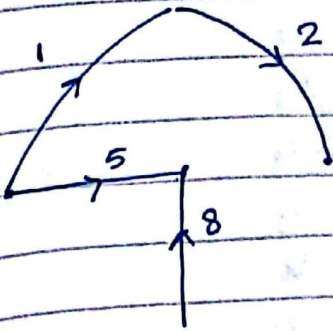

case2: add 7 to the tree

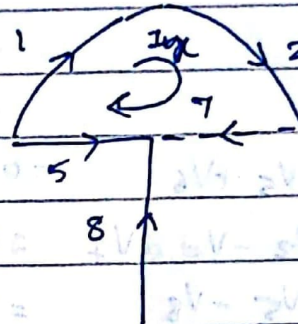


case3: add 4 to the tree

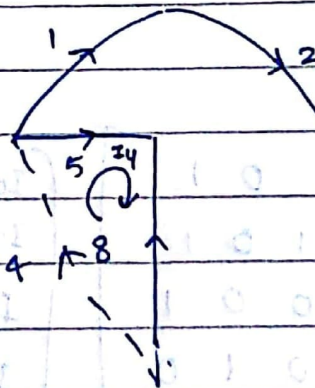

case 4: add 3 to the tree

Zieset schedule.

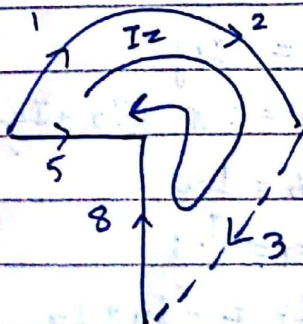

	0	1	2	3	4	5	6	7	8
I_w	-1	0	0	0	0	1	1	0	0
I_x	1	1	0	0	0	-1	0	0	0
I_y	0	0	0	0	1	1	0	0	-1
I_z	1	1	1	0	-1	0	0	0	1

$$B \cdot V_B = 0$$

$$\begin{bmatrix} -1 & 0 & 0 & 0 & 1 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 0 & -1 \\ 1 & 1 & 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \end{bmatrix}$$

$$\Rightarrow \begin{aligned} -V_1 + V_5 + V_6 &= 0 \\ V_1 + V_2 - V_5 + V_7 &= 0 \\ V_4 + V_5 - V_8 &= 0 \\ V_1 + V_2 + V_3 - V_5 + V_8 &= 0 \end{aligned}$$

$$I_B = B^T I_L$$

$$\begin{bmatrix} -1 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 1 & -1 & 1 & -1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} I_{w0} \\ I_x \\ I_y \\ I_z \end{bmatrix} \Rightarrow$$

$$I_1 = -I_{w0} + I_x + I_z$$

$$I_2 = I_x + I_z$$

$$I_3 = I_z$$

$$I_4 = I_y$$

$$I_5 = I_{w0} - I_x + I_y + I_z$$

$$I_6 = I_{w0}$$



$$I_7 = I_y$$

$$I_8 = -I_y + I_z$$



store
67

8.


1, 4, 3, 6, 5 as tree

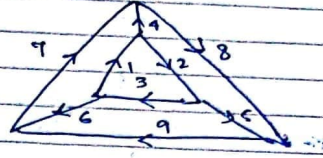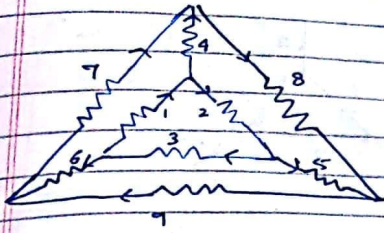

→ tree

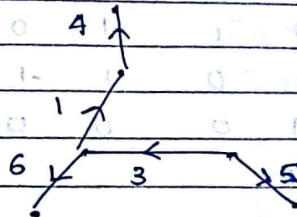
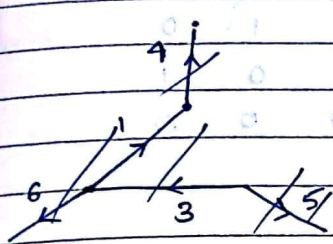


W-tree

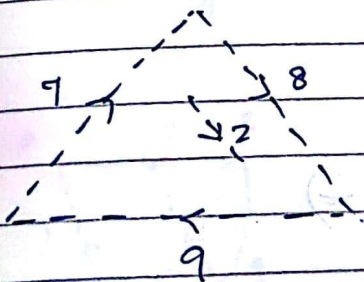

IV	0	0	1	1	0	1	0	0	1	1
IV	0	1	0	0	1	1	1	0	1	1
IV	1	0	0	1	1	0	1	0	0	0
IV	0	0	0	0	0	0	1	1	1	1


case 1 : add 7 to tree case 2: add 8 to tree

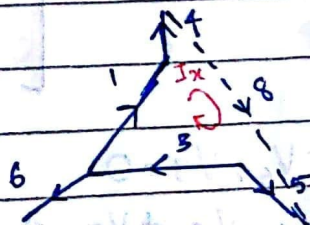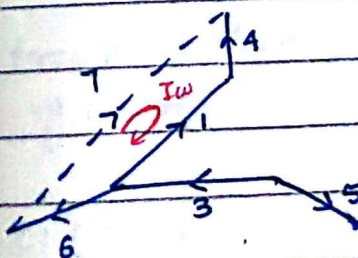

case 3: add 1 to tree



case 4: add 2 to 1 tree

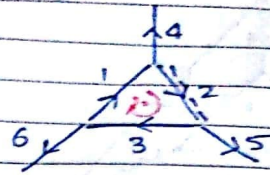

Fessel schubduelle.

	1	2	3	4	5	6	7	8	9
I_w	-1	0	0	-1	0	1	1	0	0
I_x	1	0	1	1	-1	0	0	1	0
I_y	0	0	-1	0	1	-1	0	0	1
I_z	1	1	1	0	0	0	0	0	0

B.VB

$$\begin{bmatrix} -1 & 0 & 0 & -1 & 0 & 1 & 1 & 0 & 0 \\ 1 & 0 & 1 & 1 & -1 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 0 & 1 & -1 & 0 & 0 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \\ V_9 \end{bmatrix} = 0$$

$$\begin{aligned} V_1 - V_4 + V_6 + V_7 &= 0 \\ V_1 + V_3 + V_4 - V_5 + V_8 &= 0 \\ -V_3 + V_5 - V_6 + V_9 &= 0 \\ V_1 + V_2 + V_3 &= 0 \end{aligned}$$

$B^T \cdot I_k$

$$\begin{bmatrix} -1 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 \\ 0 & 1 & -1 & 0 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ 1 & 0 & -1 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

$$\begin{bmatrix} I_w \\ I_x \\ I_y \\ I_z \end{bmatrix}$$

$\Rightarrow$

$$I_1 = -I_w + I_x + I_z$$

$$I_2 = I_z$$

$$I_3 = I_x - I_y + I_z$$

$$I_4 = -I_w + I_x$$

$$I_5 = -I_z + I_y$$

$$I_6 = I_w - I_y$$


$$I_7 = I_w$$

$$I_8 = I_x$$

$$I_9 = I_y$$

* Fundamental cutset:

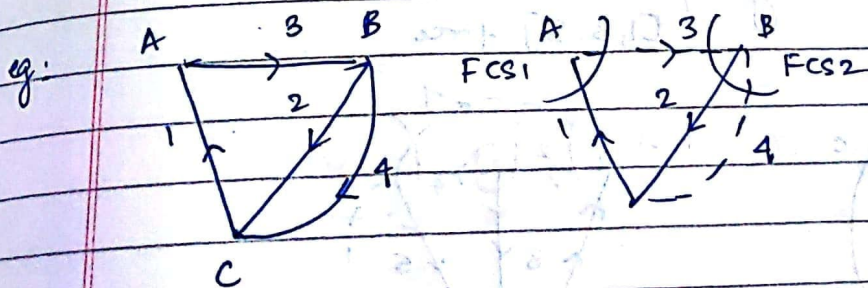- divide the graph in 2 parts.
- cut only twig & any no of links.



tree branch or
vg cutset

	1	2	3	4
e_1 (FCS1)	1	0	-1	0
e_2 (FCS2)	0	1	-1	1

row wise (KVL)

$$I_1 - I_3 = 0$$

$$I_2 - I_3 + I_4 = 0$$

column wise (KVL)

$$V_1 = e_1, V_2 = e_2$$

$$V_3 = -e_1 - e_2$$

$$V_4 = e_2$$

$$Q = \begin{bmatrix} 1 & 0 & -1 & 0 \\ 0 & 1 & -1 & 1 \end{bmatrix}$$

$$QI_B = 0$$

$$\begin{bmatrix} 1 & 0 & -1 & 0 \\ 0 & 1 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = 0$$

$$V_B = Q^T E_T$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ -1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

$$I_1 - I_3 = 0$$



$$I_2 - I_3 + I_4 = 0$$

$$V_1 = e_1 \quad V_3 = -e_1 - e_2$$

$$V_2 = e_2 \quad V_4 = e_2$$

* no of twigs = no of cutsets.

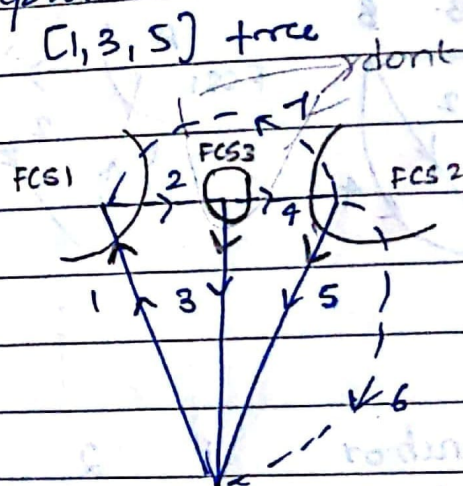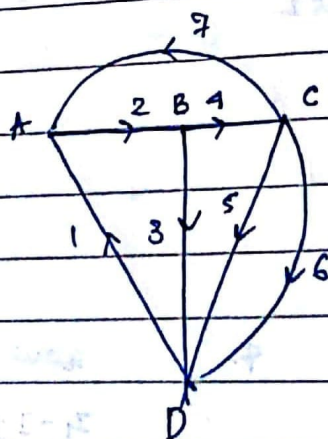Q. Determine the fundamental cutset for the directed graph.



$[1, 3, 5] \rightarrow 3$ cut sets

1 cut set - 1 twig, rest links

• cut twig 1, then twig 3, & twig 5

	1	2	3	4	5	6	7
FCS1(e_1)	1	-1	0	0	0	0	1
FCS2(e_2)	0	0	0	-1	1	1	1
FCS3(e_3)	0	-1	1	1	0	0	0

$$Q = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & -1 & 1 & 1 & 1 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \end{bmatrix}$$


$$QIB = 0$$

$$\begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & -1 & 1 & 1 & 1 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \\ I_7 \end{bmatrix} \Rightarrow \begin{aligned} I_1 - I_2 + I_7 &= 0 \\ -I_4 + I_5 + I_6 + I_7 &= 0 \\ -I_2 + I_3 + I_4 &= 0 \end{aligned}$$

$$V_B = Q^T E_T$$

$$\begin{bmatrix} 1 & 0 & 0 \\ -1 & 0 & -1 \\ 0 & 0 & 1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 0 \\ 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= e_1, & V_3 &= e_3 \\ V_2 &= -e_1 - e_3, & V_4 &= -e_2 + e_3 \\ V_5 &= e_2, & V_6 &= e_2 \\ V_7 &= e_1 + e_2. \end{aligned}$$

Q.

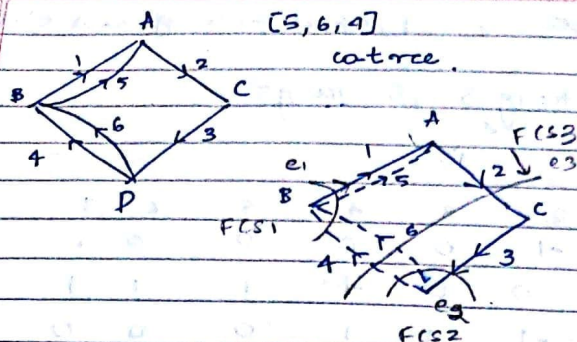

3-twigs - 3 cuts.

	1	2	3	4	5	6
e_1	1	0	0	-1	1	-1
e_2	0	0	1	-1	0	-1
e_3	0	1	0	-1	0	-1

$$Q = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 1 & -1 & 0 & -1 \\ 0 & 1 & 0 & -1 & 0 & -1 \end{bmatrix}$$

$$V_1 = e_1 \quad V_2 = e_2 \quad V_3 = e_2 \quad V_4 = e_1 - e_2 - e_3 = Q^T E^T$$

$$V_5 = e_1 \quad V_6 = -e_1 - e_2 - e_3$$

$$Q I_B = 0$$

$$I_1 - I_4 + I_5 - I_6 = 0$$

$$I_3 - I_4 - I_6 = 0$$


$$I_2 - I_4 - I_6 = 0$$

$$= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ -1 & -1 & -1 \\ 1 & 0 & 0 \\ -1 & -1 & -1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}$$

$\Leftrightarrow$


$$\begin{bmatrix} 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 1 & -1 & 0 & -1 \\ 0 & 1 & 0 & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix}$$

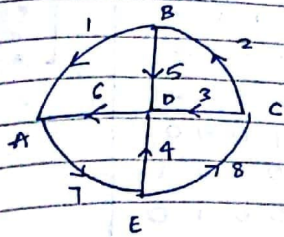Q. write the cutset matrix store 67 $\text{twigs} = \{6, 5, 7, 8\}$



$4 \text{ twigs} = 4 \text{ cuts}$

$\text{links} = (1, 2, 3, 4)$

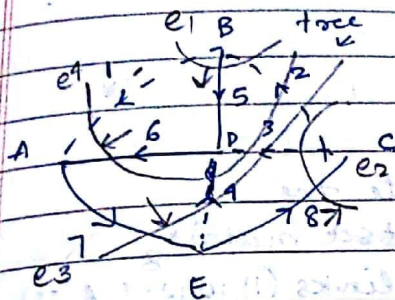

add.

	1	2	3	4	5	6	7	8
e1	1	-1	0	0	1	0	0	0
e2	0	-1	-1	0	0	0	0	1
e3	0	-1	-1	-1	0	0	1	0
e4	1	-1	-1	-1	0	1	0	0

$$Q \begin{bmatrix} 1 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & 0 & 1 \\ 0 & -1 & -1 & -1 & 0 & 0 & 1 & 0 \\ 1 & -1 & -1 & -1 & 0 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \\ I_7 \\ I_8 \end{bmatrix} \Rightarrow \begin{aligned} I_1 - I_2 + I_5 &= 0 \\ -I_2 - I_3 + I_8 &= 0 \\ -I_2 - I_3 - I_4 + I_7 &= 0 \\ I_1 - I_2 - I_3 - I_4 + I_6 &= 0 \end{aligned}$$

$\Phi^T[e] =$

$V_1 = e_1 + e_4$

$V_2 = -e_1 - e_2 - e_3 - e_4$

$V_3 = -e_2 - e_3 - e_4$

$V_4 = -e_3 - e_4$

$V_5 = e_1$

$V_6 = e_1$

$V_7 = e_3$


$V_8 = e_2$

$\Leftarrow$

$$\begin{bmatrix} 1 & 0 & 0 & 1 \\ -1 & -1 & -1 & -1 \\ 0 & -1 & -1 & -1 \\ 0 & 0 & -1 & -1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ e_4 \end{bmatrix}$$

Q.

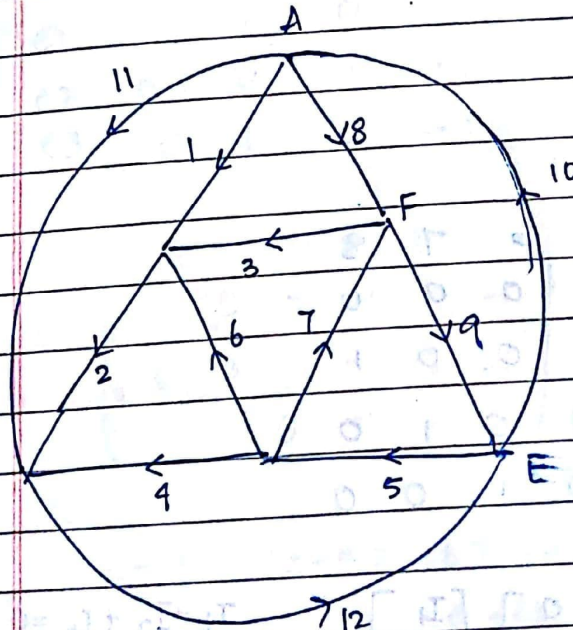

Write the


cutset matrix

links (11, 10, 12, 9, 6, 7)

$\Rightarrow$ twigs (1, 2, 3, 4, 5)

$= \text{utls} = 5$

$\Rightarrow$

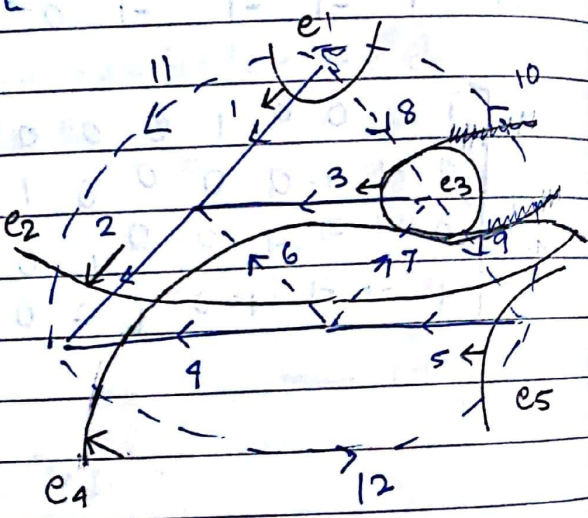

store
67

	1	2	3	4	5	6	7	8	9	10	11	12
e_1	1	0	0	0	0	0	0	1	0	-1	1	0
e_2	0	1	0	0	0	-1	-1	0	1	-1	1	0
e_3	0	0	1	0	0	0	-1	-1	1	0	0	0
e_4	0	0	0	1	0	1	1	0	-1	1	0	-1
e_5	0	0	0	0	1	0	0	0	-1	1	0	-1

Q $\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_{12} \end{bmatrix} \Rightarrow$

$$\begin{aligned} I_1 + I_8 - I_{10} + I_{11} &= 0 \\ I_2 - I_6 - I_7 + I_9 - I_{10} + I_{11} &= 0 \\ I_3 - I_7 - I_8 + I_9 &= 0 \\ I_4 + I_6 + I_7 - I_9 + I_{10} - I_{12} &= 0 \\ I_5 - I_9 + I_{10} - I_{12} &= 0 \end{aligned}$$

Q^T $\begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ e_4 \\ e_5 \end{bmatrix} =$

$$\begin{aligned} V_1 &= e_1 & V_7 &= -e_2 - e_3 + e_4 \\ V_2 &= e_2 & V_8 &= e_1 - e_3 + e_4 \\ V_3 &= e_3 & V_9 &= e_2 + e_3 - e_4 - e_5 \\ V_4 &= e_4 & V_{10} &= -e_1 - e_2 + e_4 + e_5 \\ V_5 &= e_5 & V_{11} &= e_1 + e_2 \\ V_6 &= -e_2 + e_4 & V_{12} &= -e_4 - e_5 \end{aligned}$$

Tie-set

- graph
- tree
- add link one by one
- loop direction based on link direction
- no of loops =
no of links
- Row wise = KVL
voltage terms
 $V_B \cdot B = 0$

CB matrix)

- Column wise = KCL
current terms

Cut-set

- graph
- tree & co-tree
- cut twigs
(1 twig at a time)
- no of cuts = no of twigs
- direction of twig
FCS is based on
direction of twig
- Row wise = current terms
column wise = voltage terms

* In a graph → $n = \text{nodes}$

$b = \text{branch}$

$\text{twig} = (n - 1)$

$\text{links} = b - n + 1$

FOURIER SERIES

$$x(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega_0 t + \sum_{n=1}^{\infty} b_n \sin n\omega_0 t \quad - (1)$$

$$\int_0^T x(t) dt = \int_0^T [a_0 + a_1 \cos \omega_0 t + a_2 \cos 2\omega_0 t + a_3 \cos 3\omega_0 t + \dots + b_1 \sin \omega_0 t + b_2 \sin 2\omega_0 t + b_3 \sin 3\omega_0 t + \dots] dt$$

$$= \int_0^T x(t) dt = \int_0^T a_0 dt$$

these harmonics are sinusoidal and

$$= \int_0^T x(t) dt = a_0 T$$

orthogonal to each other.

$$a_0 = \frac{1}{T} \int_0^T x(t) dt$$


$$a_0 = \frac{1}{T} \int_0^T x(t) dt = a_n = \frac{2}{T} \int_0^T x(t) \cos n\omega_0 t dt \quad b_n = \frac{2}{T} \int_0^T x(t) \sin n\omega_0 t dt$$

Polar form

TIME DOMAIN AND FREQUENCY DOMAIN

- system representation
- system governing equation
- characteristic equation
- order of the system
- poles and zeros
- initial condition
- Transfer function

* Integro-differential equation

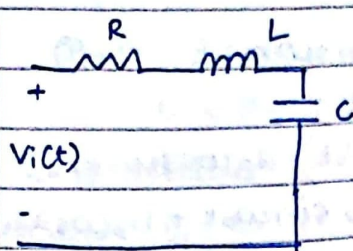

$$V_i(t) = Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i(t) dt$$


this is in time domain.

↳ convert this to Laplace transform

↳ After algebraic manipulation

↳ take inverse Laplace

↳ result [time domain]

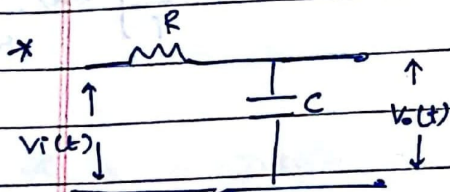

$$\left. \begin{aligned} \text{KVL 1: } V_i(t) &= Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt \\ V_o(t) &= \frac{1}{C} \int_{-\infty}^t i(t) dt \end{aligned} \right\} \text{System governing equation}$$

taking Laplace transform

$$\mathcal{L} \int_0^t F(t) dt = \frac{F(s)}{s} - \frac{f(0^-)}{s}$$

$$V_o(s) = \frac{1}{C} \left[\frac{I(s)}{s} - \frac{q(0^-)}{s} \right] \text{ capacitor } \Rightarrow \infty$$

↗ initial charge on

$$V_L = L \frac{di}{dt}$$

$$V_L(s) = L [sI(s) - I(0)]$$

Take Laplace transform

$$V_i(s) = RI(s) + \frac{1}{Cs} [I(s) - q(0)]$$

$$V_i(s) = RI(s) + \frac{I(s)}{Cs}$$

$$V_o(s) = \frac{I(s)}{Cs}$$

$$\text{Transfer function} = H(s) = \frac{V_o(s)}{V_i(s)}$$

$$= \frac{I(s)}{Cs}$$

$$= \frac{I(s)}{I(s) + RI(s) \times Cs}$$

$$\frac{I(s)}{Cs} \left[\frac{RI(s) \times Cs + 1}{I(s)} \right]$$

$$\Rightarrow \frac{I(s)}{Cs} \Rightarrow \frac{Cs}{RCs + 1} \Rightarrow \frac{1}{RCs + 1}$$

$$\frac{(R+1)I(s)}{Cs}$$

General form

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{Q(s)}{P(s)} = \frac{\text{zero factors}}{\text{pole factors}} = \frac{(1+T_1s)(1+T_2s)}{(1+T_3s)(1+T_4s)}$$

$$Q(s)=0 \quad s = -\frac{1}{T_1}, \quad s = -\frac{1}{T_2}$$

$$P(s)=0 \quad s = -\frac{1}{T_3}, \quad s = -\frac{1}{T_4}$$

• 2 critical frequency poles, 4 zeros.

x

$$RCs + 1 = 0$$

↳ characteristic equation

$$s = -\frac{1}{RC} \rightarrow \text{pole}$$

x

$$T \text{ function } H(s) = \frac{1}{RCs + 1}$$


damping factor

$$s = \sigma + j\omega$$


S-plane

x = poles


o = zeros

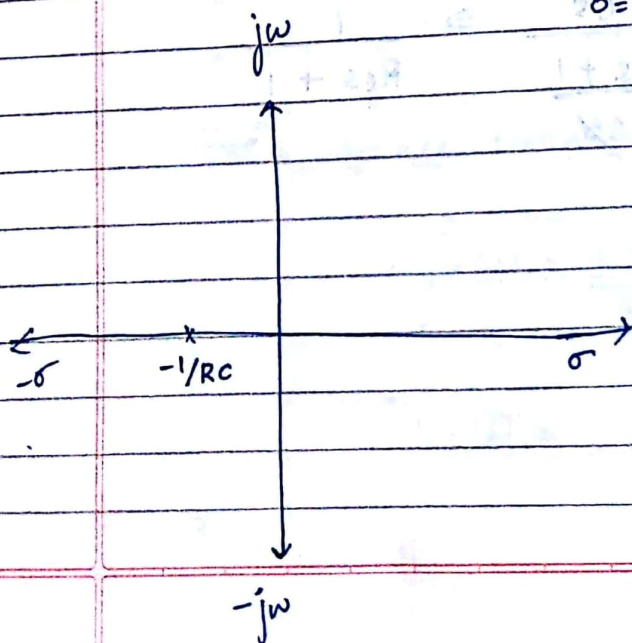


$$\sigma > 1$$

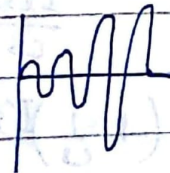

$$\sigma < 1$$

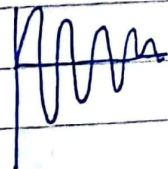

$$\sigma = 1$$

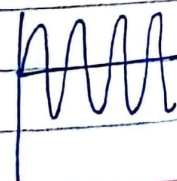


Time Response Analysis.

store 67

→ Transient Response

→ Steady state response.

$$T = \frac{RCs}{RCs + 1}$$

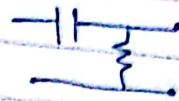

$$\frac{1}{RCs + 1}$$




for any system, transient time should be less

$$\frac{1}{s+1} \quad \frac{1}{s+2}$$

$$s_1 = -1 \quad s_2 = -2$$
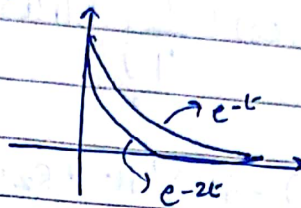
$$\Rightarrow e^{-t} \quad \Rightarrow e^{-2t}$$







• pole that goes away from the origin, it is more stable

Order of the system:

• order of a system = no of storage elements

H/W Derive transfer function for

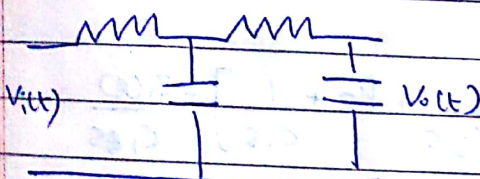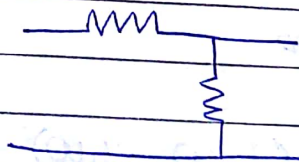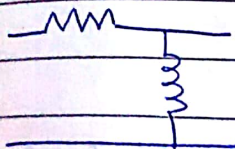

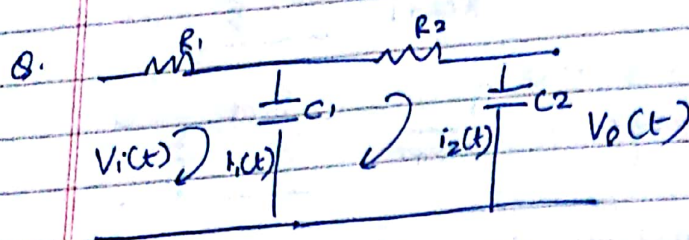

Mesh 1:
$$V_i(t) = R_1 i_1(t) + \frac{1}{C_1} \int_0^t [i_1(t) - i_2(t)] dt \quad \text{--- (1)}$$

Mesh 2:
$$\frac{1}{C_1} \int_0^t [i_2(t) - i_1(t)] dt + R_2 i_2(t) + \frac{1}{C_2} \int_0^t i_2(t) dt = 0$$

$$V_o(t) = \frac{1}{C_2} \int_0^t i_2(t) dt$$

taking ratio $\frac{V_o(s)}{V_i(s)} = \frac{1}{R_1 C_2 s}$

Laplace transform
of eq (1)

$$V_i(s) = R_1 I_1(s) + \frac{1}{C_1} \left[\frac{I_1(s)}{s} - \frac{I_2(s)}{s} \right]$$

$$V_i(s) = R_1 I_1(s) + \frac{I_1(s)}{C_1 s} - \frac{I_2(s)}{C_1 s} \quad \text{--- (1)}$$

Laplace transform
of eq (2)

$$\frac{1}{C_1} \left(\frac{I_2(s)}{s} - \frac{I_1(s)}{s} \right) + R_2 I_2(s) + \frac{1}{C_2} \frac{I_2(s)}{s} = 0$$

$$I_2(s) \left[\frac{1}{C_2 s} + R_2 + \frac{1}{C_1 s} \right] = \frac{I_1(s)}{C_1 s}$$

store
67

$$I_2(s) \left[\frac{C_1}{C_2} + C_1 R_2 + 1 \right] = I_1(s) \quad \text{--- (3)}$$

sub eq (3) in eq (1)

$$V_1(s) = R_1 I_2(s) \left[\frac{C_1}{C_2} + C_1 R_2 + 1 \right] + \frac{1}{C_1 s} \left[\frac{C_1}{C_2} + C_1 R_2 + 1 \right] I_2(s)$$

$$- \frac{I_2(s)}{C_1 s}$$

$$V_1(s) = R_1 I_2(s) + C_1 R_2 R_1$$

$$= \left[R_1 + \frac{R_1 C_1}{C_2} + R_1 R_2 C_1 s + \frac{1}{s C_1} + \frac{1}{s C_2} + R_2 - \frac{1}{C_1 s} \right] I_2(s)$$

$$V_1(s) = \left[\frac{R_1 s C_2 + R_1 C_1 s + R_1 R_2 C_1 C_2 s^2 + 1 + R_2 C_2 s}{s C_2} \right] I_2(s)$$

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$\frac{V_0(s)}{V_1(s)} = \frac{I_2(s)}{C(s)}$$

$$V_0(t) = \frac{1}{C_2} \int^t i_2(t) dt$$




$$V_0(s) = \frac{I_2(s)}{C_2 s} \quad \text{--- (4)}$$

$$\frac{V_0(s)}{V_1(s)} = \frac{I_2(s) \times s C}{C(s) \times [R s C + R C s + R^2 C^2 s^2 + 1 + R^2 C s]} \times \frac{1}{C_2 s} I_2(s)$$


$$V_0(s) =$$

$$V_1(s) \quad R^2 C^2 s^2 + 3 R C s + 1$$

Q. Derive the transfer function.

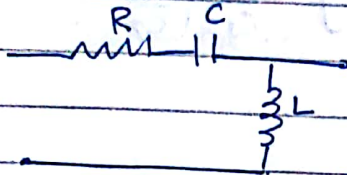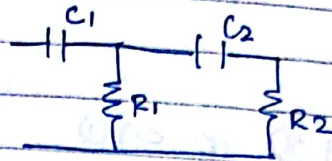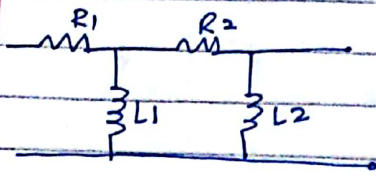

* For the circuit

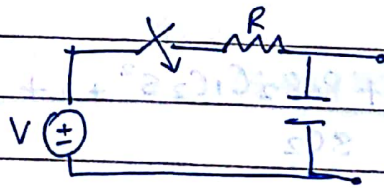

$$V_i(t) = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$$

$V_i(t) \Rightarrow$ step i/p

$$\frac{V}{s} = RI(s) + \frac{I(s)}{Cs}$$

$$\frac{V}{s} = I(s) \left[R + \frac{1}{Cs} \right]$$

$$V = I(s) \left[Rs + \frac{1}{C} \right]$$

$$I(s) = \frac{V}{\left(\frac{s+1}{RC}\right)R}$$


$$I(s) = \frac{V}{R} \times \frac{1}{s + \frac{1}{RC}}$$

$L^{-1}T$

$$i(t) = \frac{V}{R} e^{-t/RC}$$

$RC = \tau = \text{Time constant.}$


$$i(t) = \frac{V}{R} e^{-t/\tau}$$

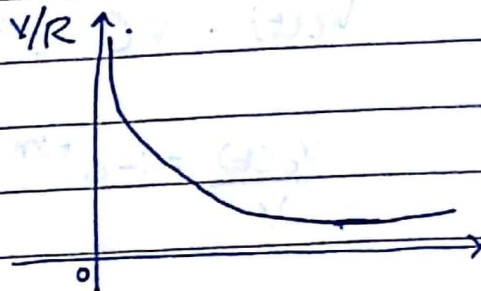

$$i(t) = I_0 e^{-t/\tau}$$

$$\frac{i(t)}{I_0} = e^{-t/\tau}$$

t	$i(t)/I_0$	
$t=0\tau$	$e^0 = 1$	
$t=1\tau$	$e^{-1} = 0.367$	
$t=2\tau$	$e^{-2} = 0.13$	
$t=3\tau$	$e^{-3} = 0.04$	
$t=4\tau$	$e^{-4} = 0.018$	
$t=5\tau$	$e^{-5} = 6.43m = 0.006$	
$t=6\tau$	$e^{-6} = 2.47m = 0.0024$	

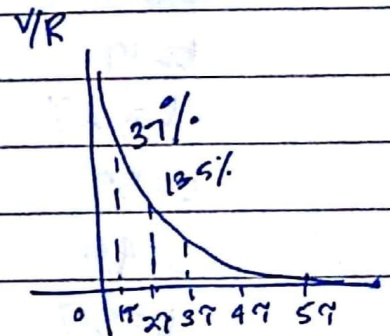

when $t = \tau$

$$i(t) = I_0$$

* I_0 is the max current value

so the current decreases to 37% of its initial value.

* the current reaches to 63% of its final value

$$V_C(t) = V_i(t) - V_R(t)$$

$$V_C(t) = V - I(t) \cdot R$$

$$V_C(t) = V - R \left(\frac{V}{R} e^{-t/\tau} \right)$$

$$V_C(t) = V - V e^{-t/\tau}$$



$$V_C(t) = V (1 - e^{-t/\tau})$$

$$\frac{V_C(t)}{V} = 1 - e^{-t/\tau}$$

t	$V_C(t)/V$
$t = 0\tau$	1
$t = 1\tau$	0.632
$t = 2\tau$	0.864
$t = 3\tau$	0.95
$t = 4\tau$	0.98
$t = 5\tau$	0.99

Done

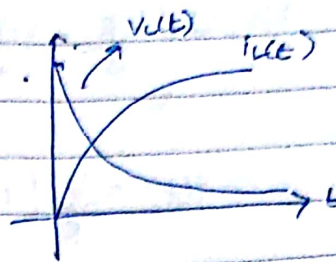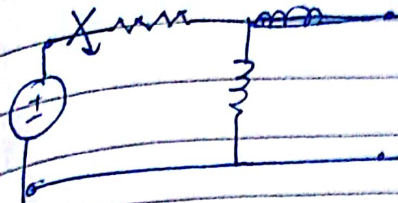* Derive the current equation for RL circuit



$$Ri(t) + L \frac{di}{dt}$$

Laplace transform of eq

$$\frac{V}{s} = RI(s) + LSI(s)$$

$$I(s) = \frac{V/s}{(R + Ls)}$$

$$I(s) = \frac{V/s}{L(s + R/L)}$$

$$I(s) = \frac{V}{L} \times \frac{1}{s(s + R/L)}$$

taking partial fraction.

$$\frac{V/L}{s(s + R/L)} = \frac{A}{s} + \frac{B}{s + R/L}$$

$$\frac{V}{L} = A \left(s + \frac{R}{L} \right) + Bs$$

put $s=0$
put $s=-R/L$

$$A = V/R$$

$$B = -V/R$$

$$\text{LT} \\ I(s) \Rightarrow \left[\frac{V/R}{s} - \frac{V/R}{s + R/L} \right] = \frac{V}{R} \left[1 - e^{-R/L t} \right]$$

$$i(t) = \frac{V}{R} \left[1 - e^{-t/(L/R)} \right]$$

$$i_L(t) = \frac{V}{R} (1 - e^{-t/\tau})$$

$$V_L(t) = -V e^{-t/\tau}$$

$$\begin{aligned} * \quad V_C(t) \\ \text{or} \quad i_L(t) &= [\text{final value}] + [\text{initial value} - \text{final value}] e^{-t/\tau} \end{aligned}$$






$$\begin{aligned} * \quad V_L(t) \\ \text{or} \quad i_C(t) &= [\text{final value}] + [\text{initial value} - \text{final value}] (1 - e^{-t/\tau}) \end{aligned}$$

$$V_C(t) = V(1 - e^{-t/\tau})$$

elements

$t=0$ initial
condition

$t=\infty/0^-$ final
condition.

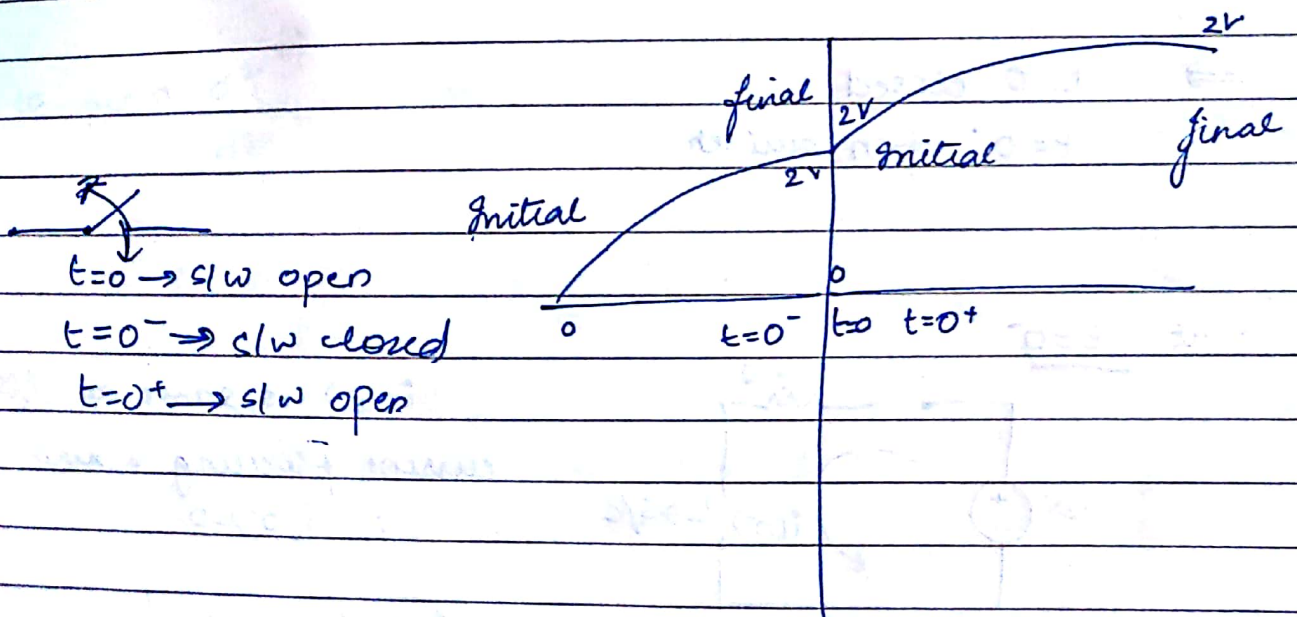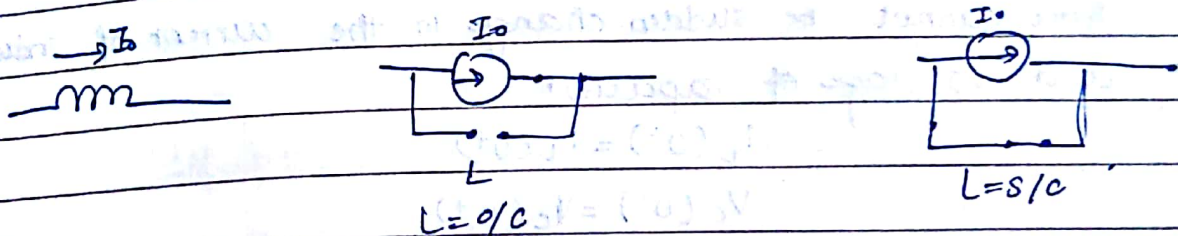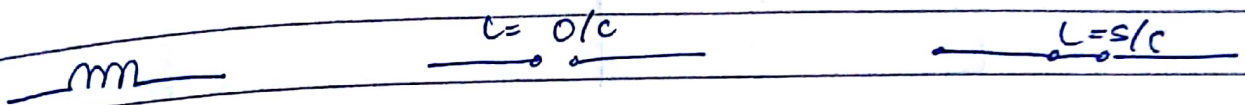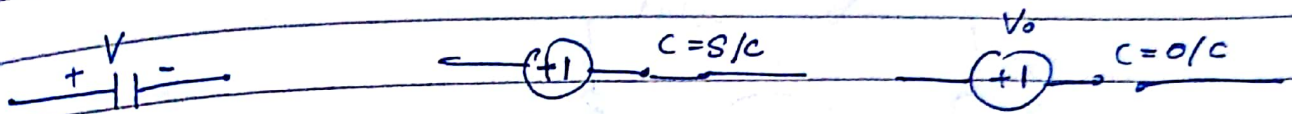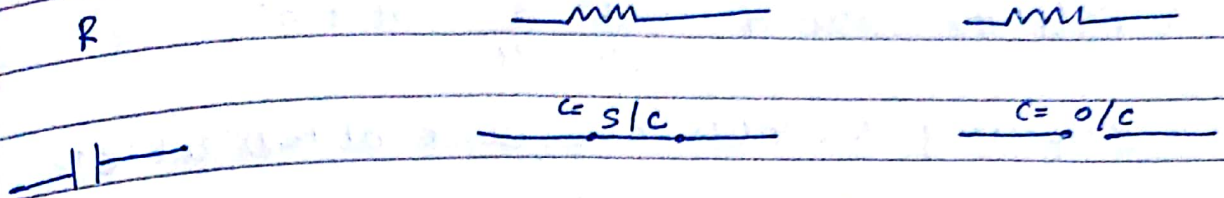


$t=0 \rightarrow$ sw open
 $t=0^- \rightarrow$ sw closed
 $t=0^+ \rightarrow$ sw open

Problems

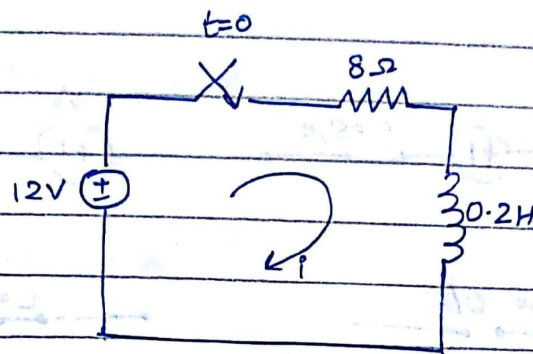1. In the given network, switch K is closed at $t=0$ with zero current in the inductor. Find the value of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$.

Referring the table take cases at $t=0^-$ & $t=0^+$




- * there cannot be sudden change in the current of inductor and voltage of capacitor

$$\therefore i_L(0^-) = i_L(0^+)$$

$$V_C(0^-) = V_C(0^+)$$

$\Rightarrow$ $t=0^+$ closed
 $t=0^-$ open switch

° at $t=0^-$

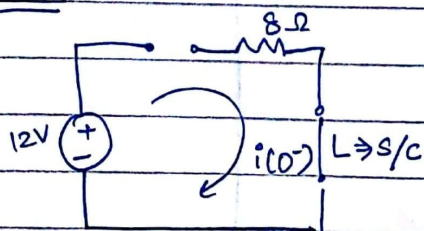


$i(0^-)$ is same as $i_L(0)$

current flowing is zero


$$\therefore i_L(0^-) = 0$$

$$\boxed{i_L(0^-) = i_L(0^+)} \\ \Rightarrow i(0^+) = i(0^-)$$

• at $t=0^+$

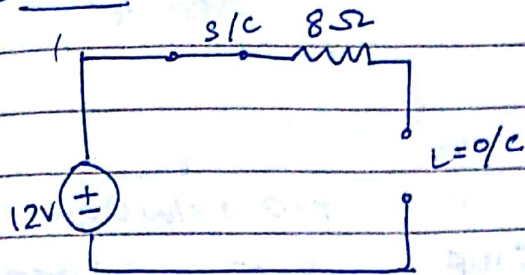

replace with original comp

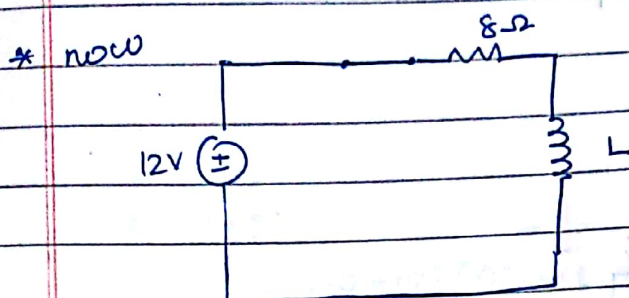

KVL

$$-12 + 8i(t) + L \frac{di}{dt}$$

at $t=0^+$

$$-12 + 8i(0^+) + L \frac{di(0^+)}{dt} = 0 \quad \text{--- (1)}$$

$$-12 + L \frac{di(0^+)}{dt} = 0$$

diff eq (1)

$$L \frac{di(0^+)}{dt} = 12$$

to find $\frac{d^2i}{dt^2}$ diff eq (1)

$$\frac{di(0^+)}{dt} = \frac{12}{0.2}$$

$$= 60 \text{ A/sec}$$


$$0 + 8 \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2} = 0$$

$$8 \times 60 + 0.2 \times \frac{d^2i(0^+)}{dt^2} = 0$$

$$\frac{d^2i(0^+)}{dt^2} = \frac{-480}{0.2} = \frac{-480 \times 10}{2} = -2400 \text{ A/sec}^2$$


2. The switch is closed at $t=0$, determine i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$

at $t=0^+$

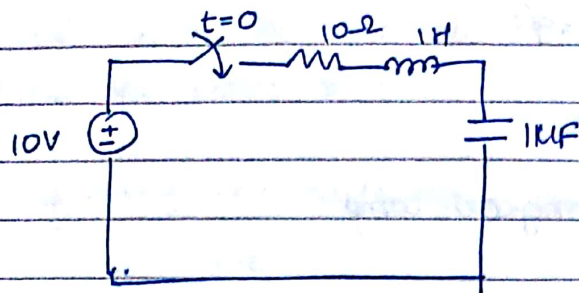

$t=0 \rightarrow$ s/w closed
 $t=0^- \rightarrow$ s/w open
 $t=0^+ \rightarrow$ s/w closed


• at $t=0^-$

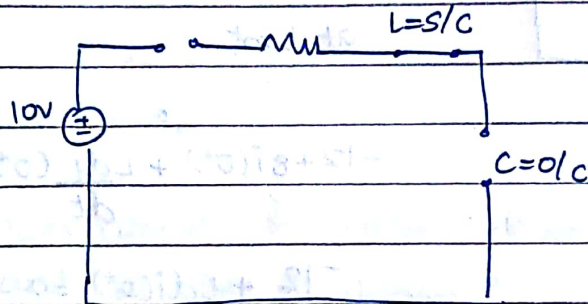


$$i_L(0^-) = 0 = i_L(0^+)$$

$$V_C(0^-) = 0 = V_C(0^+)$$

• at $t=0^+$

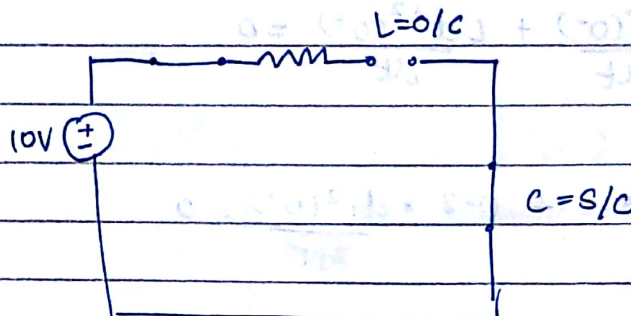

To find $\frac{di}{dt}$

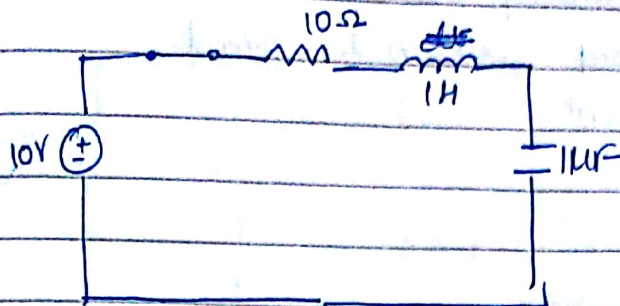

KVL

$$-10 + 10i(t) + L \frac{di(t)}{dt}$$

$$+ \frac{1}{C} \int_0^t i(t) dt = 0 \quad \text{--- (1)}$$

at $t=0^+$

$$-10 + 10i(0^+) + L \frac{di(0^+)}{dt} + \frac{1}{C} \int_0^t V_C(0^+) dt = 0$$

$$-10 + L \frac{di(0^+)}{dt} = 0$$

$$\frac{di(0^+)}{dt} = \frac{10}{1} = 10 \text{ A/sec}$$

To find $\frac{d^2i}{dt^2}$

diff the KVL eq:

$$10 \frac{di(t)}{dt} + L \frac{d^2i(t)}{dt^2} + \frac{1}{C} i(t) = 0$$


$$10 (10) + 1 \frac{d^2i(t)}{dt^2} + \frac{1}{1} = 0$$

$$100 + \frac{d^2i(t)}{dt^2} = 0$$


$$\frac{d^2i(t)}{dt^2} = -100 \text{ A/sec}^2$$

3. The switch K is changed from position 1 to position 2 at $t=0$. steady state condition having being reached position 1. Find $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0^+$.

→

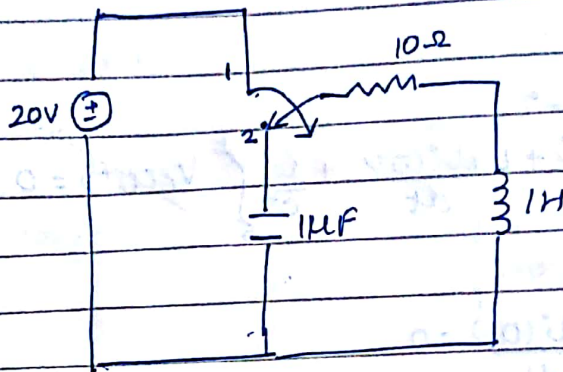

It was in pos 1 at $t=0^-$.

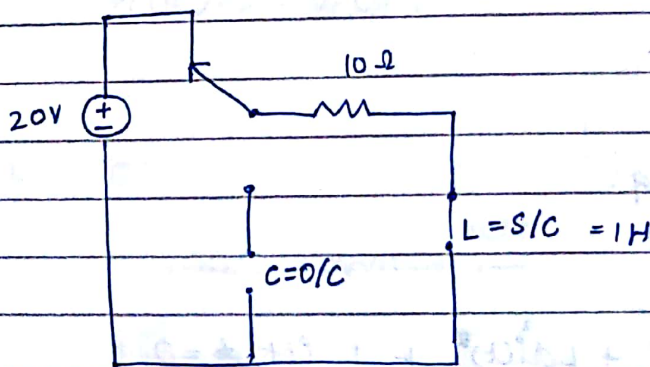

By ohm's law

$$I = V/R$$

$$= 20/10$$


$$= 2A$$

$$i_L(0^-) = i_L(0^+) = 2A$$


$$V_C(0^-) = 0 = V_C(0^+)$$

at $t=0^+ \Rightarrow$ pos 2.

store
67

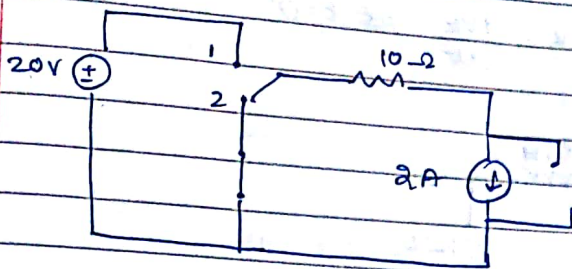

To find $\frac{di}{dt}$ at $t=0^-$

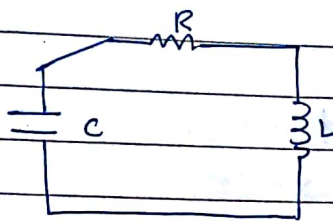

$$\frac{1}{C} \int_0^t i(t) dt + Ri(t) + L \frac{di}{dt} = 0 \quad \text{--- (1)}$$

$V_C(0^+)$

$$Ri(0^+) + L \frac{di(0^+)}{dt} = 0$$

$$\frac{di(0^+)}{dt} = -20 \text{ A/sec}$$

To find $\frac{d^2i(t)}{dt^2}$ at $t=0^+$

diff eq ①


$$\frac{1}{C} i(t) + R \frac{di(t)}{dt} + L \frac{d^2i(t)}{dt^2} = 0$$

$$\frac{2}{1\mu} + 10 \times (-20) + 1 \frac{d^2i(t)}{dt^2} = 0$$

$$-200 + 2 + \frac{d^2i(t)}{dt^2} = 0$$

$$\frac{d^2i(t)}{dt^2} = 200 - \frac{2}{1\mu} = 200 - 2 \times 10^6 = -1.9 \times 10^6$$

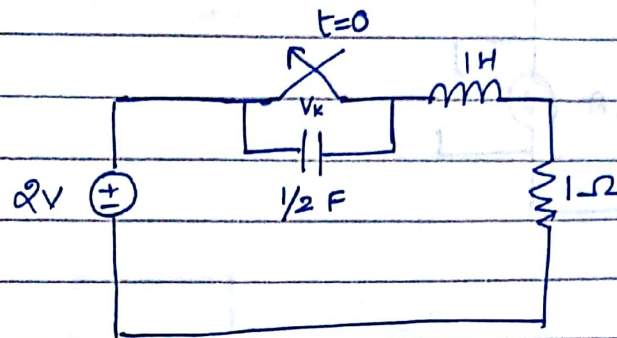
4. The circuit is in steady state with switch K closed. At $t=0$, switch is open, determine the voltage across the switch V_K , $\frac{dV_K}{dt}$ at $t=0^+$



$t=0^- \rightarrow$ switch was closed

$t=0^+ \rightarrow$ switch is opened

- at $t=0^-$

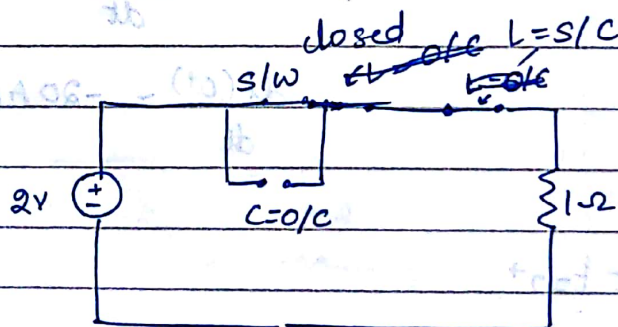


$$i_L(0^-) = 2A = i_L(0^+)$$

$$V_C(0^-) = 0 = V_C(0^+)$$

$$V_C = V_K$$

$$\Rightarrow V_K(0^+) = 0$$

• at $t=0^+$

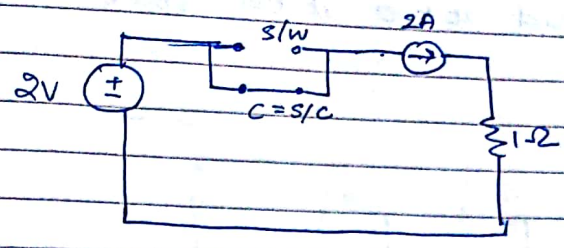

$$i_c(t) = C \frac{dv_c}{dt}$$


$$i_c(t) = C \frac{dv_k}{dt}$$

at $t=0^+$

$$i_c(t) = C \frac{dv_k}{dt}$$


$$2 = \frac{1}{2} \frac{dv_k}{dt}$$

$$4k = \frac{dv_k}{dt}$$

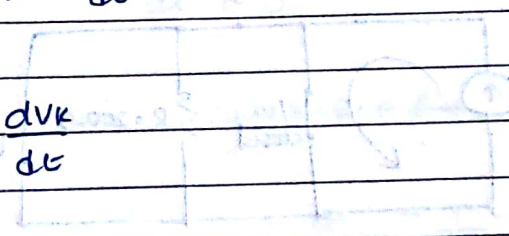

$$0 = (0) = (0)$$


$$0 = (0)$$

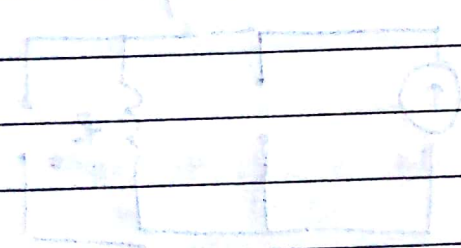

5. switch K is opened at $t=0$ at $t=0^+$ solve


$$V, \frac{dV}{dt}, \frac{d^2V}{dt^2}$$

→

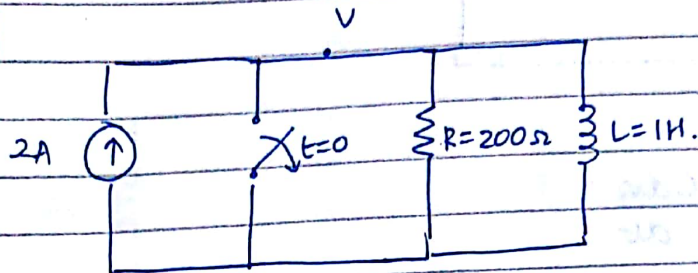

⇒ $t=0^-$ = switch was closed
 $t=0$ = switch open
 $t=0^+$ = switch open


at $t=0^-$

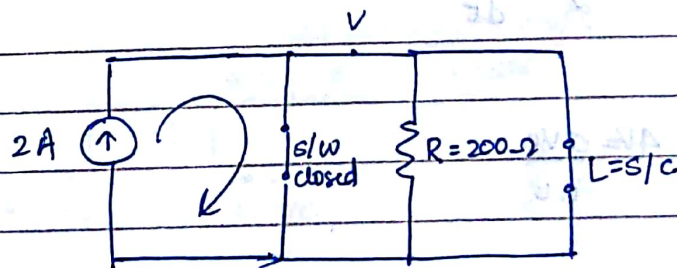


$$i_L(0^-) = i_L(0^+) = 0$$

$$V(0^-) = 0$$

at $t=0^+$

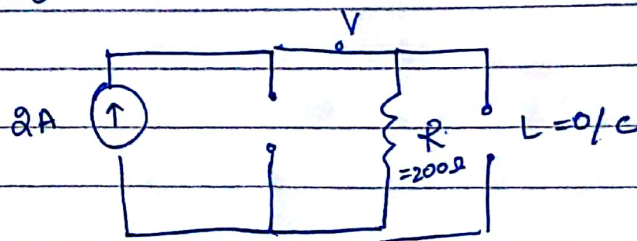
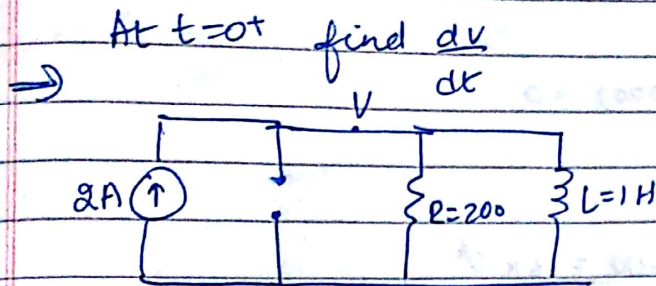
$$V(0^+) = 2 \times 200 = 400 \text{ V}$$



$\frac{dV}{dt} \rightarrow$ write KCL eq.

$$-2 + \frac{V}{200} + \frac{1}{L} \int_0^t V dt = 0 \quad \text{--- (1)}$$

diff this eq

$$0 + \frac{1}{200} \frac{dV}{dt} + \frac{1}{L} V(t) = 0 \quad \text{--- (2)}$$

at $t=0^+$

$$\frac{dV}{dt} = -200 \times$$

$$\frac{1}{200} \frac{dV}{dt} + \frac{1}{L} V(0^+) = 0$$

$$\frac{dV}{dt} = -\frac{400 \times 200}{1} = -80000$$

diff eq (2)


$$\frac{1}{200} \frac{d^2V}{dt^2} + \frac{1}{L} \frac{dV}{dt} = 0$$

$$\frac{1}{200} \frac{d^2 V}{dt^2} + \frac{1}{L} \frac{dV}{dt} = 0$$

$$\frac{1}{200} \frac{d^2 V}{dt^2} + (-800000) = 0$$

$$\frac{d^2 V}{dt^2} = 160000000 = 16 \times 10^6$$


H/w

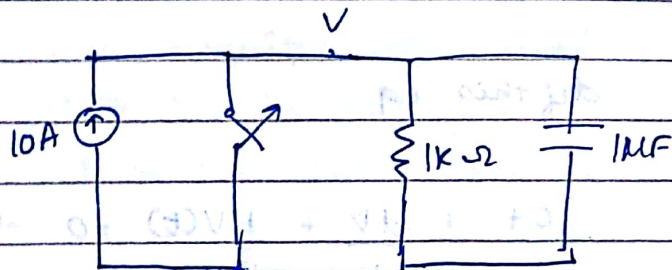


s/w K is open at $t=0$

At $t=0^+$ find $V, \frac{dV}{dt}, \frac{d^2 V}{dt^2}$

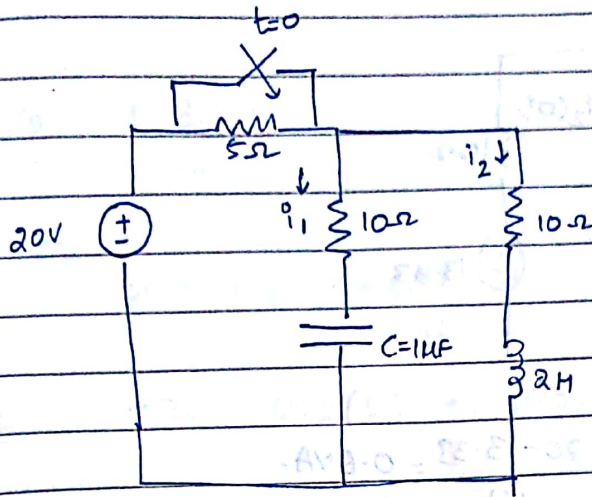6. steady state is reached with switch K open, the switch is closed at $t=0$. Determine $I_1, I_2, \frac{di_1}{dt}, \frac{di_2}{dt}$ at $t=0^+$



$t=0^-$ (previous stage)
open switch

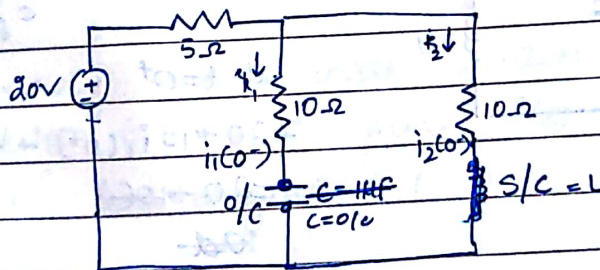


$$i_1(0^-) = 0$$

$$i_1 = i_2(0^-) = \frac{20}{5+10} = \frac{20}{15} = 1.33$$


$$V_c(0^-) = V_c(0^+) = \frac{20 \times 10}{15} = 13.3 \text{ V.}$$

main V
 opp branch R
 Total R

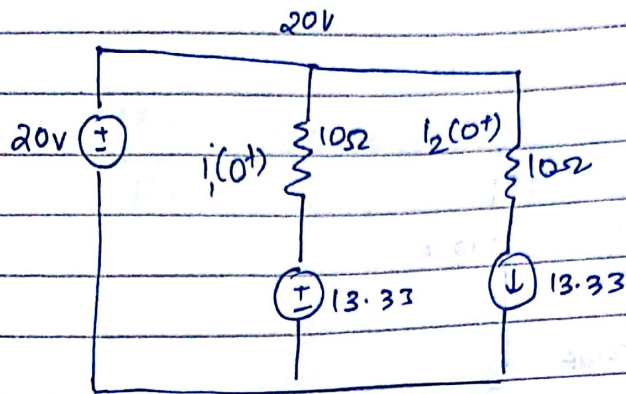- replace cap by 13.3V voltage source.
- replace inductor by current source $\downarrow 1.33$


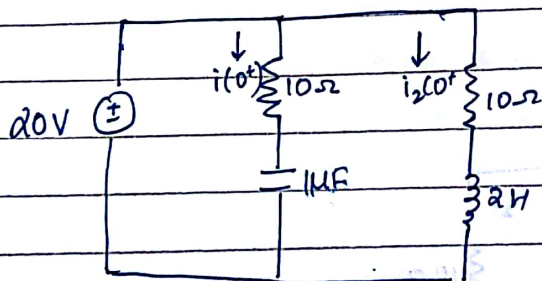
$$i_1(0^+) = \frac{20 - 13.3}{10} = 0.67 \text{ A}$$



KVL

$$-20 + 10i_1(t) + \frac{1}{C} \int_0^t i_1(t) dt = 0 \quad \text{--- (1)}$$

at $t=0^+$

$$-20 + 10i_1(0^+) + V_C(0^+) = 0$$

$$-20 + 10i_1(0^+) = 0$$

$$10i_1(0^+) = 20$$

to find $\frac{di_1}{dt}$ at $t=0^+$

diff eq (1)

$$0 + 10 \frac{di_1(0^+)}{dt} + \frac{i_1(t)}{C} = 0$$

$$10 \frac{di_1(0^+)}{dt} = -\frac{0.67}{1\mu F}$$

$$\frac{di_1(0^+)}{dt} = -0.67 \times 10^5 \text{ A/sec}$$

$$\frac{10 di_1(0^+)}{dt} = -0.67$$

To find $\frac{di_2}{dt}$

KVL:

$$-20 + 10i_2(t) + L \frac{di_2}{dt} = 0$$


$$-20 + 10i_2(0^+) + L \frac{di_2(0^+)}{dt} = 0$$

$$i_2(0^+) = 1.33$$


$$\frac{di_2(0^+)}{dt} = \frac{(-1.33)10 + 20}{L}$$

$$= \frac{-13.3 + 20}{2} = \frac{6.7}{2} = 3.35$$

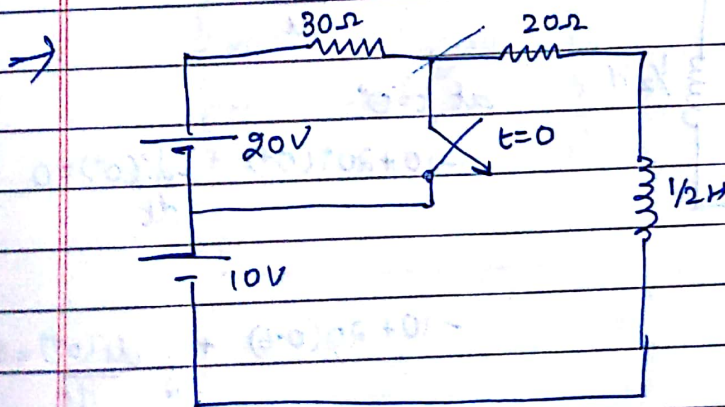7) Steady state with switch K open at $t=0$, the switch is closed find $i(t)$ at $t=0^+$ and $\frac{di(t)}{dt}$ at $t=0^+$ & also find $i(\infty)$.




$t=0^- \Rightarrow$ s/w open

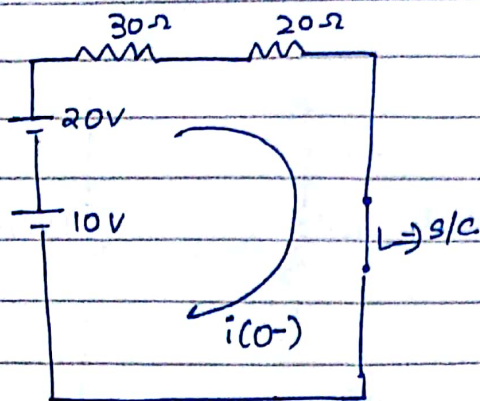

$$i(0^-) = \frac{30}{50} = 0.6A$$

$$i_L = i(0^-) = i(0^+)$$

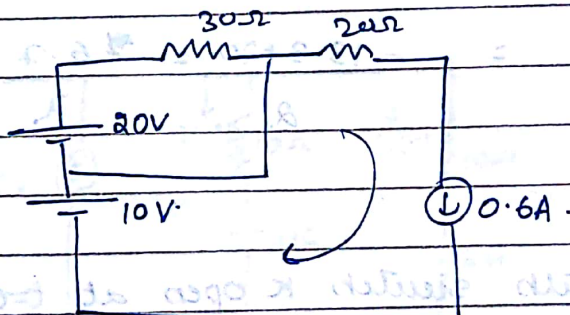

KVL

$$-10 + 20i + L \frac{di}{dt} = 0$$

at $t=0^+$


$$-10 + 20i(0^+) + L \frac{di(0^+)}{dt} = 0$$

$$-10 + 20(0.6) + \frac{1}{2} \frac{di(0^+)}{dt} = 0$$

~~-10 + 20~~

$$-10 + 12 + \frac{1}{2} \frac{di(0^+)}{dt} = 0$$
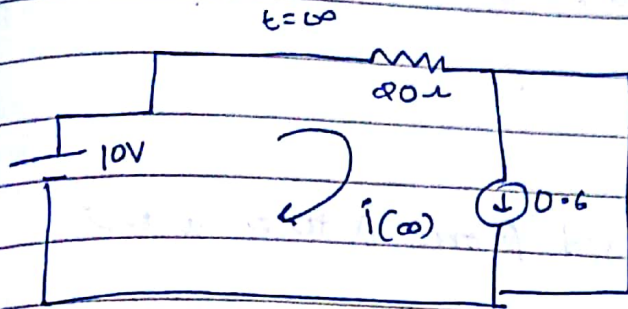
$$\frac{di(0^+)}{dt} = -2 \times 2 = -4 \text{ A/sec}$$




$$i(\infty)$$

$$-i(0) + 20i(\infty) = 0$$

$$i(\infty) = \frac{10}{25}$$

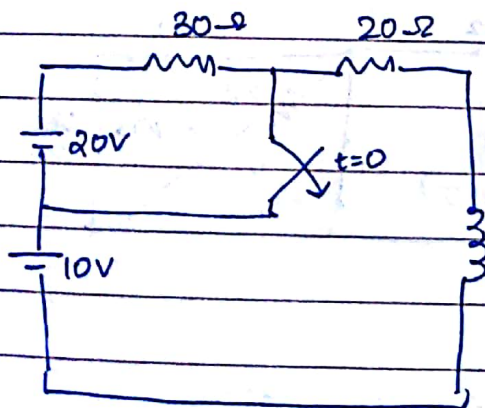- b) The network reaches steady state with switch K open, at $t=0$, the switch is closed. Find $i(t)$ for the numerical values given. Sketch the current waveform.



2 port
i/p o/p Imp - x
A parameters - x

Fourier time.
concept of time const
System govern charac
Initial cond

$$i_L = [\text{final value}] + [\text{initial} - \text{final value}] e^{-t/\tau}$$

$$= 0.5 + [0.6 - 0.5] e^{-t/\tau}$$

$$i_L(t) = 0.5 + 0.1 e^{-t/\tau}$$


transfer func-
CRC & RC
RL models

$$\tau = L/R = 0.5/20 = 25 \text{ ms}$$


How much

Imp 9) The switch is changed from A to B at $t=0$.
Show that at $t=0^+$
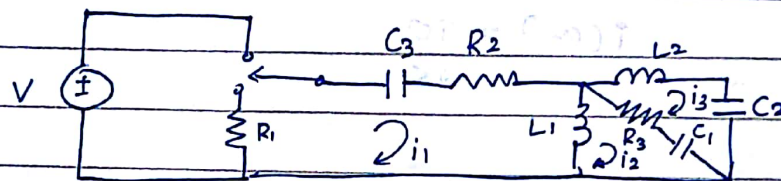
$$i_1 = i_2 = \frac{-V}{R_1 + R_2 + R_3}, \quad i_3 = 0.$$



→ switch at $t=0^+$ switch will be at B.

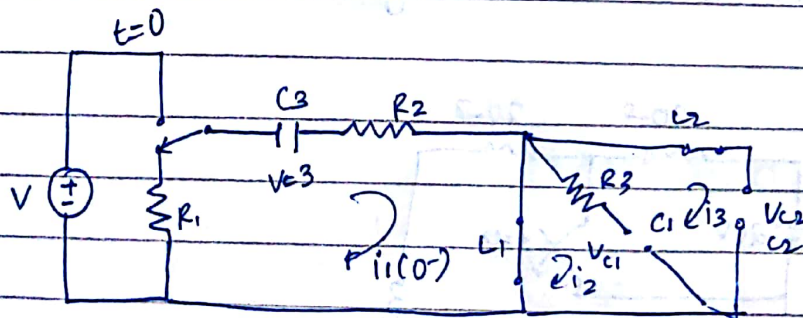


$$i_1(0^-) = 0$$

$$V_{c3}(0^-) = V_{c1}(0^-)$$

$$V_{c3}(0^+) = V_{c1}(0^+) = 0$$

$$V_{c2}(0^-) = 0 = V_{c2}(0^+)$$

At $t=0^+$

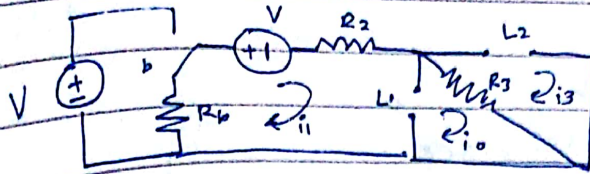


$$R_1 i_1 + V + R_2 i_2 + R_3 i_3 = 0$$

$$i_1 (R_1 + R_2 + R_3) = -V$$

$$\therefore i_1 = \frac{-V}{R_1 + R_2 + R_3}$$

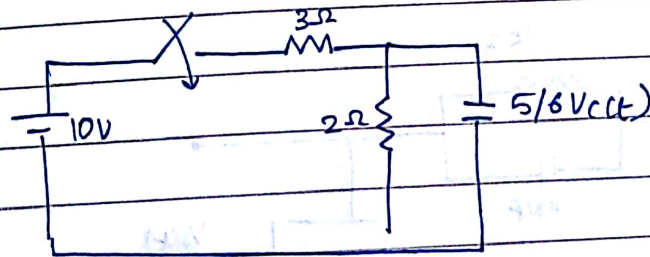- 10 In the circuit shown the switch is closed at $t=0$. Assuming zero initial condition, find $V_C(t)$ at $t=1\text{sec}$.
~~find the value of $V_C(t)$~~



$$V_C(t) = [\text{final}] + [\text{initial} - \text{final}] e^{-t/\tau}$$

$$\Rightarrow V_C(\infty) = \frac{10 \times 2}{5}$$

$$V_C(\infty) = \frac{1}{2} \times 4V$$

$$V_C(t) = 4 + [0 - 4] e^{-t/\tau}$$

continued


$$V_C(t) = 4(1 - e^{-t/1}) \text{ V}$$

τ value is calculated.

$$\tau = R_{eq} C$$

$$\tau = 1.2 \times \frac{5}{6} = 1 \text{ sec}$$


$$\rightarrow V_C(t) \Big|_{t=1 \text{ sec}} = 2.52 \text{ Volts}$$

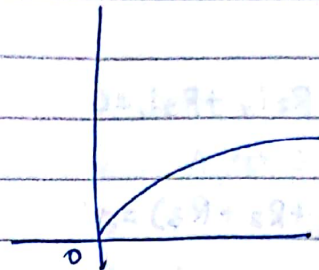

11) In the figure shown below assume that all the caps are initially uncharged. If $V_1(t) = 10u(t) \text{ Volts}$ find $V_o(t)$.

$$V_1(t) = 10u(t)$$

$$V_o(t) = ?$$

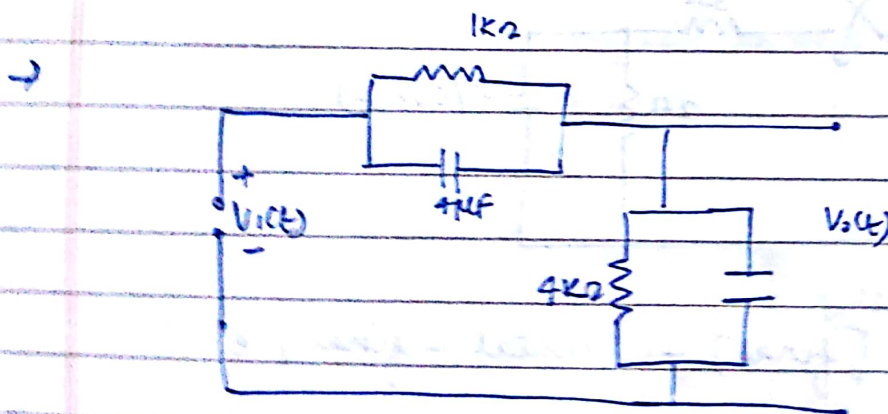

$$V_o(t) = [\text{final value}] + [\text{initial value}] e^{-t/\tau}$$

$$V_o(0^-) = V_o(0^+) = 0 \text{ V}$$

final value = the capacitor

behaves as

$\frac{V_c(t)}{V_c(t)}$

Final value = 8

Initial = 0.

$$V_c(t) = 8 + [0 - 8] e^{-t/\tau}$$


$$\tau = R_{eq} C_{eq} = 0.8k \times 8\mu$$

$$\tau = 6.4ms$$

• Time Response

$$i_c(t) = \frac{V}{R} e^{-t/\tau}$$

$$V_c(t) = V(1 - e^{-t/\tau})$$

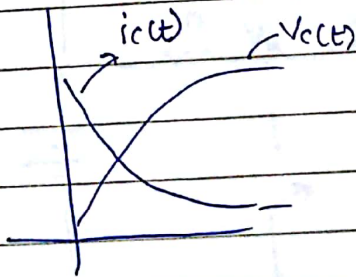




• Frequency response

$$H(s) = \frac{1}{Rs + 1}$$

$$s = \sigma + j\omega$$


$$H(s) = \frac{1}{RC(j\omega)}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + R^2 C^2 \omega^2}}$$

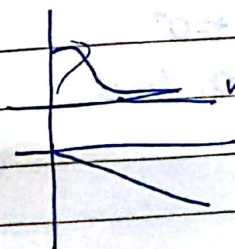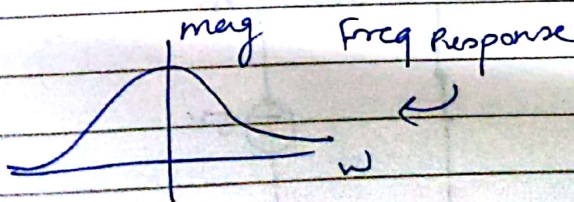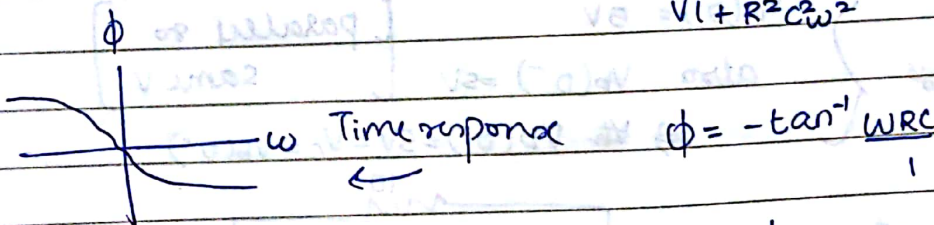


13 NOV 2018

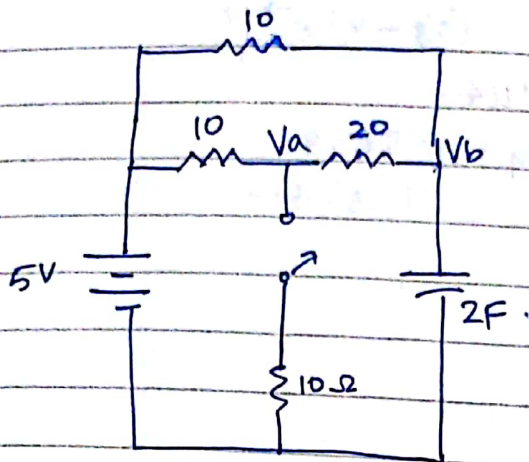12. The steady state is reached with switch K open. at $t=0$, the switch K is closed, Determine the values of $V_a(0^-)$ and $V_a(0^+)$




→ At $t=0^-$ switch open.

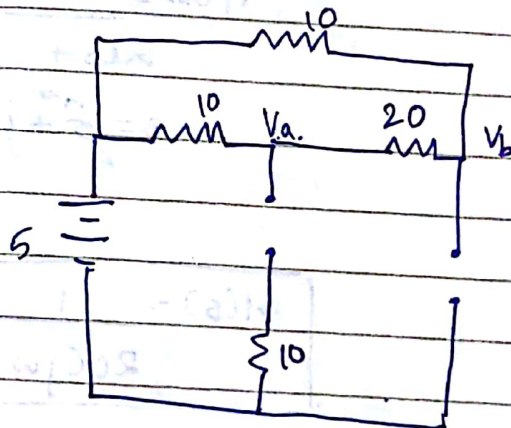

* doubt { $V_a(0^-) = 5V$
also $V_b(0^-) = 5V$ [parallel so same V]
 $\Rightarrow V_b(0^-) = 5V = V_c = V_b(0^+)$

At $t=0^+$
Switch closed

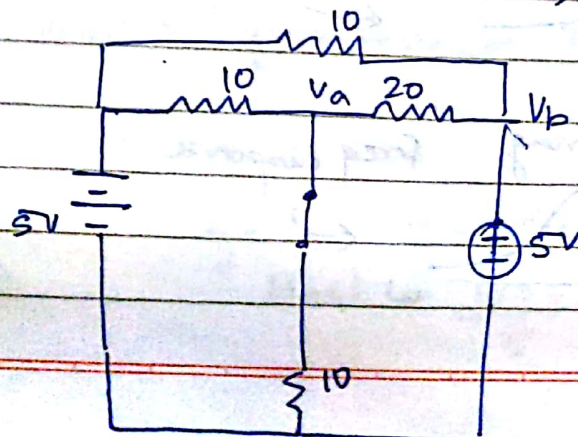

store
67

applying KVL

$$\frac{V_a - 5}{10} + \frac{V_a}{10} + \frac{V_a - 5}{10} = 0$$


$$\frac{V_a(0^+) - 5}{10} + \frac{V_a(0^+)}{10} + \frac{V_a(0^+) - 5}{20} = 0$$

$$V_a(0^+) \left[\frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right] = \frac{5}{20} + \frac{5}{10}$$

$$V_a(0^+) = \frac{0.75}{0.075}$$


$$V_a(0^+) = \underline{\underline{3.33\text{V}}}$$

HW

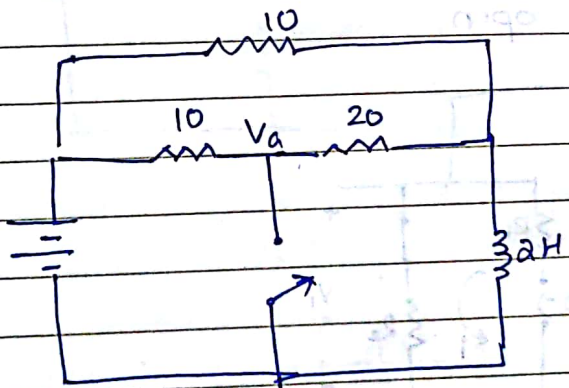


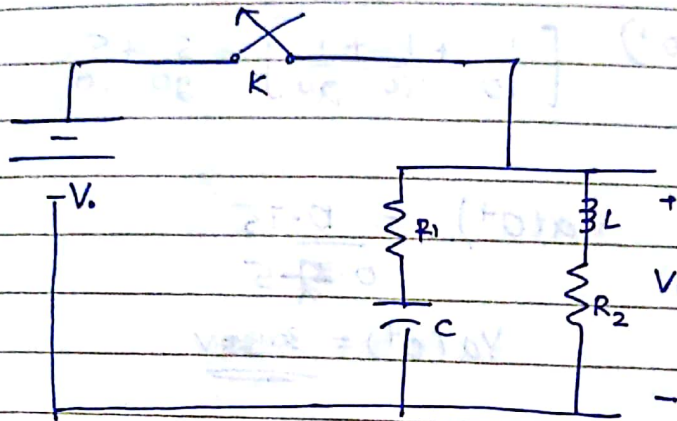13. The switch K in the network is closed at $t=0$. Connecting the battery to an unenergised network, determine i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$.

Determine V_1 , $\frac{dV_1}{dt}$ and $\frac{d^2V_1}{dt^2}$ at $t=0^+$.



→ At $t=0^-$ switch was open.

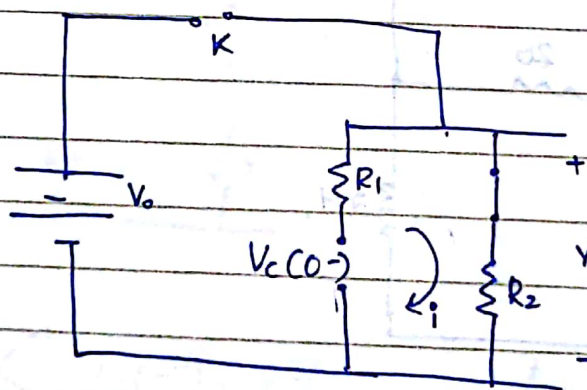


$$V_C(0^-) = 0 = V_C(0^+)$$

$$V_1(0^-) = \frac{V_0}{R_2} \cdot 0$$

$$i(0^-) = 0$$


$$i(0^-) = i(0^+) = 0$$

At $t=0^+$ switch was closed

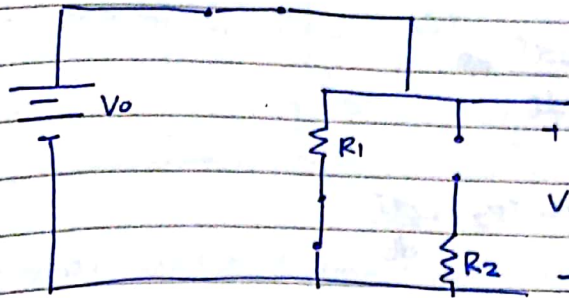

$$V_1(0^+) = V_0$$

$\Rightarrow$

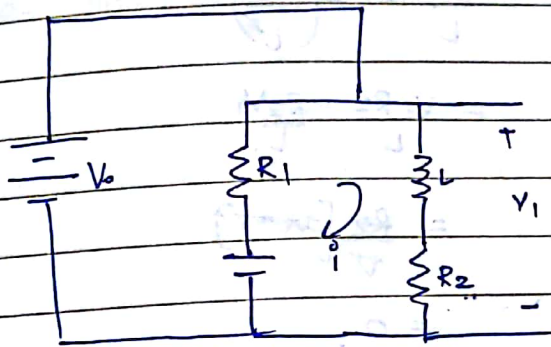

$$-V_0 + L \frac{di}{dt} + R_2 i = 0 \quad \text{--- ①}$$

$$\left[\frac{di}{dt} = \frac{V_0}{L} \text{ A/sec} \right] \quad \text{--- ②}$$

diff eq ①

$$\frac{d^2 i}{dt^2} =$$

$$+L \frac{d^2 i}{dt^2} + R_2 \frac{di}{dt} = 0$$

$$L \frac{d^2 i}{dt^2} + R_2 \frac{V_0}{L} = 0$$

$$\left[\frac{d^2 i}{dt^2} = -\frac{R_2 V_0}{L^2} \right] \text{ Asec}^2$$

$$V_1(0^-) =$$

$$V_1 = iR_2 + L \frac{di}{dt}$$

$$V_1 = iR_2 + L \frac{di}{dt}$$

def this eq

$$\frac{dV_1}{dt} = \frac{di}{dt} R_2 + L \frac{d^2i}{dt^2}$$


$$= \frac{V_0}{L} R_2 + \cancel{L} \left(-\frac{R_2}{L} \right) V_0$$

$$= \frac{V_0 R_2}{L} - \frac{R_2 V_0}{L}$$

$$= \frac{R_2}{L} [V_0 - V_0]$$


$$= 0$$

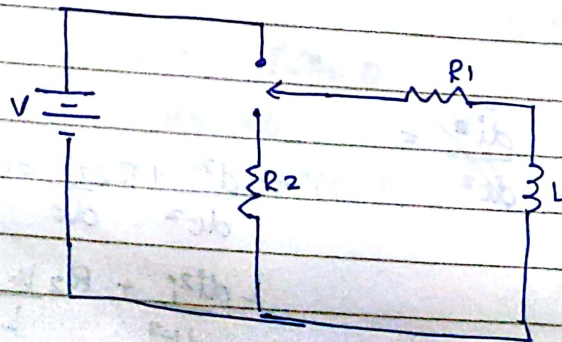4) In the network of figure, switch K is moved from position 1 to position 2 at $t=0$. Steady state current having previously been reached in the RL circuit, find the particular solution for the current $i(t)$.



$$i(t) = \frac{V}{R} e^{-\frac{R_1 + R_2}{L} t}$$

2)

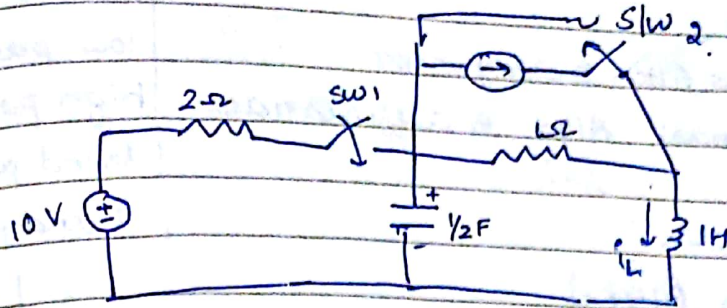

Assume that switch 1 has been opened and switch 2 has been closed for a long time and steady state condition is at $t=0^-$. Find $i_L(0^+)$ and $v_C(0^+)$

$\frac{dv(0^+)}{dt}$ and $\frac{di(0^+)}{dt}$


$$\text{Ans} = i_L(0^+) = 0 \quad v_C(0^+) = -8 \quad \frac{di(0^+)}{dt} = -2 \text{ A/sec} \quad \frac{dv_C(0^+)}{dt} = 12 \text{ V/s}$$

* Application of RC.


- RC as low pass filter & integrator.
- RC as high pass filter & differentiator.

low pass	
high pass	
band pass	
band rejection	

* RC as low pass filter.

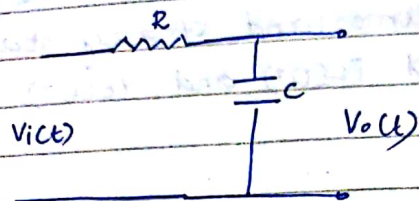
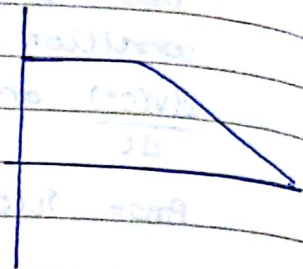
$$X_C = \frac{1}{2\pi fC} = \text{Reactance}$$



- $f=0$ $X_C = \infty$ $\text{cap} = q/c$ $V_{out} = V_{in}$
- $f=\infty$ $X_C = 0$ $\text{cap} = s/c$ $V_{out} = 0$.

$$H(s) = \frac{1}{RCs+1} \quad \leftarrow \text{Transfer function}$$

$$\text{sub } s=j\omega$$

$$H(s) = \frac{1}{RCj\omega+1}$$

$$\omega = 2\pi f$$

$$H(j\omega) = \frac{1}{RCj2\pi f+1}$$

$$f_c = \text{cut off freq} = \frac{1}{2\pi RC}$$

$$H(j\omega) = \frac{1}{j f/f_c + 1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$\phi = -\tan^{-1}\left(\frac{f}{f_c}\right)$$

$$f=0$$


$$\begin{matrix} \text{mag} & \phi \\ 1 & 0 \end{matrix}$$

$$f=f_c$$


$$\frac{1}{\sqrt{2}} \quad -\pi/4 \quad -45^\circ$$

$$f=\infty$$



$$0 \quad -\pi/2 \quad -90^\circ$$

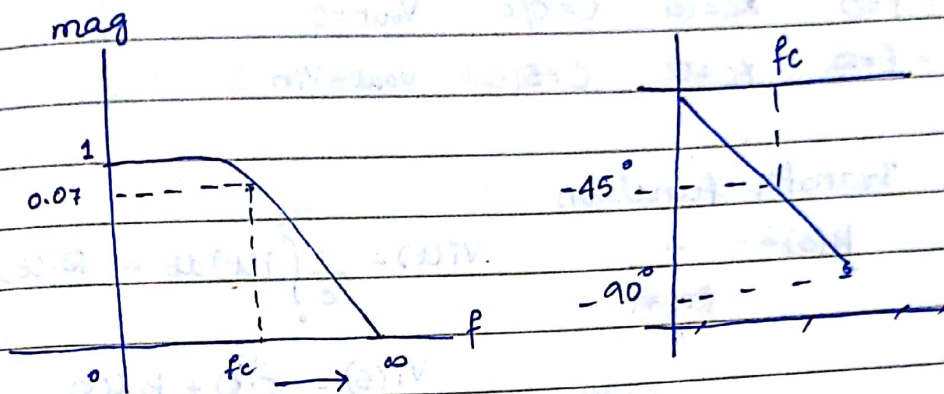

• f_c is also called as -3db line

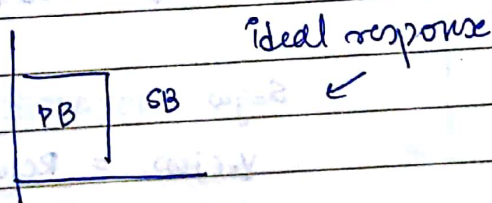

* RC as a HIGH PASS FILTER.

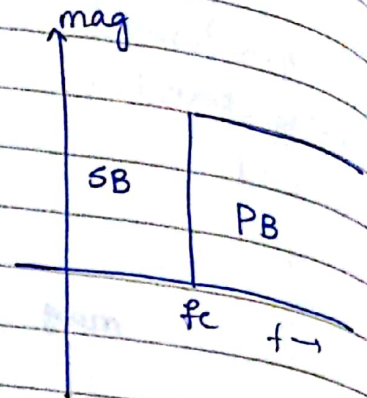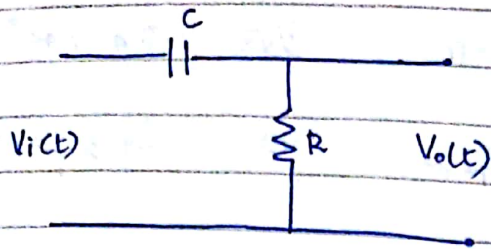

- $f=0$ $X_C=\infty$ $C=0/C$ $V_{out}=0$
- $f=\infty$ $X_C=0$ $C=S/C$ $V_{out}=V_{in}$

Transfer function

$$H(s) = \frac{+}{RCS + 1}$$

$$V_i(t) = \frac{1}{C} \int i(t) dt + Ri(t)$$

sub $s=j\omega$.

$$V_i(s) = \frac{I(s)}{Cs} + RI(s)$$

$$V_o = Ri(t)$$

$$V_o(s) = RI(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{RCS}{RCS + 1}$$

$$s=j\omega$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{RCj\omega}{RCj\omega + 1}$$

$$\omega = 2\pi f$$

$$H(j\omega) = \frac{RCj2\pi f}{RCj2\pi f + 1}$$

$$= \frac{j(f/f_c)}{j(f/f_c) + 1}$$

$$|H(j\omega)| = \frac{f/f_c}{\sqrt{(f/f_c)^2 + 1}}$$

$$\phi = \tan^{-1} \frac{f}{f_c} - \tan^{-1} \frac{f}{f_c}$$



$\underbrace{\quad}_{0}$ $\underbrace{\quad}_{90^\circ}$ $\underbrace{\quad}_{\tan^{-1} \frac{1}{f}}$

$$\phi = 90 - \tan^{-1}(f/f_c)$$


$f=0$ mag 0 ϕ 90°

$f=f_c$ mag 1/√2 ϕ 45°

$f=\infty$ mag 1 ϕ 0°

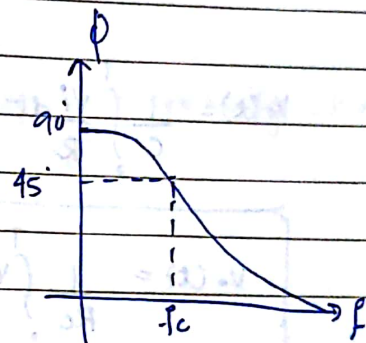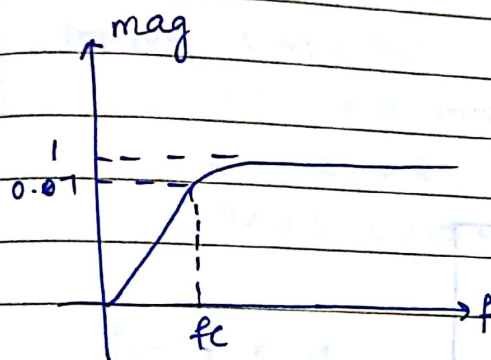


* RC as INTEGRATOR.

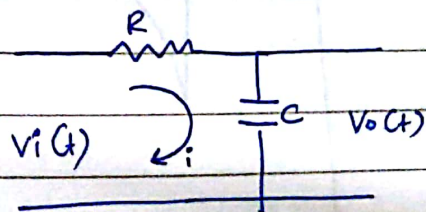

To make RC work as integrator $R_C \gg T$

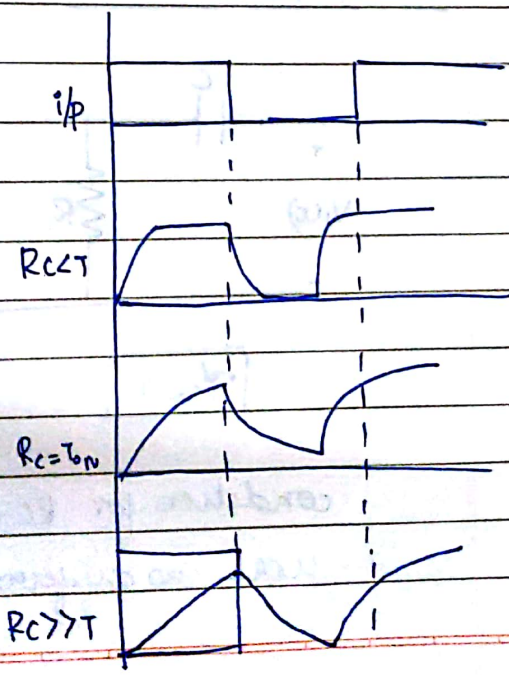$\Rightarrow \therefore RC \gg T$ to get
 triangular wave from
 square wave



small τ = cap charges fast
 large τ = cap charges slow

$$V_o(t) = \frac{1}{C} \int_0^T i(t) dt$$

$$i(t) = \frac{V_R}{R}$$


Approx $V_R \approx V_{in}$ under the condn $RC \gg T$.

cuz cap charges very slowly cuz of less τ and takes less $V_{in} \therefore V_R$ takes more $V_{in} \therefore V_R \approx V_{in}$.

$$V_o(t) = \frac{1}{C} \int_0^T \frac{V_i dt}{R}$$


$$V_o(t) = \frac{1}{RC} \int_0^T V_i(t) dt$$


* RC as DIFFERENTIATOR

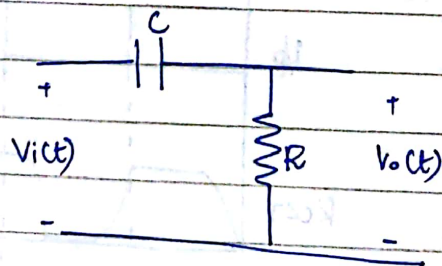

$$\tau \ll T$$

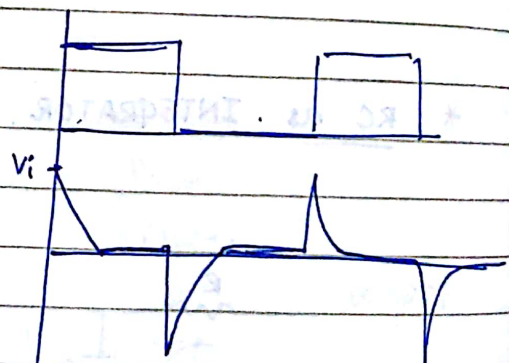condition for RC to
 work as differentiator



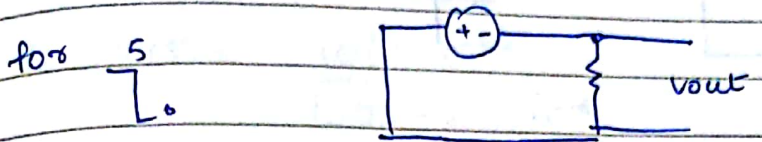

$$V_o(t) = R \cdot i(t)$$

$$i(t) = C \frac{dv}{dt}$$

Approx $V_c \approx V_{in} \approx V$

cuz τ is $\ll$ small. $\therefore$ cap is completely charged


less V across R

more V across C .


$$\therefore i(t) = C \cdot \frac{dV_i}{dt}$$

$$V_o(t) = R \cdot C \frac{dV_i(t)}{dt}$$

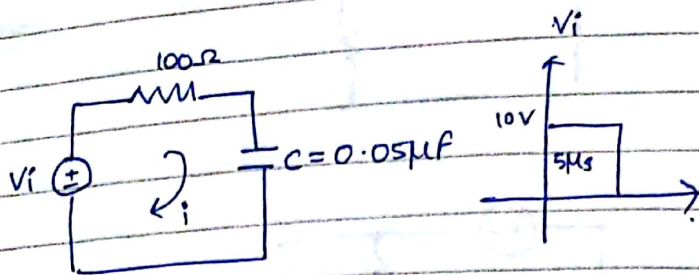Q.1 Find the current $I(t)$ assuming 0 initial condition


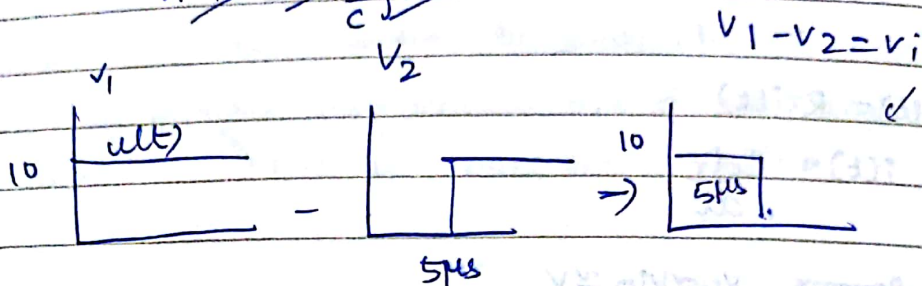
$$-V_i + 100i + \frac{1}{C} \int i dt = 0$$



$$V_i(t) = 10 [u(t) - u(t - 5\mu s)]$$

$$V(s) = 10 \left[\frac{1}{s} - \frac{e^{-5\mu}}{s} \right]$$

KVL

$$-\frac{V_i(t)}{s} + R \cdot i(t) + \frac{1}{C} \int_0^t i(t) dt = 0$$

LT.

$$-V_i(s) + 100 \cdot I(s) + \frac{I(s)}{Cs}$$

$$V_i(s) = I(s) \left[100 + \frac{1}{Cs} \right]$$

$$V_i(s) = I(s) \left[\frac{100s + 1}{0.05} \right]$$

$$V_i(s) = I(s) \left[\frac{100s + 20 \times 10^{-6}}{s} \right]$$

$$\frac{10}{s} [1 - e^{-5u}] = I_s \left[\frac{100s + 20 \times 10^{-6}}{s} \right]$$

$$I(s) = \frac{10(1 - e^{-5u})}{100s + 20 \times 10^{-6}}$$

$$I(s) = \frac{10(1 - e^{-5u})}{100(s + 2 \times 10^5)}$$



$$I(s) = 0.1 \frac{(1 - e^{-5u})}{s + 2 \times 10^5} = \frac{0.1}{s + 2 \times 10^5} - \frac{e^{-5u} \cdot 0.1}{s + 2 \times 10^5}$$

L^{-1}

$$i(t) = 0.1 e^{-2 \times 10^5 t} - \frac{0.1}{0.1} e^{-2 \times 10^5 t}$$

$$0.1 e^{-2 \times 10^5 t} (t - 5u) \quad u(t - 5u)$$

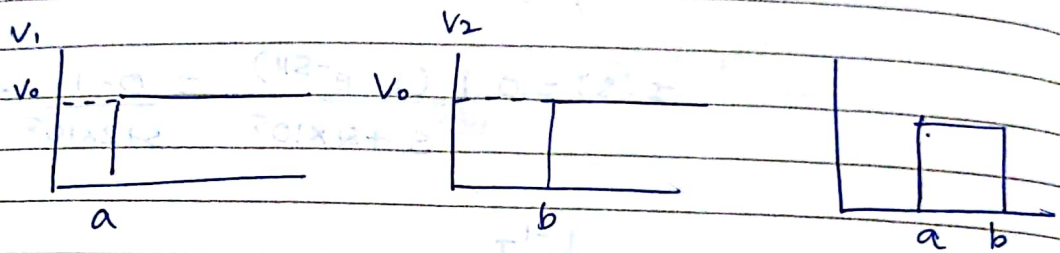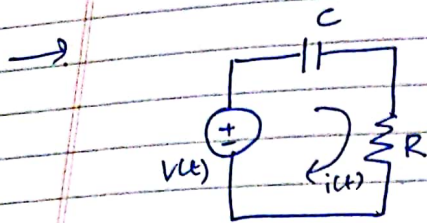Q-2 Consider the RC network shown below. Input is the rect pulse as shown below, find $i(t)$ by assuming zero initial condition.



$$V(t) = V_0 [u(t-a) - u(t-b)]$$

KN eg

$$V_i(t) = \frac{1}{C} \int_0^t i(t) dt + R \cdot i(t)$$

$$V_0 [u(t-a) - u(t-b)] = \frac{1}{C} \int_0^t i(t) dt + R \cdot i(t)$$

taking Laplace

$$\frac{V_0}{s} [e^{-as} - e^{-bs}] = \left[R + \frac{1}{Cs} \right] I(s)$$

$$\frac{V_0}{s} [e^{-as} - e^{-bs}] = I(s) \left[\frac{RCs + 1}{Cs} \right]$$

$$\frac{V_0}{s} [e^{-as} - e^{-bs}] = \frac{I(s)}{RC} \left[\frac{s+1}{RC} \right]$$

$$V_0 [e^{-as} - e^{-bs}] = I(s) \cdot R \left(\frac{s+1}{RC} \right)$$

$$I(s) = \frac{V_0 (e^{-as} - e^{-bs})}{R \left(\frac{s+1}{RC} \right)}$$

$$I(s) = \frac{V_0}{R} \left[\frac{e^{-as}}{s+1} - \frac{e^{-bs}}{s+1} \right]$$

← I T
inverse laplace

$$i(t) = \frac{V_0}{R} \left[e^{-\frac{(t-a)}{RC}} u(t-a) - e^{-\frac{(t-b)}{RC}} u(t-b) \right]$$

PHASORS

Rotating vector which helps to represent phase shift

Representation of phasor 1.

polar form	$V_m \angle \theta$
Rectangular form	$A + jB$
Exp form	$V_m e^{j\phi}$

Rec $\rightarrow$ Polar

polar $\rightarrow$ rec

$$V_m = \sqrt{A^2 + B^2}$$

$$A = V_m \cos \theta$$

$$\theta = \tan^{-1} \left(\frac{B}{A} \right)$$

$$B = V_m \sin \theta$$

For R $\Rightarrow$ V & I are in phase

For Cap, C

$$X_C = \frac{1}{j\omega C}$$

$$\frac{V}{I} = \frac{1}{j\omega C}$$

$$V j\omega C = I$$

$$I = j\omega C \cdot V$$

$\therefore$ I leads V


For inductor

$$X_L = j\omega L$$

$$\frac{V}{I} = j\omega L$$

$$\frac{V}{j\omega L} = I$$

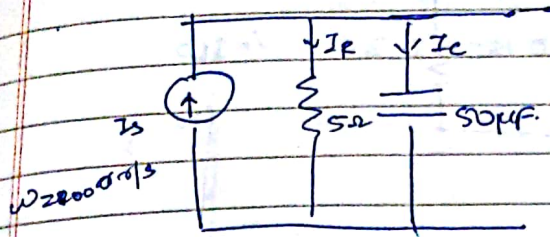1) Determine $I(s)$ using phasor diagram.



$$I(s) = I_R + I_C$$

$$V = 110^\circ = 1 + j0$$


$$I_R = \frac{V}{R} = \frac{110^\circ}{5} = 0.2 \angle 0^\circ = 0.2 + j0 \text{ Amp}$$

$j = 90^\circ$ always

$$X_C = \frac{1}{j\omega C} = \frac{1}{j \times 2000 \times 50 \times 10^{-6}} = \frac{1}{j0.1} = -j10 = 10 \angle -90^\circ$$

$$I_C = \frac{V}{X_C} = \frac{110^\circ}{10 \angle -90^\circ} = 0.1 \angle 90^\circ = j0.1 \text{ A}$$

$$I(s) = I_R + I_C$$

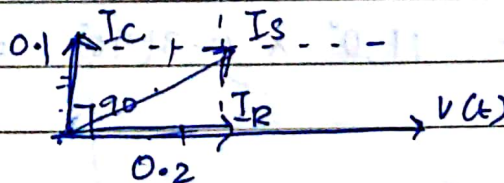


||gm law of addition

$$I_s = I_R + I_C$$

$$I_s = 0.2 + j0.1 \Rightarrow 0.22 \angle 26.56^\circ$$

2)

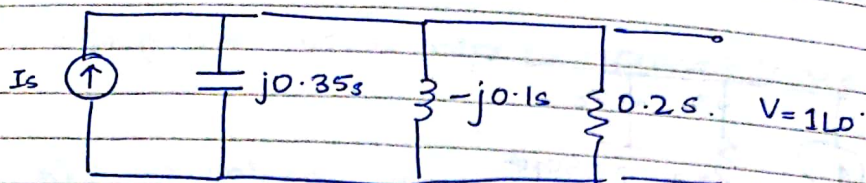

$\Rightarrow$

$$I_x = I_L + I_R$$

$$I_s = I_C + I_x$$

$$\rightarrow I_R = \frac{V}{R} = V \times 0.2 = 0.2 \angle 0^\circ$$

$$I_C = \frac{V}{X_C} \Rightarrow \frac{1 \angle 0^\circ \times 0.1 \angle 90^\circ}{62.8 \angle 90^\circ} =$$

they are in series so multiply

$$X_L = \omega L = 2\pi \times 0.1 = 0.628 \angle 90^\circ$$

$$X_L = -j0.1s = 0.1 \angle -90^\circ$$

$$I_C = \frac{V}{X_C}$$

in series so multiply.

$$X_C = V \times j0.35 = 0.3 \angle 90^\circ$$

$$= \frac{1 \angle 0^\circ}{0.3 \angle 90^\circ} = 3.33 \angle -90^\circ$$

$$I_C = 1 \angle 0^\circ \times 0.3 \angle 90^\circ = 0.3 \angle 90^\circ$$

$$= 0.3j$$

$$I_x = I_L + I_R$$

$$= 0 - 0.1j + 0.2$$



$$= 0.2 - 0.1j = 0.22 \angle -26.5^\circ$$

$$I_s = I_c + I_x$$

$$= 0.3j + 0.2 - 0.1j$$

$$= 0.2 + 0.2j$$


$$= 0.28 \angle 45^\circ$$

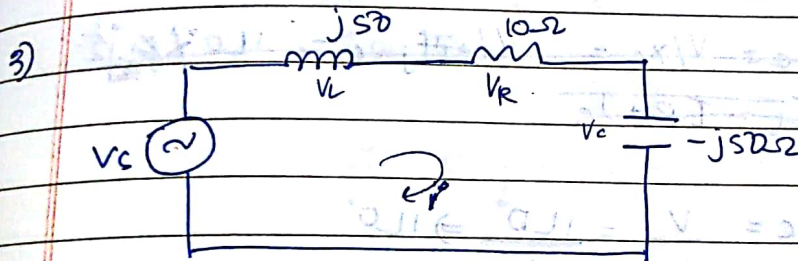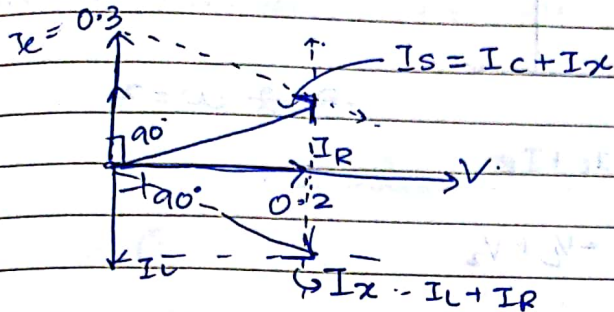


Let $I = 0.2 \angle 0^\circ$ Amp

Ans $\Rightarrow$
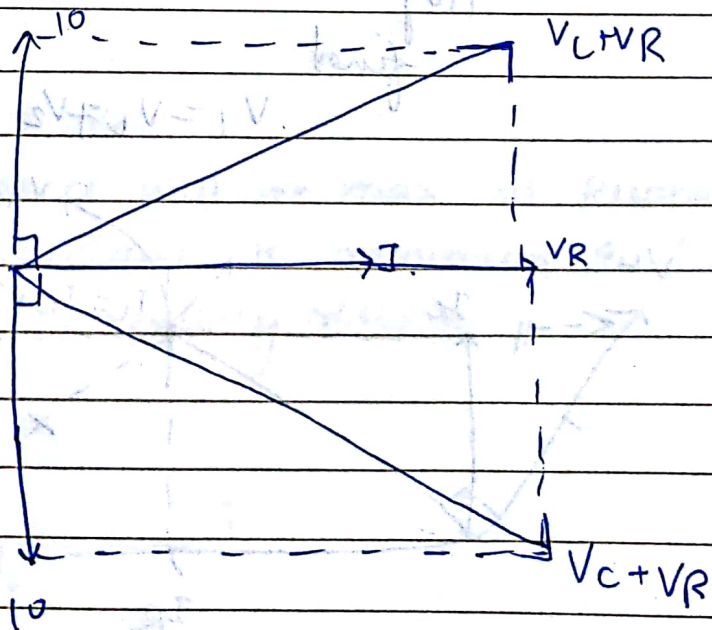
$$V_R = 2 \angle 0^\circ \quad V_C = 1 \angle -90^\circ \quad V_L = 1 \angle 90^\circ$$



4)

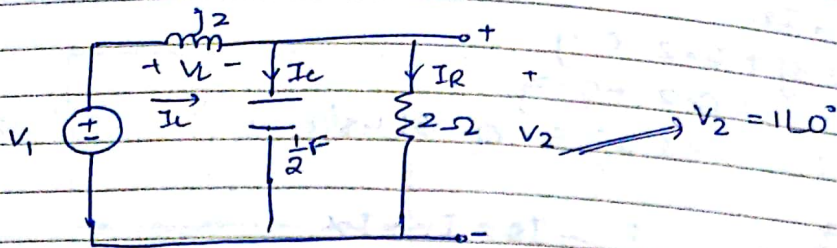

$$I_L = I_C + I_R$$

$$V_1 = V_L + V_2$$

$$I_R = \frac{V}{R} = 0.5 \angle 0^\circ$$


$$I_C = \frac{V}{X_C} = \frac{V}{\frac{1}{j\omega C}} = 1 \angle 0^\circ$$

$$I_C = \frac{V}{X_C} = \frac{1 \angle 0^\circ}{1} \Rightarrow 1 \angle 0^\circ$$

$$I_L = I_R + I_C$$


11y
final

$$V_1 = V_L + V_2$$

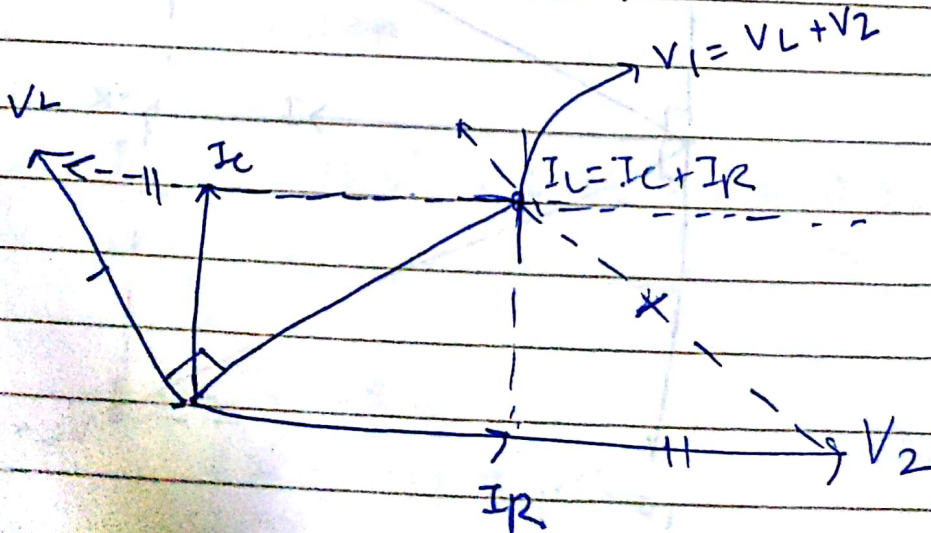

RESONANCE

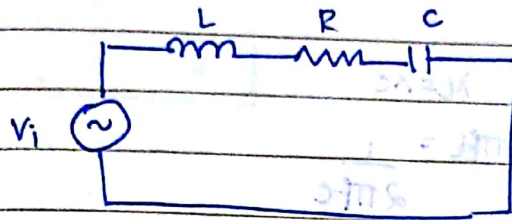- Series Resonance - acceptor circuit
parallel Resonance - rejector circuit



$$Z = R + X_L + X_C$$

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$


At resonance


$$X_L = X_C$$

then

$$|Z| = R$$

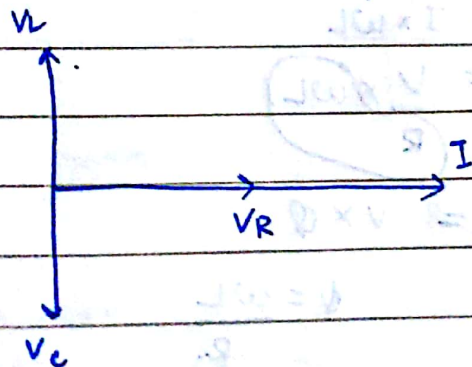the current will be max at Resonance
& impedance is minimum & the
circuit is purely resistive



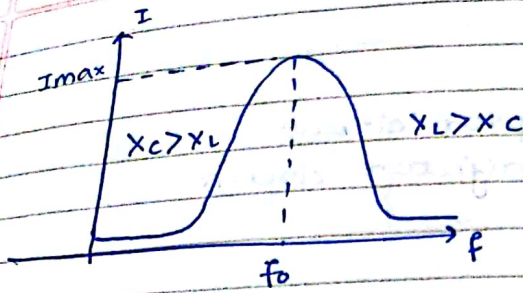

At resonance $X_L = X_C$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$f = \sqrt{\frac{1}{4\pi^2 LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Series Resonance — voltage magnifying device

$$V_{XL} = I \times X_L$$

$$= I \times \omega L$$

$$= \frac{V}{R} \times \omega L$$

$$V_{XL} = V \times Q$$

$$Q = \frac{\omega L}{R}$$

$$Q = \frac{\omega_0 L}{R}$$


quality factor

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega_0 L}{R}$$

$$Q = \sqrt{\frac{L}{C} \times \frac{1}{R}}$$

Bandwidth

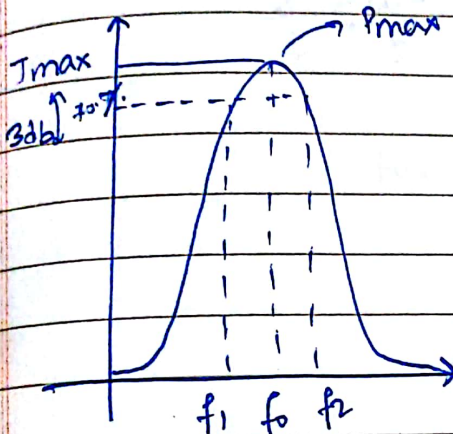


$$P_{max} = I_{max}^2 \cdot R$$

$$I = \frac{I_{max}}{\sqrt{2}}$$

$$P_{f1f2} = \left(\frac{I_{max}}{\sqrt{2}} \right)^2 \times R$$

half power frequency

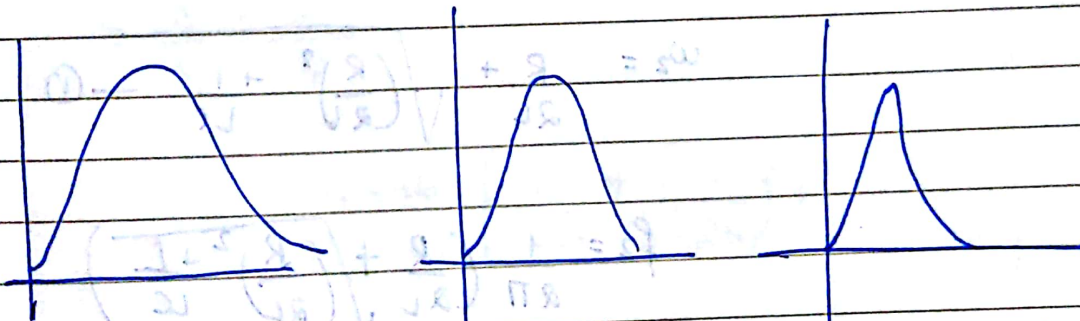

BW more
 $R \uparrow$

$Q = \text{less}$
less selectivity

less
 $R \downarrow$

very less
 $R \text{ very less}$
high selectivity
 $\uparrow Q \text{ high}$

Half path frequency

Der

ω_1 & ω_2

$$I = \frac{I_{\max}}{\sqrt{2}}$$

$$\frac{V}{Z} = \frac{I_{\max}}{\sqrt{2}}$$

$$\frac{V}{Z} = \frac{V}{R\sqrt{2}}$$

$$Z = \sqrt{2} R$$

$$\sqrt{R^2 + (X_L - X_C)^2} = \sqrt{2} R$$

$$R = X_L - X_C$$

$$R = \omega_2 L - \frac{1}{\omega_2 C}$$

$$\omega_2^2 LC - \omega_2 CR - 1 = 0$$

$$\omega_2 = \frac{(RC) \pm \sqrt{(RC)^2 + 4LC}}{2LC}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \text{--- (1)}$$

$$f_2 = \frac{1}{2\pi} \left(\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right)$$

$$X_C - X_L = R$$

$$\omega^2 LC + \omega CR - 1 = 0$$

$$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \text{--- (2)}$$

$$f_1 = \frac{1}{2\pi} (\omega_1)$$

$$\text{Bandwidth} = \omega_2 - \omega_1$$

$$Q = \frac{\omega_0 L}{R}$$

$$\frac{R}{L} = \frac{\omega_0}{Q}$$

$$BW = \omega_2 - \omega_1$$

$$= \frac{R}{L} \text{ rad/sec}$$

$$= \frac{f_0}{Q} \text{ freq}$$

$$\omega_0 = \frac{1}{LC} \text{ rad/sec}$$

$$\Rightarrow \frac{R}{L} = \frac{\omega_0}{Q}$$

$$\omega_2 = \omega_0 \left[\frac{-1}{2Q_0} + \sqrt{\left(\frac{1}{2Q_0}\right)^2 + 1} \right]$$

2) Resonant freq is the GM of the 2 half path frequencies

$$\rightarrow R = \omega L - \frac{1}{\omega C}$$

at ω_1

$$R = \frac{1}{\omega_1 C} - \omega_1 L$$

at ω_2

$$R = \omega_2 L - \frac{1}{\omega_2 C}$$

equating the above eq:

$$\frac{1}{\omega_1 C} - \omega_1 L = \omega_2 L - \frac{1}{\omega_2 C}$$

$$\frac{1}{\omega_1 C} + \frac{1}{\omega_2 C} = \omega_2 L + \omega_1 L$$

$$\frac{1}{C} \left(\frac{\omega_2 + \omega_1}{\omega_1 \omega_2} \right) = L (\omega_1 + \omega_2)$$

$$\omega_1 \cdot \omega_2 = \frac{1}{LC}$$

WKT,

$$\omega_0^2 = \frac{1}{LC}$$


$$\omega_0^2 = \omega_1 \omega_2$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

or

$$f_0 = \sqrt{f_1 f_2}$$

⇒ Parallel Resonance (Rejector ciruits).

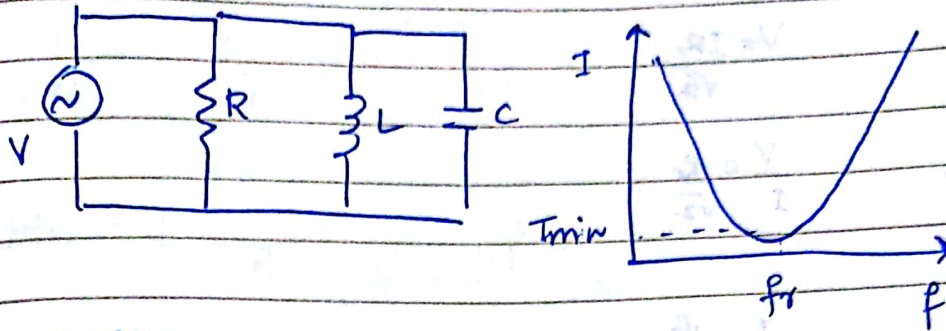

At resonance

$R = \max$

$I = \min$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Admittance:

$$Y = Y_R + Y_C + Y_L$$

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$|Y| = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2} \quad \text{--- (1)}$$

Deriv of ω_1 & ω_2

$$V = \frac{V_0}{\sqrt{2}}$$

$$V = \frac{IR}{\sqrt{2}}$$

$$\frac{V}{I} = \frac{R}{\sqrt{2}}$$

$$\frac{I}{V} = \frac{\sqrt{2}}{R}$$

$$|Y| = \frac{\sqrt{2}}{R}$$

$$|Y|^2 = \frac{2}{R}$$

After equating both (this is $\otimes$)

$$\left(\frac{2}{R^2}\right) = \left(\frac{1}{R^2}\right) + \left(\omega_c - \frac{1}{\omega_L}\right)^2$$

$$\frac{1}{R^2} = \left(\omega_c - \frac{1}{\omega_L}\right)^2$$

$$\omega_c - \frac{1}{\omega_L} = \frac{1}{R}$$

$$\omega_2^2 LC - \omega_2 L - R = 0$$

$$\omega_2 = \left(\frac{L + \sqrt{L^2 - 4LCR^2}}{2LCR} \right)$$

$$\omega_2 = \frac{1}{2CR} + \sqrt{\left(\frac{1}{2CR}\right)^2 + \frac{1}{LC}}$$

$$\omega_1 = -\left(\frac{1}{2CR}\right) + \sqrt{\left(\frac{1}{2CR}\right)^2 + \frac{1}{LC}}$$

$$BW = \omega_2 - \omega_1 = \frac{1}{CR}$$

$$\frac{BW}{2} = \frac{1}{2CR}$$

$$\omega_2 = \frac{BW}{2} + \sqrt{\left(\frac{BW}{2}\right)^2 + \omega_c^2}$$

$$\left(\frac{2}{R^2}\right) = \left(\frac{1}{R^2}\right) + \left(\omega_c - \frac{1}{\omega L}\right)^2$$

$$\left(\omega_c - \frac{1}{\omega L}\right)^2 = \frac{1}{R^2}$$

$$\omega_c - \frac{1}{\omega L} = \frac{1}{R}$$

$$\omega_2^2 LC - \omega_2 L - R = 0$$

$$\omega_2 = \left(\frac{1}{2CR} + \sqrt{\left(\frac{1}{2CR}\right)^2 + \frac{1}{LC}} \right)$$

$$\omega_2 = \frac{1}{2CR} + \sqrt{\left(\frac{1}{2CR}\right)^2 + \frac{1}{LC}}$$

$$\omega_1 = -\left(\frac{1}{2CR}\right) + \sqrt{\left(\frac{1}{2CR}\right)^2 + \frac{1}{LC}}$$

$$B\omega = \omega_2 - \omega_1$$




Quality factor


- $Q_0 = \omega_0 CR$

- $Q = \frac{R}{\omega_0 L}$

$$Q = \frac{R}{\omega_0 L}$$

- $Q = \frac{R}{L} \times \sqrt{LC}$

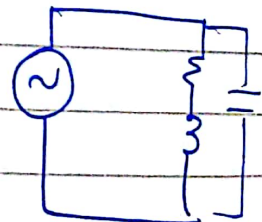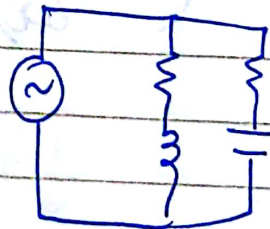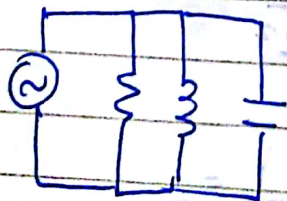

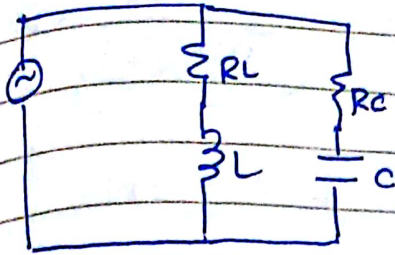

$$Y_L = \frac{1}{R_L + j\omega L}$$

$$Y_C = \frac{1}{R_C - j \frac{1}{\omega C}} = \frac{R_C + j \frac{1}{\omega C}}{R_C^2 + \frac{1}{\omega^2 C^2}}$$

Total admittance

$$Y = Y_L + Y_C$$

$$Y = \left[\frac{R_L}{R_L^2 + \omega^2 L^2} + \frac{R_C}{R_C^2 + 1} \right] - j \left[\frac{\omega L}{R_L^2 + \omega^2 L^2} - \frac{1/\omega C}{R_C^2 + 1/\omega^2 C^2} \right]$$

@ Resonance

$$\frac{\omega L}{R_L^2 + \omega^2 L^2} = \frac{1/\omega C}{R_C^2 + \frac{1}{\omega^2 C^2}}$$

$$\frac{\omega r L}{R_L^2 + \omega^2 L^2} = \frac{\omega r C}{1 + \omega^2 R_C^2 C^2}$$

$$L[1 + \omega^2 R_C^2 C^2] = C[R_L^2 + \omega^2 L^2]$$

$$\omega^2 [L R_C^2 C^2 - L^2 C] = C R_L^2 - L$$

$$\omega^2 L C [R_C^2 C - L] = R_L^2 C - L$$

$$\omega_r^2 = \frac{1}{LC} \frac{(R_L^2 C^2 - L)}{(R_L^2 C - L)}$$

$$\omega_r = \sqrt{\frac{1}{LC} \left(\frac{L - CR_L^2}{L - CR_L^2} \right)}$$


$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} \left(\frac{L - CR_L^2}{L - CR_L^2} \right)}$$

$$\text{if } R_L = 0 \quad f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R_L^2}{C^2}}$$

$$\text{if } R_L = R_c, \quad f_r = \frac{1}{2\pi\sqrt{LC}}$$

$\neq$

• Impedance at Resonance

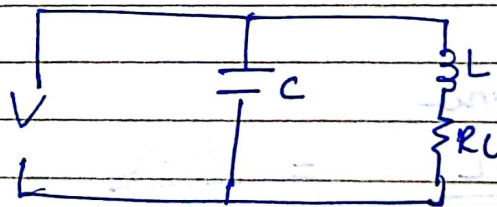

$$Y = Y_L + Y_C$$

$$Y = \frac{R_L}{R_L^2 + \omega^2 L^2} - j \left(\frac{\omega L}{R_L^2 + \omega^2 L^2} - \omega C \right)$$

② Resonance



$$\frac{\omega L}{R_L^2 + \omega^2 L^2} = \omega C$$

$$R_L^2 + \omega^2 L^2 = \frac{L}{C}$$

$$Y_0 = \frac{R_L}{R_L^2 + \omega^2 L^2} \rightarrow \frac{1}{C}$$

$$Y_0 = \frac{R_L C}{L} \Rightarrow \boxed{Z_T = \frac{L}{CR_L}} \text{ imp @ Resonance}$$

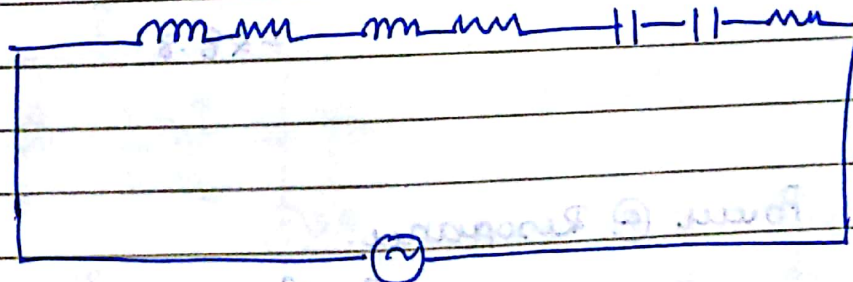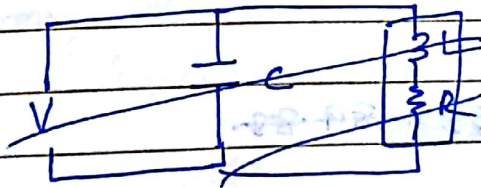Q. 2 coils of one of 0.5Ω & $L_1 = 32 \text{ mH}$ & other 1.3Ω & $L_2 = 18 \text{ mH}$ and 2 capacitors $C_1 = 20 \mu\text{F}$ $C_2 = 60 \mu\text{F}$ are all connected in series with 0.2Ω resistance, Determine resonance frequency Q of the coils Q of entire circuit, power dissipated at resonance if the voltage applied is 10 V .



$$R_T = 0.5 + 1.3 + 0.2$$

$$R_T = 2 \Omega$$

$$L_T = 50 \text{ mH}$$

$$C_T = 15 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{50 \times 10^{-3} \times 15 \times 10^{-6}}}$$

$$\omega_0 = 1154.7 \text{ rad/sec.}$$

$$Q_1 = \frac{\omega_0 L_1}{R}$$

$$= \frac{1154.7 \times 32 \times 10^{-3}}{0.5}$$

$$= 73.9$$

$$Q_2 = \frac{\omega_0 L_2}{R}$$

$$= \frac{1154.7 \times 80 \times 10^{-3}}{1.3}$$

$$= 70.98$$

$$Q_T = Q_1 + Q_2 = 144.88$$

$$Q_1 = \frac{\omega_0 L_T}{R_T} = \frac{1154.7 \times 50 \times 10^{-3}}{2}$$

$$= 28.8$$

Power @ Resonance:

$$P = \frac{V^2}{R_T} = \frac{10^2}{2} = 50 \text{ W}$$

Q) Put the values of the circuit parameters whose plot is shown in fig below, what are the new values of ω_0 & BW, if C is increased 4 times given data is